

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 40492

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2021.

Fifth Semester

Electrical and Electronics Engineering

EE 8501 – POWER SYSTEM ANALYSIS

(Regulations 2017)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. How the base values are chosen in per unit representation of a power system?
2. Define bus admittance matrix.
3. What is a bus?
4. What is P-Q bus in power flow analysis?
5. What are the reactances used in the analysis of symmetrical faults on the synchronous machines as its equivalent reactance?
6. What is the need for short circuit analysis?
7. Name any two methods of reducing short circuit current.
8. What are unsymmetrical faults?
9. Define power angle.
10. What is the use of swing curve?

PART B — (5 × 13 = 65 marks)

11. (a) Obtain the per unit impedance (reactance) diagram of the power system shown in Figure 11(a).

Generator No. 1 : 30 MVA, 10.5 kV, $X'' = 1.6 \text{ Ohm}$

Generator No. 2 : 15 MVA, 6.6 kV, $X'' = 1.2 \text{ Ohm}$

Generator No.3 : 25 MVA, 6.6 kV, $X'' = 0.56 \text{ Ohm}$


Transformer T1 (3phase) : 15 MVA, 33/11 kV, $X = 15.2 \text{ Ohm}$ per phase on HT side

Transformer T2 (3phase) : 15 MVA, 33/6.2 kV, $X = 16 \text{ Ohm}$ per phase on HT side

Transmission line : 20.5 Ohm/phase

Load A : 15MW, 11kV, 0.9 p.f. lagging

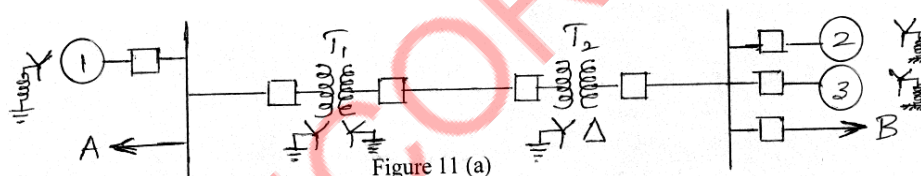Load B : 40 MW, 6.6 kV, 0.85 lagging p.f.



Or

- (b) The parameters of a four system are as under:

Line No.	Line Starting No.	Line Ending No.	Line Impedence (pu)	Line Charging Admittance (pu)
1	1	2	$0.2 + j0.8$	$j0.02$
2	2	3	$0.3 + j0.9$	$j0.03$
3	2	4	$0.25 + j1.0$	$j0.04$
4	3	4	$0.2 + j0.8$	$j0.02$
5	1	3	$0.1 + j0.4$	$j0.01$

Draw the network and find bus admittance matrix.

12. (a) Derive the load flow algorithm using Newton Rapson method with flow chart and discuss the advantages of the method.

Or

- (b) In the power system network shown in Figure 12 (b), bus 1 is slack bus with $V_1 = 1.0 + j0.0$ per unit and bus 2 is a load bus with $S_2 = 280\text{MW} + j60\text{MVAR}$. The line impedance on a base of 100MVA is $Z = 0.02 + j0.04$ per unit. Using Gauss — Seidal method, give V_2 . Use an initial estimate of $V_2^{(10)} = 1.0 + j0.0$ and perform four iterations. Also find S_1 and the real, reactive power loss in the line, assuming that the bus voltages have converged.

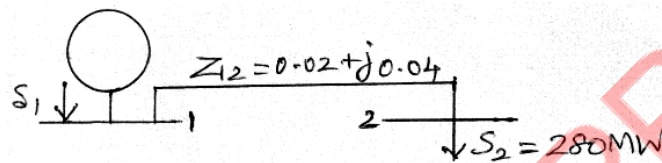


Figure 12 (b)

13. (a) Explain the step by step procedure for systematic fault analysis using bus impedance matrix.

Or

- (b) Two synchronous machines are connected through three phase transformers to the transmission line shown in Figure 13 (b) the ratings and reactance of the machines and transformers are

Machine 1 and 2: 100 MVA, 20kV; $X_d'' = X_1 = X_2 = 20\%$, $X_0 = 4\%$, $X_n = 5\%$
Transformers T_1 and $T_2 = 100 \text{ MVA}$, $20 \Delta / 345 \text{ Y kV}$; $X = 8\%$.

On a chosen base of 100 MVA, 345 kV in the transmission line circuit the line reactances are $X_1 = X_2 = 15\%$ and $X_0 = 50\%$. Draw each of the three sequence networks and find the zero sequence bus impedance matrixes by means of Z bus building algorithm.

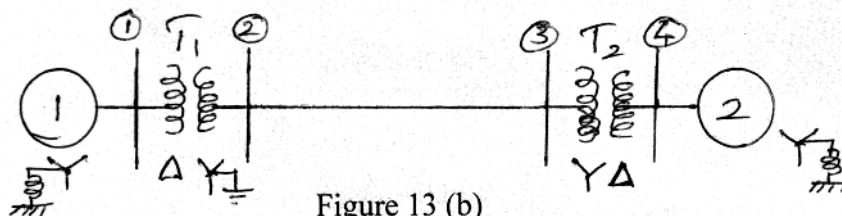


Figure 13 (b)

14. (a) Examine the sequence network for a double line to ground (LLG) fault.

Or

- (b) The one-line diagram of a power system is shown below in Figure 14 (b).

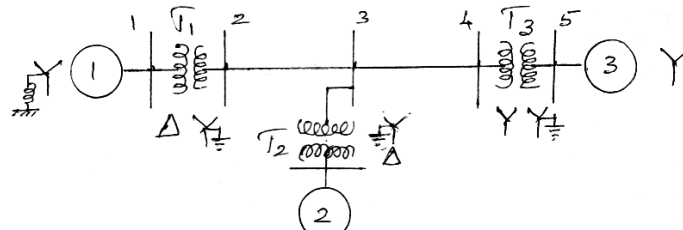


Figure 14 (b)

The following are the p.u. reactances of different elements on a common base

Generator 1: $X_{g0} = 0.075$; $X_n = 0.075$; $X_1 = X_2 = 0.25$

Generator 2: $X_{g0} = 0.15$; $X_n = 0.15$; $X_1 = X_2 = 0.2$

Generator 3: $X_{g0} = 0.072$; $X_1 = X_2 = 0.15$

Transformer 1: $X_0 = X_1 = X_2 = 0.12$

Transformer 2: $X_0 = X_1 = X_2 = 0.24$

Transformer 3: $X_0 = X_1 = X_2 = 0.1276$

Transmission line 2—3: $X_0 = 0.5671$; $X_1 = X_2 = 0.18$

Transmission line 3—5: $X_0 = 0.4764$; $X_1 = X_2 = 0.12$

Prepare the three sequence networks and determine reactances Z_{bus0} , Z_{bus1} and Z_{bus2} .

15. (a) Describe the equal area criterion for transient stability analysis of a system.

Or

- (b) (i) A 2pole, 50 Hz, 11kv turbo alternator has a rating of 100 MW, power factor 0.85 lagging. The rotor has a moment of inertia of 10,000 kgm². Calculate H and M.
- (ii) A three phase fault is applied at the point P as shown in Figure 15(b) (ii) below. Find the critical clearing angle for clearing the fault with simultaneous opening of the breakers 1 and 2. The reactance values of various components are indicated in the diagram. The generator is delivering 1.0 p.u. power at the instant preceding the fault.

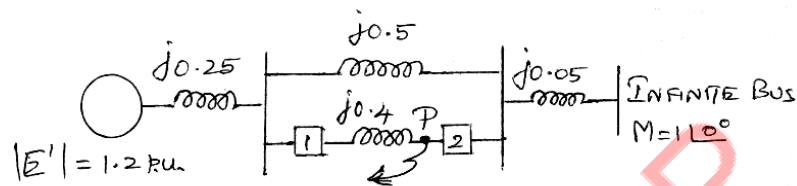


Figure 15 (b) (ii)

PART C — (1 × 15 = 15 marks)

16. (a) Figure 16 (a) shows the one line diagram of a simple three bus power system with generation at buses at 1 and 2. The voltage at bus 1 is $V = 1 + j0.0$ V per unit. Voltage magnitude at bus 2 is fixed at 1.05 pu. with a real power generation of 400 MW. A Load consisting of 500MW and 400 MVAR base. For the purpose of hand calculation, line resistance and line charging susceptances are neglected.

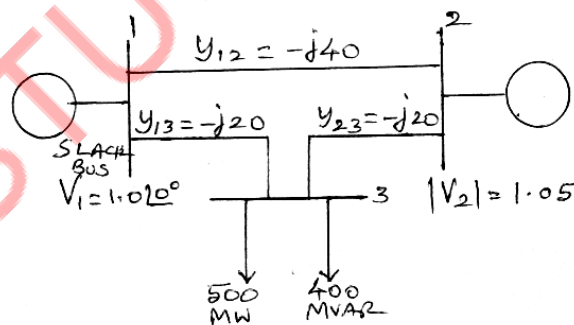


Figure 16 (a)

Using Newton-Raphson method, start with the initial estimates of $V_2^0 = 1.05 + j0.0$ and $V_3^0 = 1.05 + j0.0$, and keeping $|V_2| = 1.05$ pu., examine the phasor values V_2 and V_3 . Perform two iterations.

Or

- (b) In the power system shown in figure 16(b) phase fault occurs at point P and the faulty line was opened a little late. Find the power output equations for the pre-fault during fault and post fault calculation. values are marked in p.v. reactances.

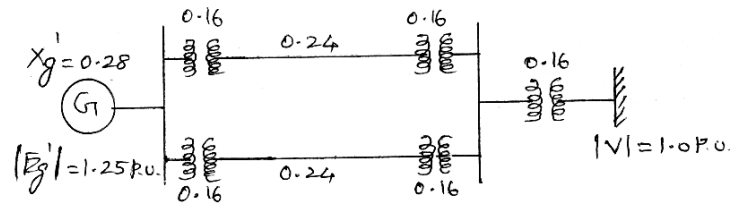


Figure 16(b)



Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : X 10399

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2020

Fifth Semester

Electrical and Electronics Engineering

EE 8501 – POWER SYSTEM ANALYSIS

(Regulations 2017)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

1. Give the representation of an off nominal transformer in power system.
2. Give the bus incidence matrix for the given power system.
3. State at least four applications of power flow studies in the planning and operation of electric power systems.
4. What is the need of slack bus for load flow analysis ?
5. Define Fault level of a bus in power system, give the expression in per unit.
6. What is the advantage of symmetrical components ?
7. The Z-bus method is very suitable for fault studies on large systems rather than Y bus. Why ?
8. Name the faults in which zero sequence currents are absent.
9. Define rotor angle stability.
10. State the significance of critical clearing time.

X 10399

-2-



PART – B

(5×13=65 Marks)

11. a) Fig. 1 shows a single-line diagram of a power system. The ratings of generators and transformers are :

Generator G_1 : 30 MVA, 6.6 kV, $j0.2$ pu

Generator G_2 : 15 MVA, 6.6 kV, $j0.15$ pu

Motor M_1 : 15 MVA, 6.6 kV, $j0.15$ pu

Transformer T_1 : 30 MVA, 6.6 Δ – 115 Y kV, $j0.2$ pu

Transformer T_2 : 15 MVA, 6.6 Δ – 115 Y kV, $j0.1$ pu

Transformer T_3 : 15 MVA, 6.6 Δ – 115 Y kV, $j0.1$ pu

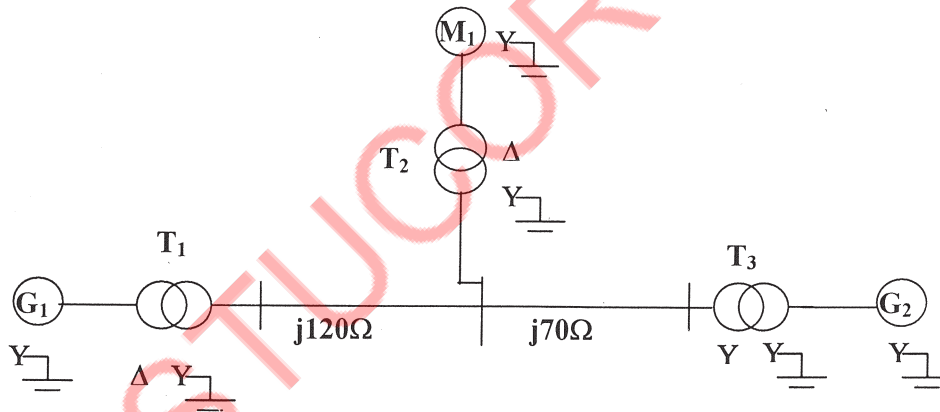


Fig. 1

Draw impedance diagram with all values in pu on a base of 30 MVA, 6.6 kV in the circuit of generator G_1 . (13)

(OR)

- b) i) Subtransient reactance of a 500 MVA, 18 kV generator is 0.25 pu on its ratings. It is connected to a network through a 20/400 kV transformer. Find out the subtransient reactance of the generator on a base of 100 MVA and 20 kV. (4)
- ii) Derive the Π model for a transformer with off-nominal tap-ratio. (9)



12. a) Fig. 2 shows the one-line diagram of a simple three-bus power system with generation at bus 1. The line impedances are marked in per unit on a 100 MVA base. Find out the bus voltages after two iterations using Gauss-Seidel method. (13)

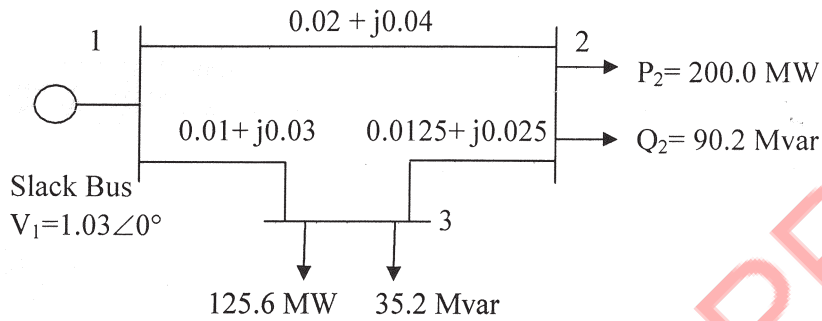


Fig. 2

(OR)

- b) A sample system is described in Fig. 3. The line data, bus data and load flow results are given Table 1 and 2. Compute the following :
- Slack bus power. (4)
 - Reactive Power Generation from G2. (3)
 - Line flows. (3)
 - Line losses. (3)

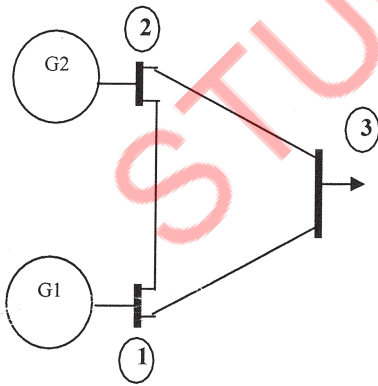


Fig. 3

Table 1 Line Data

Line	Admittance	Half line charging admittance
1-2	$1.47 - j5.88$	$j0.15$
1-3	$2.94 - j11.77$	$j0.07$
2-3	$2.75 - j9.17$	$j0.04$

Table 2 Bus Data and Load Data

Bus	Bus voltage	Generation		Load	
		MW	MVAR	MW	MVAR
1	$1.04 \angle 0^\circ$	--	--	0	0
2	$1.02 \angle -3.09^\circ$	100	-	50	20
3	$0.93 \angle -7.01^\circ$	0	0	250	150

X 10399

-4-



13. a) A synchronous generator and motor are rated 30000 kVA, 13.2 kV and both have subtransient reactances of 20%. The line connecting them has a reactance of 10% on the base of the machine ratings. The motor is drawing 20000 kW at 0.8 p.f. leading and a terminal voltage of 12.8 kV when a symmetrical three-phase fault occurs at the motor terminals. Find the subtransient currents in the generator, the motor, and the fault by using the internal voltages of the machines. (13)

(OR)

- b) Deduce the Z bus building algorithm. Illustrate the step by step procedure of Z bus formulation. (13)
14. a) Derive the relationship for fault currents in terms of symmetrical components when there is a line-to-line (L-L) fault between phase b and c. Also draw a diagram showing interconnection of sequence networks for L-L fault. (13)

(OR)

- b) A single line to ground fault (phase a) occurs in a transmission system at transformer T1 star terminal. Draw the sequence network. Find current fed to fault.

Given :

Rating of generator is 1200 kVA, 600 V with $X' = X_2 = 10\%$, $X_0 = 5\%$ Rating of each machine is 600 kVA, 600 V with $X' = X_2 = 12\%$, $X_0 = 6\%$

Each transformer is rated 1200 MVA, 600 V on delta side and 3.3 kV on star side, with leakage reactance of 5%.

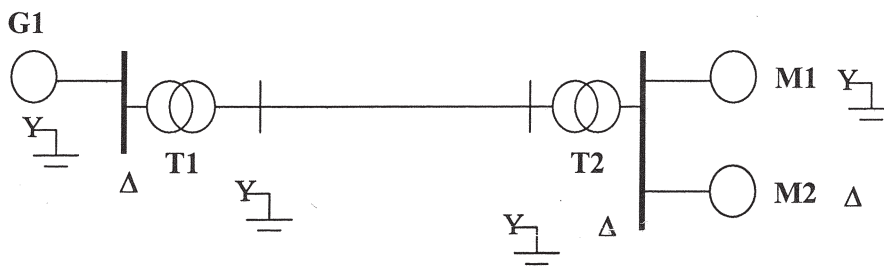
Reactance of the transmission line is $X_1 = 10\%$, $X_2 = 10\%$, $X_0 = 20\%$. (13)

Fig. 4



15. a) What is Equal Area Criterion ? Using equal area criterion, drive an expression for critical clearing angle and critical clearing time for a system having a generator feeding a large system through a double circuit line with a temporary three-phase bolted fault on one of the line at the sending end. (13)

(OR)

- b) Discuss the procedure for solving the swing equation using modified-Euler method. (13)

PART – C

(1×15=15 Marks)

16. a) Fig. 5 shows transmission network. The pu reactances of the equipments are as shown. The voltage behind transient reactance of generator is 1.1 pu. The system is transmitting 1 pu real power when fault occurs at the middle of one of the line. Determine :

i) transfer reactance for prefault, during fault and post fault conditions and (8)

ii) critical clearing angle for the fault at the mid-point of the line. (7)

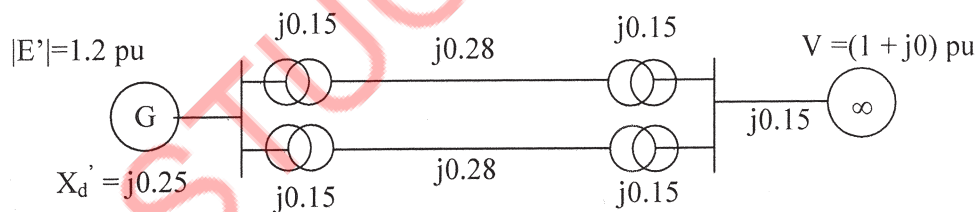


Fig. 5

(OR)

- b) The one line diagram of a simple power system is shown in Fig. 6. The neutral of each generator is grounded through a current-limiting reactor of $0.25/3$ pu on a 100 MVA base. The system data expressed in per unit on a common 100 MVA base is tabulated below. The generators are running on no-load at their rated voltage and rated frequency with their emfs in phase. Using bus impedance matrix determine the fault current for a single line to ground fault at bus 3 through a fault impedance $Z_f = j0.1$ pu. Also determine the bus voltages and line currents during fault. (15)



Element	Base MVA	V-rating	X_1	X_2	X_0
G1	100	20 kV	0.15	0.15	0.05
G2	100	20 kV	0.15	0.15	0.05
T1	100	20/220 kV	0.1	0.1	0.1
T2	100	20/220 kV	0.1	0.1	0.1
L12	100	220 kV	0.125	0.125	0.3
L13	100	220 kV	0.15	0.15	0.35
L23	100	220 kV	0.25	0.25	0.7125


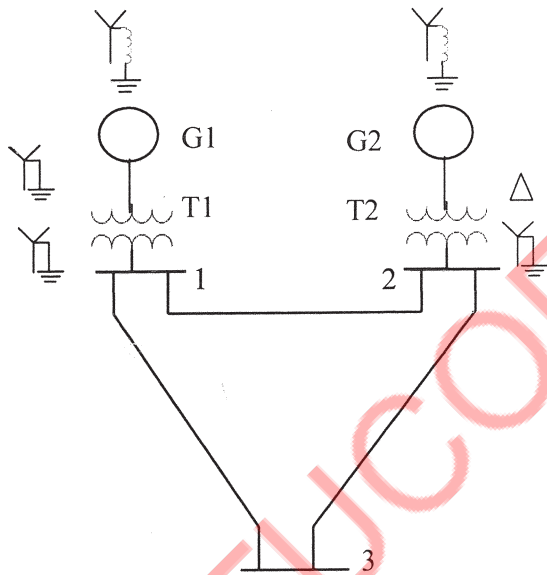


Fig. 6

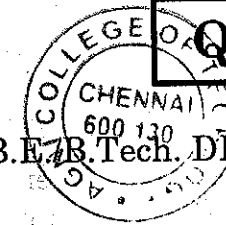

Question Paper Code : 90204

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2019

Fifth Semester

Electrical and Electronics Engineering

EE 8501 – POWER SYSTEM ANALYSIS

(Regulations 2017)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

1. What are the needs for power system planning ?
2. Define bus incidence matrix.
3. What is slack bus ?
4. What are the advantages of N-R method ?
5. What do you mean by symmetrical faults ?
6. What is the need for short circuit analysis ?
7. Define positive sequence impedance.
8. Name the various unsymmetrical faults in a power system.
9. Define steady state stability.
10. State equal area criterion.

PART - B

(5×13=65 Marks)

11. a) Calculate the per unit quantities of the given one-line diagram. T_2 is composed of three single phase units each rated at 30 MVA, 66/10 kV with 5% reactance. Take generator rating as base.

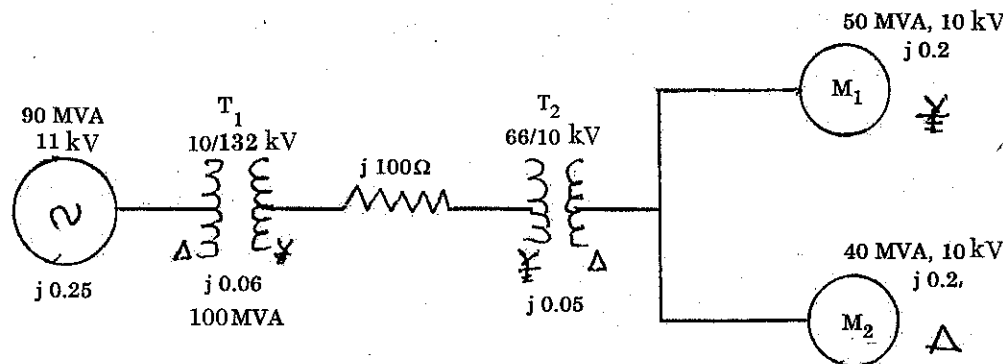


Figure 11(a)

(OR)

- b) Determine the bus admittance matrix for the given power system.

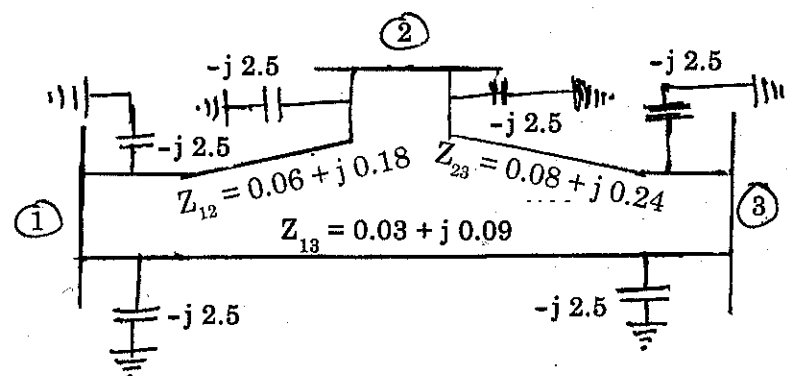


Figure 11(b)

12. a) Derive load flow algorithm using Gauss – Seidel method with flow chart and discuss the advantages of the method.

(OR)

- b) The one-line diagram of a simple three bus power system with generators at bus 1 and 2. The magnitude of voltage at bus 1 and 2 are adjusted to 1.06 and 1.05 p.u. The scheduled load at bus 2 is marked. Line impedances are marked to per unit on a 100 MVA base and the line charging is neglected. Solve by N-R method.

Bus Number	Type	Generator (p.u.)		Load (p.u.)		Voltage (p.u.)	Angle (deg)	Reactive Power Limit	
		P_g	Q_g	P_d	Q_d			Q_{min}	Q_{max}
1	Slack	0	0	0	0	1.06	0	—	—
2	PQ	0	0	6	2.5	0	0	—	—
3	PV	2	0	0	0	1.05	0	0.1	2.5

Element	Bus Code	Self-impedance (Ω)
1	1-2	$0.01 + j0.05$
2	1-3	$0.07 + j0.2$
3	2-3	$0.02 + j0.15$

13. a) Describe the construction of Bus impedance matrix (Z_{Bus}) using building algorithm for lines without mutual coupling.

(OR)

- b) A four bus sample power system is shown in Figure 13(b). Perform the short circuit analysis for a three phase fault on bus 4 are given below.

G_1 : 11.2 kV, 100 MVA, $X = 0.08$ p.u.

G_2 : 11.2 kV, 100 MVA, $X = 0.08$ p.u.

T_1 : 11/110 kV, 100 MVA, $X = 0.06$ p.u.

T_2 : 11/110 kV, 100 MVA, $X = 0.06$ p.u.

Assume pre fault voltages 1.0 p.u. and pre fault currents to be zero.

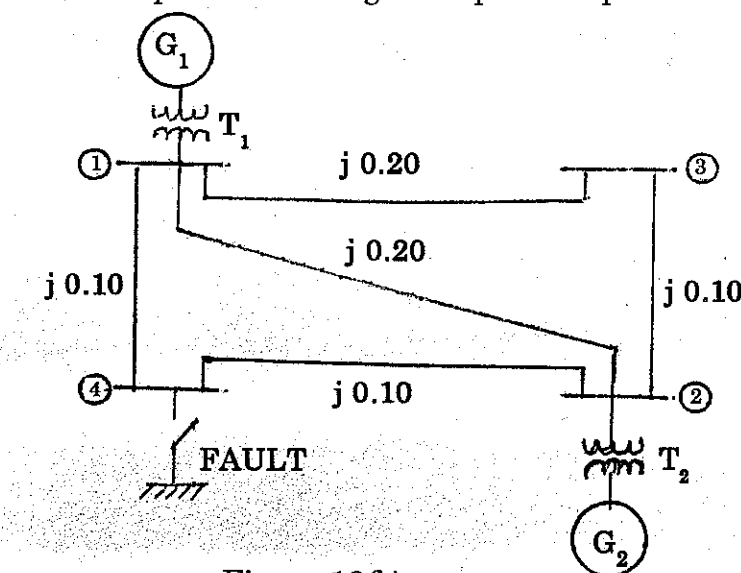


Figure 13(b)

14. a) Derive the expression for fault current in line-to-line fault on an unloaded generator in terms of symmetrical components.

(OR)

- b) A 50 MVA, 11 kV synchronous generator has a sub-transient reactance of 20%. The generator supplies two motors over a transmission line with transformers at both ends as shown in Figure 14(b). The motors have rated inputs of 30 and 15 MVA, both 10 kV, with 25% sub-transient reactance. The three phase transformers are both rated 60 MVA, 10.8/121 kV, with leakage reactance of 10% each. Current limiting reactors of 2.5 ohms each connected in the neutral of the generator and the motor number 2. The zero sequence reactance of the transmission line is 300 ohms. The series reactance of the line is 100 ohms. Draw the positive, negative and zero sequence networks.

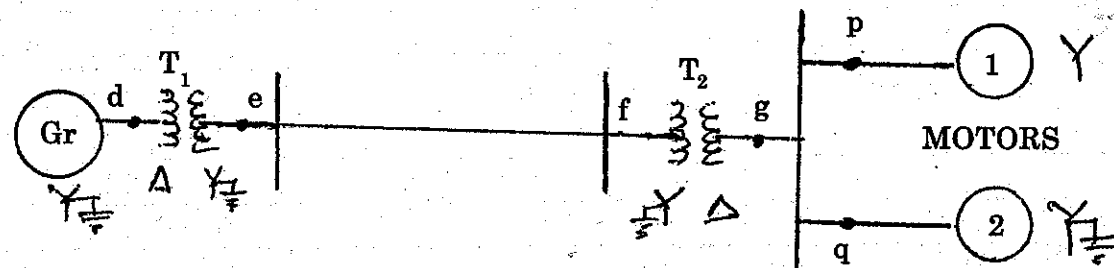


Figure 14(b)

15. a) Derive swing equation used for stability studies in power system.

(OR)

- b) A single line diagram of a system is shown in Figure 15(b). All the values are in per unit on a common base. The power delivered into bus 2 is 1.0 p.u. at 0.80 power factor lagging. Obtain the power angle equation and the swing equation for the system. Neglect all losses.

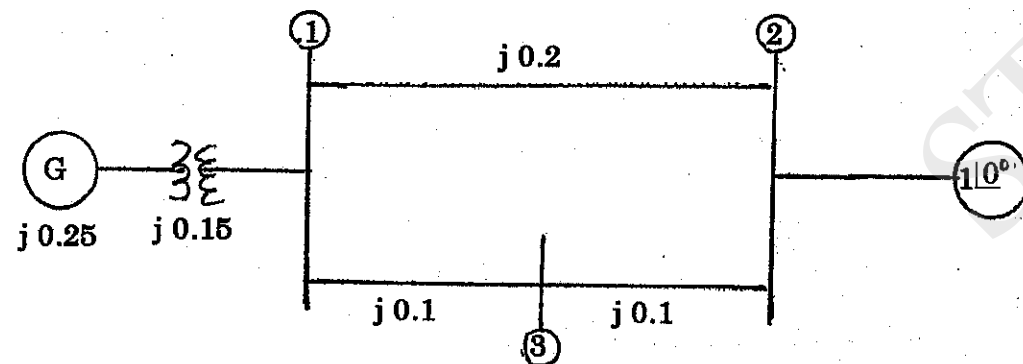


Figure 15(b)

PART - C

(1×15=15 Marks)

16. a) Two alternators are operating in parallel and supplying a synchronous motor which is receiving 60 MW power at 0.8 power factor lagging at 6.0 kV. Single line diagram for this system is given in Figure 16(a). Data are given below. Compute the fault current when a single line to ground fault occurs at the middle of the line through a fault resistance of 4.033 ohm.

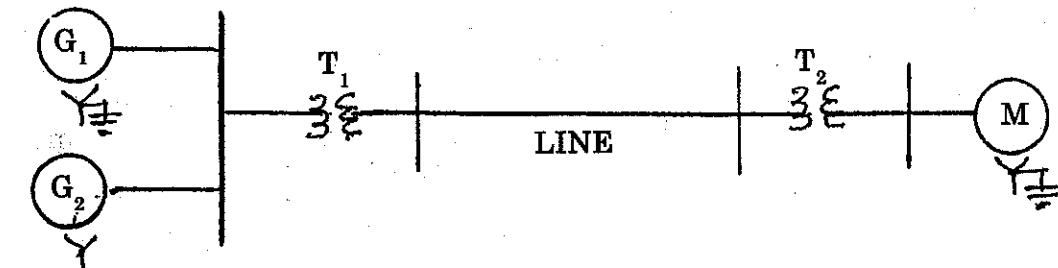


Figure 16(a)

(OR)

- b) Find the critical clearing angle for the system shown in Figure 16(b) for a 3Φ fault at the point P. The generator is delivering 1 p.u. power under balanced conditions.

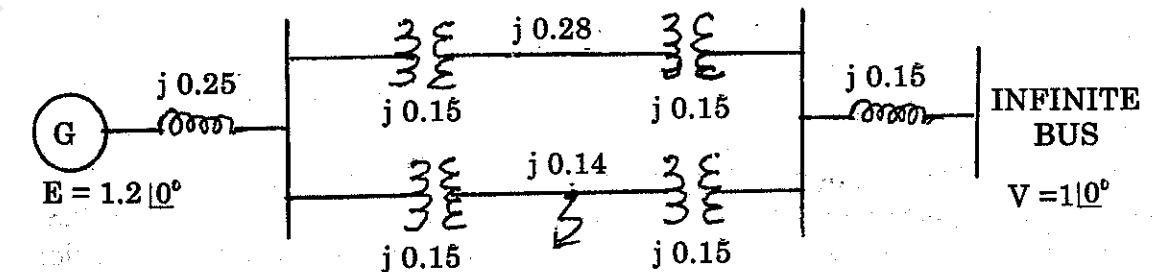


Figure 16(b)

14. (a) (i) Derive the expression for fault current in line to line fault on unloaded generator and draw an equivalent network showing the interconnection of networks. (10)
- (ii) A 3 phase salient pole synchronous generator is rated 30 MVA, 11 kV and has a direct axis subtransient reactance of 0.25 p.u. The negative and zero sequence reactances are 0.35 and 0.1 p.u. respectively. The neutral of the generator is solidly grounded. Calculate the subtransient current in the generator when a line to line fault occurs at the generator terminals with generator operating unloaded at rated voltage. (6)

Or

- (b) Two 11 kV, 20 MVA, three phase star connected generators operate in parallel as shown in Fig. The positive, negative and zero sequence reactance of each being respectively $j 0.18$, $j 0.15$, $j 0.10$ p.u. The star point of one of the generator is isolated and that of the other is earthed through a 2.0 ohm resistor. A Single line to Ground fault occurs at the terminals of one of the generators. Estimate (i) fault current (ii) current in grounded resistor and (iii) Voltage across grounding resistor. (16)

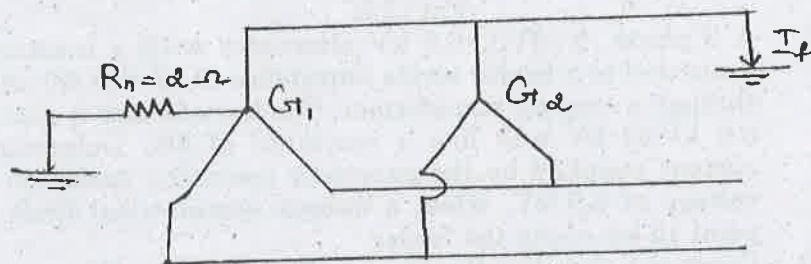


Fig.14.b.

15. (a) (i) Discuss the methods by which transient stability can be improved. (6)
- (ii) Find the critical clearing angle of the system shown in Fig. 15.a., for a 3 phase fault at the point 'F'. The generator is delivering 1.0 pu. power under prefault conditions. (10)

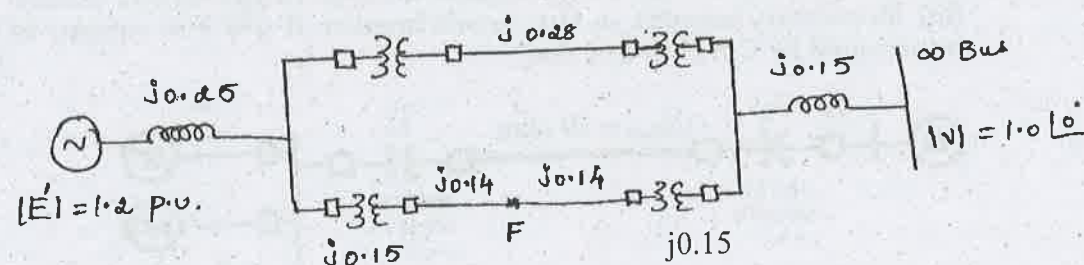


Fig.15.a.

Or

- (b) Derive the swing equation of a single machine connected to an infinite bus system and explain the steps of solution by Runge -Kutta method. (16)

Reg. No. :

Question Paper Code : 71776

B.E./B.Tech. DEGREE EXAMINATION, APRIL/MAY 2017.

Fifth Semester

Electrical and Electronics Engineering

EE 6501 — POWER SYSTEM ANALYSIS

(Regulations 2013)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

- What are the advantages of per unit computation.
- A Y corrected generator rated at 300 MVA, 33kV has a reactance of 1.24 p.u. Find the ohmic value of the reactance.
- Compare Newton Raphson and Gauss Seidal methods of load flow solutions.
- Write the quantities that are associated with each bus in a system.
- What is the significance of subtransient reactance and transient reactance in short circuit studies?
- For a fault at a given location, rank the various faults in the order of severity.
- Express the unbalanced voltages in terms of symmetrical components.
- Draw the zero-sequence network of Y/Δ transformer with neutral ungrounded.
- Define swing curve. What is the use of Swing curve?
- State Equal Area Criterion.

PART B — (5 × 16 = 80 marks)

- (a) 300 MVA, 20 kV, 3 Φ generator has sub transient reactance of 20%. The generator supplies 2 synchronous motors through a 64 km transmission line having transformers at both ends as shown in Fig.11.a. In this, T1 is a 3 Φ transformer 350 MVA, 20/230 kV, 10% reactance & T2 is made of 3 single phase transformer of rating 100 MVA, 127/13.2 kV, 10% reactance.

Series reactance of the transmission line is $0.5 \Omega/\text{km}$. The ratings of 2 motors are: M1=200 MVA, 13.2 kV, 20% & M2 = 100 MVA, 13.2 kV, 20%. Draw the reactance diagram with all the reactance's marked in p.u. Select the generator rating as base values. (16)


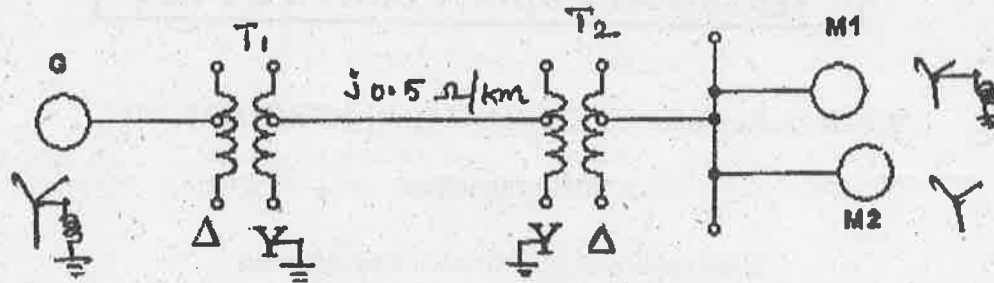


Fig.11.a.

Or

- (b) Form bus admittance matrix for the data given below using Singular transformation method. Take node '6' as reference node. (16)

Elements	Bus code	X (p.u.)
1	1-2	0.04
2	1-6	0.06
3	2-4	0.03
4	2-3	0.02
5	3-4	0.08
6	4-5	0.06
7	5-6	0.05

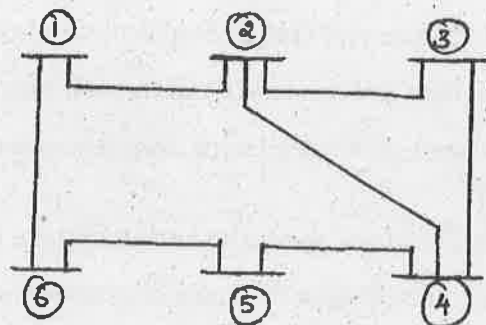

12. (a) With a neat flow chart, explain the computational procedure for load flow solution using Newton Raphson iterative method when the system contains all types of buses. (16)

Or

- (b) Single line diagram of a simple power system, with generators at busses 1 and 3 is shown in Fig. 12.b. The magnitude of voltage at bus 1 is 1.05 p.u. Voltage magnitude at bus 3 is fixed at 1.04 p.u. with active power generation of 200 MW. A load consisting of 400 MW and 250 MVAR is taken from bus 2. Line impedances are marked in p.u. on a 100 MVA base and the line charging susceptances are neglected.

Determine the voltage at buses 2 and 3 using Gauss-Seidal method at the end of first iteration. Also calculate Slack bus power.

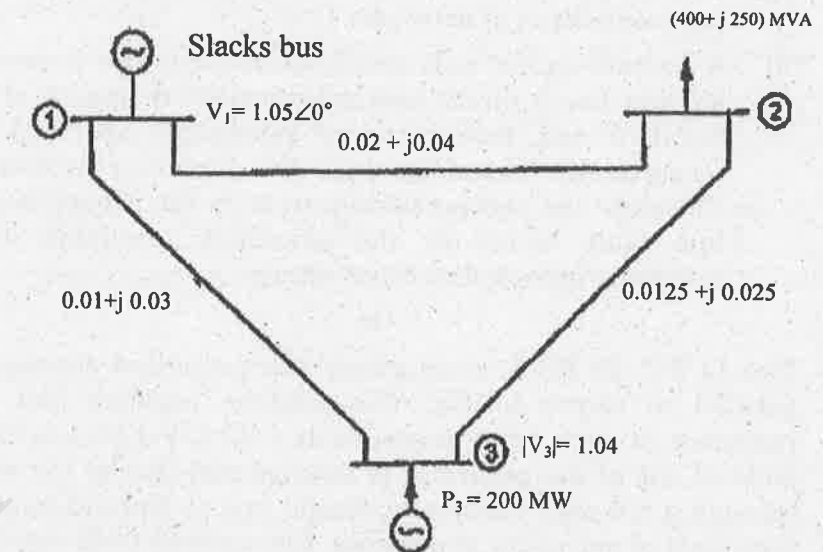


Fig.12.b.

13. (a) (i) A 3 phase, 5 MVA, 6.6 kV alternator with a reactance of 8% is connected to a feeder series impedance $(0.12 + j0.48) \text{ ohm/phase/km}$ through a step up transformer. The transformer is rated at 3 MVA, 6.6 kV/33 kV and has a reactance of 5%. Determine the fault current supplied by the generator operating under no load with a voltage of 6.9 kV, when a 3phase symmetrical fault occurs at a point 15 km along the feeder. (8)
- (ii) Draw the detailed flowchart, which explains how a symmetrical fault can be analyzed using Z_{BUS} . (8)

Or

- (b) A 100 MVA, 11 kV generator with $X'' = 0.20 \text{ p.u}$ is connected through a transformer and line to a bus bar that supplies three identical motor as shown in Fig and each motor has $X'' = 0.20 \text{ p.u}$ and $X' = 0.25 \text{ p.u}$ on a base of 20 MVA, 33 kV, the bus voltage at the motors is 33 kV when three phase balanced fault occurs at the point F. Calculate (i) Sub transient current in the fault (ii) Sub transient current in the circuit breaker B (iii) Momentary current in the circuit breaker B (iv) The current to be interrupted by C.B B in 5 cycles. (16)

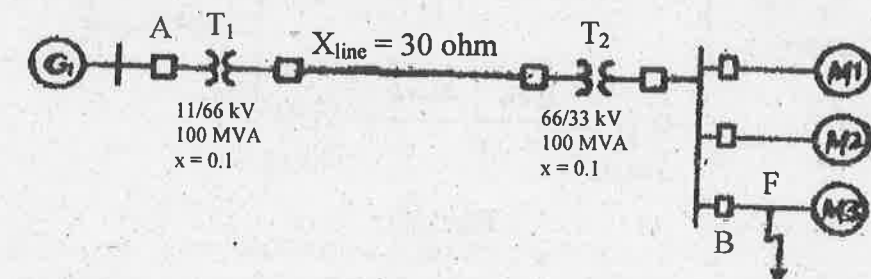


Fig.13.b.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 41003

16/05/18
Ad

B.E./B.Tech. DEGREE EXAMINATION, APRIL/MAY 2018

Fifth Semester

Electrical and Electronics Engineering

EE 6501 – POWER SYSTEM ANALYSIS

(Regulations 2013)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

1. Mention the requirements of planning the operation of a power system.
2. What is the need for base values ?
3. What is the need for slack bus in power flow analysis ?
4. Discuss the effect of acceleration factor in the load flow solution algorithm.
5. What is meant by fault calculations ?
6. What are all the assumption to be made to simplify the short circuit study ?
7. What is meant by symmetrical fault ?
8. Explain the concept of sequence impedances and sequence networks.
9. Define stability.
10. What is the significance of sub-transient reactance and transient reactance in short circuit studies ?

PART – B

(5×13=65 Marks)

11. a) i) In the single line diagram shown in figure 1, each three phase generator G is rated at 200 MVA, 13.8 kV and has reactances of 0.85 pu and are generating 1.15 pu. Transformer T_1 is rated at 500 MVA, 13.5 kV/220 kV and has a reactance of 8%. The transmission line has a reactance of 7.8 Ω .

Transformer T_2 has a rating of 400 MVA, 220 kV/33 kV and a reactance of 11%. The load is 250 MVA at a power factor of 0.85 lag. Convert all quantities to a common base of 500 MVA and 220 kV on the line and draw the circuit diagram with values expressed in pu. (10)

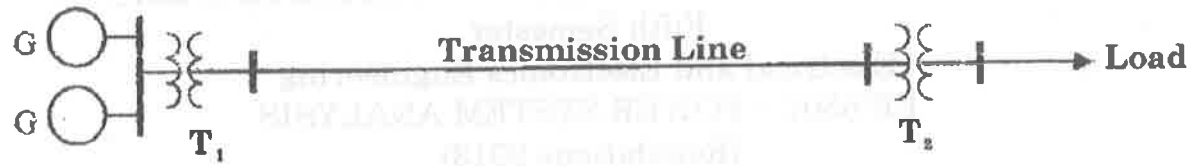


Figure 1

ii) A 200 MVA, 13.8 kV generator has a reactance of 0.85 p.u. and is generating 1.15 pu voltage. Determine the actual values of the line voltage, phase voltage and reactance. (3)

(OR)

b) Determine Z-bus for system whose reactance diagram is shown in given figure 2 where the impedance is given in p.u. preserve all the nodes. (13)

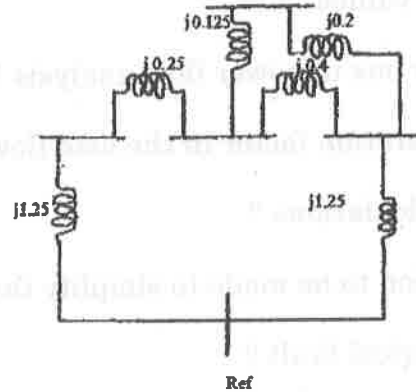


Figure 2

12. a) For the system shown in fig.3, determine the voltages at the end of the first iteration by Gauss-Seidal method. Assume base MVA as 100. (13)

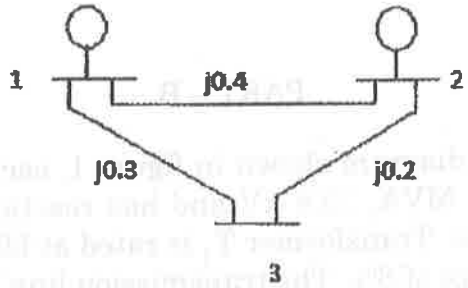


Figure 3

Bus No.	Voltage	Generator		Load		Q_{min}	Q_{max}
		P	Q	P	Q	MVAR	MVAR
1	$1.05 \angle 0^\circ$ p.u.	—	—	—	—	—	—
2	1.02 p.u.	0.3 p.u.	—	—	—	-10	100
3	—	—	—	0.4 p.u.	0.2 p.u.	—	—

(OR)

b) Perform an iteration of Newton-Raphson load flow method and determine the power flow solution for the given system. Take base MVA as 100. (13)

Line	Bus		R(p.u.)	X(p.u.)	Half line charging admittance ($Y_p/2$ (p.u.))
	From	To			
1	1	2	0.0839	0.5183	0.0636

Bus	P_L	Q_L
1	90	20
2	30	10

13. a) Figure shows a part of a power system, where the rest of the system at two points of coupling have been represented by their Thevenin's equivalent circuit (or by a voltage source of 1 pu together its fault level which corresponds to the per unit value of the effective Thevenin's impedance). (13)

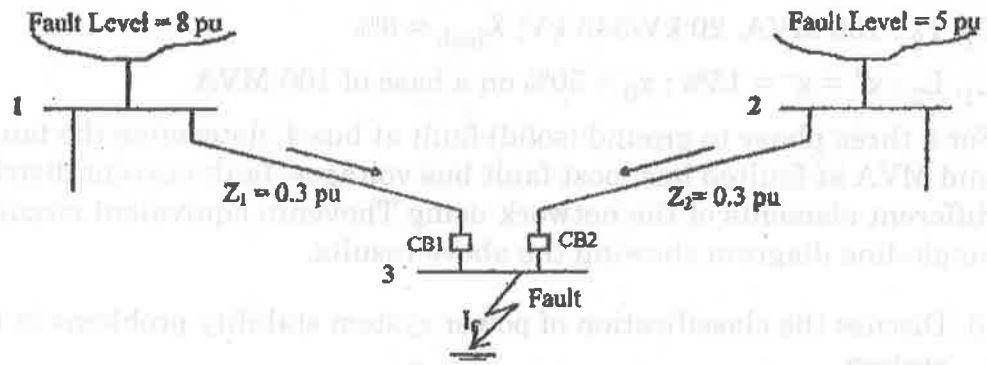


Figure 3

With CB1 and CB2 open, short circuit capacities are

SCC at bus 1 = 8 p.u. gives $Z_{g1} = 1/8 = 0.125$ pu

SCC at bus 2 = 5 p.u. gives $Z_{g2} = 1/5 = 0.20$ pu

Each of the lines are given to have a per unit impedance of 0.3 pu.

$Z_1 = Z_2 = 0.3$ p.u.


(OR)

- b) Explain how the fault current can be determined using Z_{bus} with neat flow chart. (13)

14. a) Brief discuss about the analysis of asymmetrical Faults in the power system with neat circuit diagrams and necessary equations. (13)

(OR)

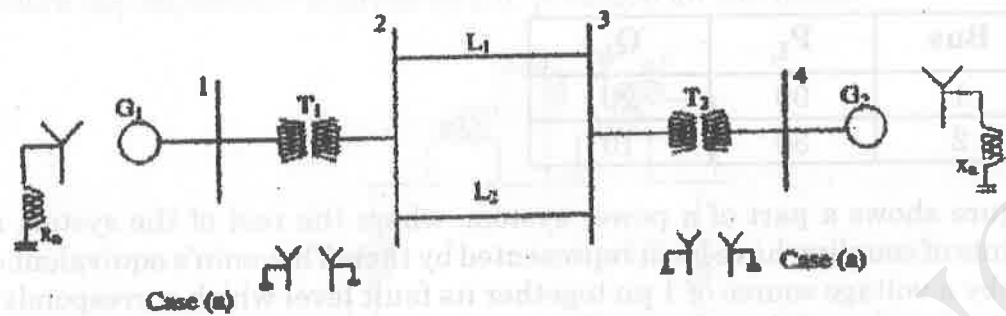- b) It is proposed to conduct fault analysis on two alternative configurations of the 4-bus system.



G_1, G_2 : 100 MVA, 20 kV, $x^+ = x^- = x_d'' = 20\%$; $x_0 = 4\%$; $x_n = 5\%$.

T_1, T_2 : 100 MVA, 20 kV/345 kV; $X_{leak} = 8\%$

L_1, L_2 : $x^+ = x^- = 15\%$; $x_0 = 50\%$ on a base of 100 MVA


For a three phase to ground (solid) fault at bus 4, determine the fault current and MVA at faulted bus, post fault bus voltages, fault current distribution in different elements of the network using Thevenin equivalent circuit. Draw a single-line diagram showing the above results. (13)

15. a) i) Discuss the classification of power system stability problems in the power system. (6)
ii) Derive the swing equation of a synchronous machine swinging against an infinite bus. (7)

(OR)

- b) A 60 Hz synchronous generator having inertia constant $H = 9.94$ MJ/MVA and a transient reactance $X_d' = 0.3$ per unit is connected to an infinite bus through a purely reactive circuit as shown in figure. Reactances are marked on the diagram on a common system base. The generator is delivering real power of 0.6 per unit, 0.8 power factor lagging to the infinite bus at a voltage of $V = 1$ per unit. Assume the per unit damping coefficient is $D = 0.138$. Consider a small disturbance of $\Delta\delta = 10^\circ = 0.1745$ radian (the breakers open and then quickly close). (13)

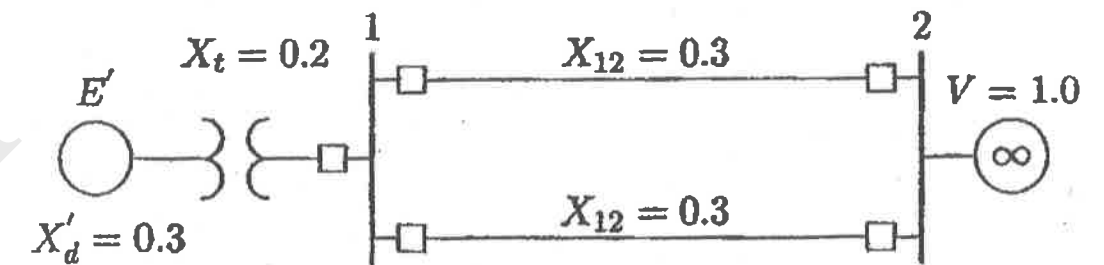- i) Obtain equations describing the motion of the rotor angle and the generator frequency.
ii) The maximum power input that can be applied without loss of synchronism.



PART - C

(1×15=15 Marks)

16. Describe the importance of stability analysis of in power system planning and operation. (15)

15. (a) Derive the swing equation of single machine connected to a infinite bus system and draw the swing curve. (13)
- Or
- (b) (i) Define and classify the power system stability (8)
- (ii) A 4-pole, 50 Hz, 11 KV turbo generator is rated 75 MW and 0.86 power factor lagging. The machine rotor has a moment of inertia of 9000 Kg-m². Find the inertia constant in MJ / MVA and M constant or momentum in MJ/elec degree. (5)

Or

PART C — (1 × 15 = 15 marks)

16. (a) Construct Z Bus using bus building algorithm : (15)

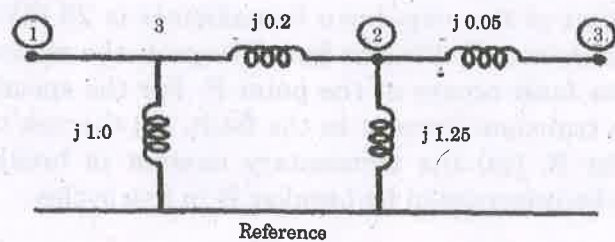


Fig. 16 (a)

Or

- (b) In the power system shown in Fig. 16(b) three phase fault occurs at point P and the faulty line was opened a little later. Find the power output equations for the pre-fault, during fault and post-fault conditions.

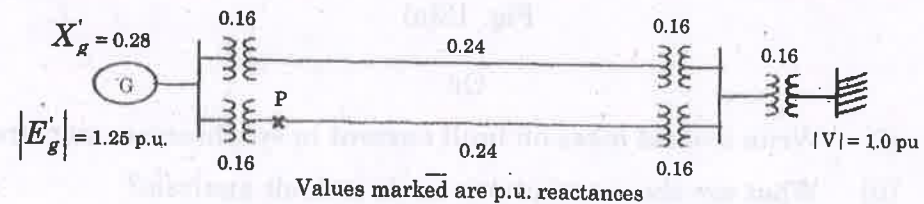


Fig. 16(b)

Reg. No. :

Question Paper Code : 52956

B.E./B.Tech. DEGREE EXAMINATIONS, APRIL/MAY, 2019.

Fifth Semester

Electrical and Electronics Engineering

EE 6501 — POWER SYSTEM ANALYSIS

(Regulation 2013)

(Common to PTEE 6501 — Power System Analysis for B.E. (Part-Time) for Fifth Semester — Electrical and Electronics Engineering — Regulation 2014)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. What is meant by base quantities in per unit representation?
2. What is impedance diagram and what are the approximations made in this diagram?
3. What are the information that are obtained from a load flow study?
4. What is swing bus?
5. Write the ways of adding an impedance to an existing system so as to modify bus-impedance matrix.
6. What is meant by fault level?
7. Name the faults which are having all three equal sequence current and which do not have zero sequence current.
8. Draw the zero sequence impedance equivalent circuit for $\Delta-\Delta$ type Three-Phase Transformers.
9. Define infinite bus in a power system.
10. Define critical clearing angle.

11. (a) The one line diagram of three phase power system is shown in Fig. 11(a). Select a common base of 100 MVA and 22 kV on generator side draw the impedance diagram in per – unit

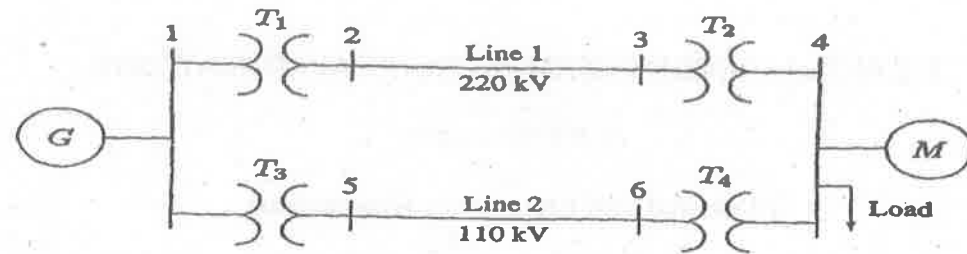


Fig. 11 (a)

G : 90 MVA , 22 KV , $X = 18\%$; T1 : 50 MVA , 22/220 KV , $X = 10\%$
 T2 : 40 MVA , 22/220 KV , $X = 6\%$; T3 : 40 MVA , 220/110 KV , $X = 6.4\%$
 T4 : 40 MVA , 110/11 KV , $X = 8\%$; M : 66.5 MVA , 10.45 KV , $X = 18.5\%$

The three phase load at bus 4 absorbs 57 MVA, 0.6 power factor lagging at 10.45 kV. Line 1 and line 2 have reactance of 48.4Ω and 65.43Ω respectively.

(13)

Or

- (b) From the impedance diagram shown in Fig.11(b). Compute the bus admittance matrix and draw the admittance diagram.

(13)

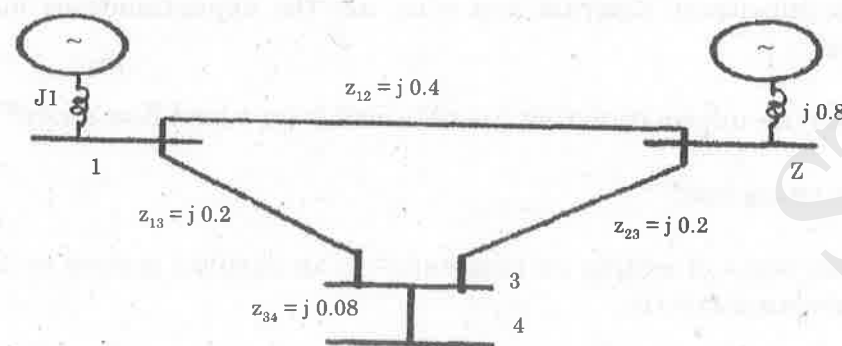


Fig.11(b)

12. (a) With neat flowchart, explain the computational procedure for load flow solution using Gauss-Seidal iterative method.

(13)

Or

- (b) Evaluate the Jacobian elements for the 3-Bus system shown in Fig. 12(b). All the impedances in this Fig. 12(b) are mentioned in per unit.

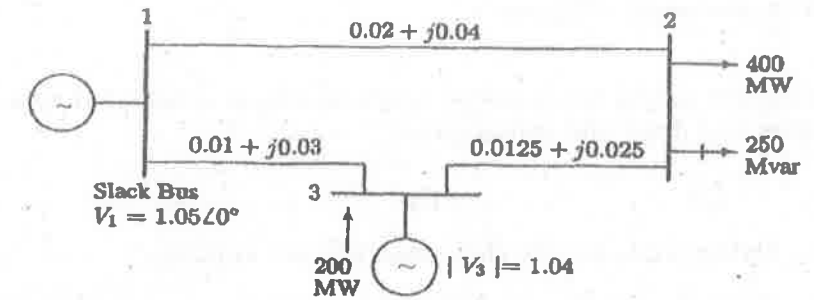


Fig. 12(b)

13. (a) A 25 MVA, 11 kV generator with $X_{d''} = 20\%$ is connected through a transformer, line and a transformer to a bus that supplies three identical motors as shown in Fig.13(a). Each motor has $X_{d''} = 20\%$ and $X_{d'} = 30\%$ on a base of 5 MVA, 6.6 kV. The three-phase rating of the step-up transformer is 25 MVA, 11/66 kV with a leakage reactance of 10% and that of the step-down transformer is 25 MVA, 66/6.6kV with a leakage reactance of 10%. The bus voltage at the motors is 6.6 kV when a three-phase fault occurs at the point F. For the specified fault, calculate (i) the sub transient current in the fault, (ii) the sub transient current in the breaker B. (iii) the momentary current in breaker B, and (iv) the current to be interrupted by breaker B in five cycles.

(13)

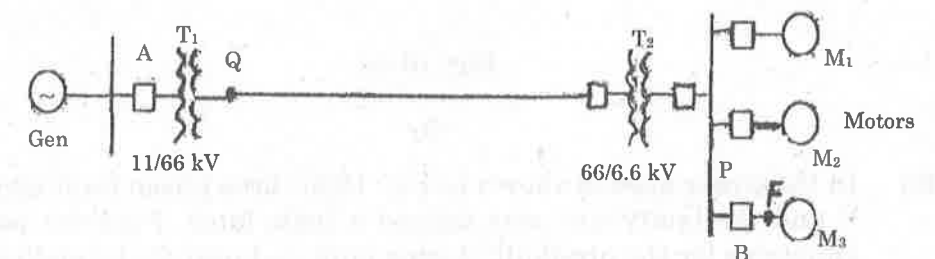


Fig. 13(a)

Or

- (b) (i) Write a short notes on fault current in synchronous machine. (8)
 (ii) What are the assumptions made in fault analysis? (5)
14. (a) Derive the expression for fault current in double line to ground fault on unloaded generator. Draw the equivalent network showing the interconnection of networks to simulate double line to ground fault. (13)

Or

14. (a) Derive the expression for fault current in line to line fault on unloaded generator. Draw an equivalent network showing the interconnection of networks to simulate line to line fault. (16)

Or

- (b) A 30 MVA, 11 kV generator has $z_1 = z_2 = j 0.05$. A Line to ground fault occurs at generator terminals. Find the fault current and line voltages during fault conditions. Assume that the generator neutral is solidly grounded and the generator is operating at no load and at rated voltage during occurrence of fault. (16)
15. (a) Derive Swing equation and discuss the importance of stability studies in power system planning and operation. (16)

Or

- (b) Find the critical clearing angle and time for clearing the fault with simultaneous opening of the breakers when a three phase fault occurs at point P close to bus 1 as shown in Fig. 15(b). The generator is delivering 1.0 pu. power at the instant preceding the fault.

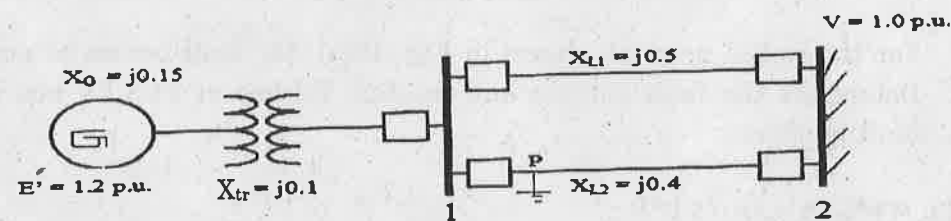


Fig. 15(b)

Reg. No. :

Question Paper Code : 80377

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2016.

Fifth Semester

Electrical and Electronics Engineering

EE 6501 — POWER SYSTEM ANALYSIS

(Regulations 2013)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. State the advantage of per unit analysis.
2. How are the loads represented in the reactance and Impedance diagram?
3. What is Jacobian matrix?
4. Write the need for Slack bus in load flow analysis.
5. What is the need for short circuit study?
6. How the shunt and series faults are classified?
7. Define short circuit capacity.
8. Why the neutral grounding impedance Z_n appears as $3Z_n$ in zero sequence equivalent circuit?
9. Define Voltage Stability.
10. State few techniques to improve the stability of the power system.

PART B — (5 × 16 = 80 marks)

11. (a) Prepare a per phase schematic of the system shown in Fig. 11(a) and show all the impedance in per unit on a 100 MVA, 132 kV base in the transmission line circuit. The necessary data are given as follows: (16)

G1 : 50MVA, 12.2kV, $X = 0.15\text{p.u}$

G2 : 20MVA, 13.8kV, $X = 0.15\text{ p.u}$

T1 : 80MVA, 12.2/161kV, $X = 0.1\text{ p.u}$

T2 : 40MVA, 13.8/161kV, $X = 0.1\text{ p.u}$

Load : 50MVA, 0.8 pf lag operating at 154 kV

Determine the p.u impedance of the load.

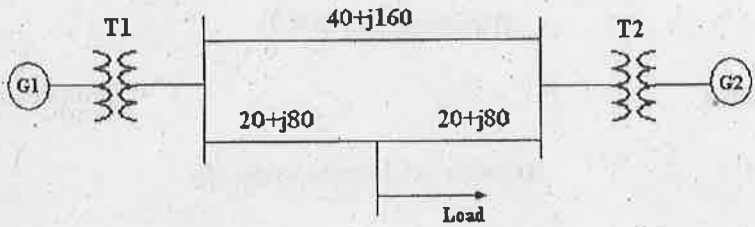


Fig. 11(a)

Or

- (b) The parameters of a 4-bus system are as under :

Line starting bus	Line ending bus	Line impedance	Line charging admittance
1	2	$0.2+j0.8$	$j0.02$
2	3	$0.3+j0.9$	$j0.03$
2	4	$0.25+j1.0$	$j0.04$
3	4	$0.2+j0.8$	$j0.02$
1	3	$0.1+j0.4$	$j0.01$

Draw the network and find bus admittance matrix. (16)

12. (a) With a neat flow chart, explain the computational procedure for load flow solution using Newton Raphson iterative method when the system contains all types of buses. (16)

Or

- (b) The Fig. 12(b) shows the one line diagram of a simple 3 bus power system with generators at buses 1 and 3. Line impedances are marked in p.u on a 100 MVA base. Determine the bus voltages at the end of second iteration using Gauss – Seidel method. (16)

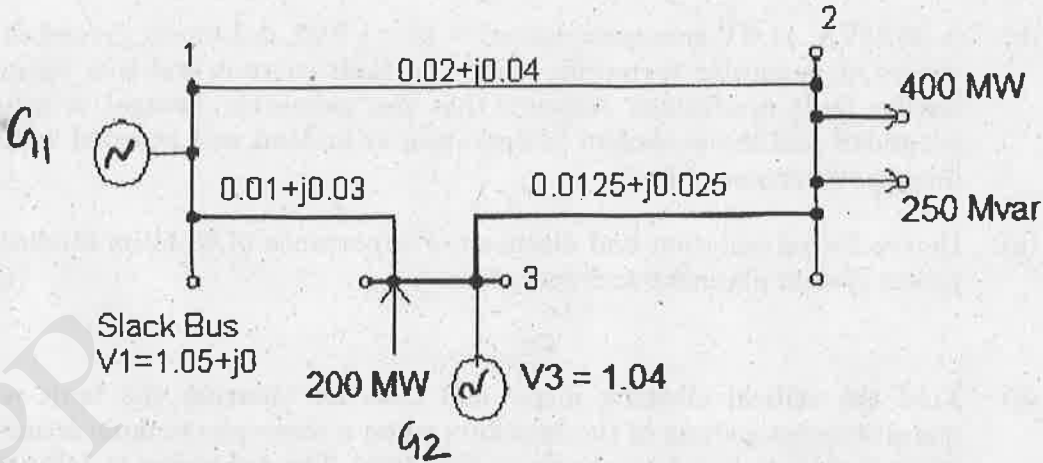


Fig. 12(b)

13. (a) For the radial network shown in Fig. 13(a) 3Φ fault occurs at point F. Determine the fault current and the line voltage at 11.8 kV bus under fault condition.

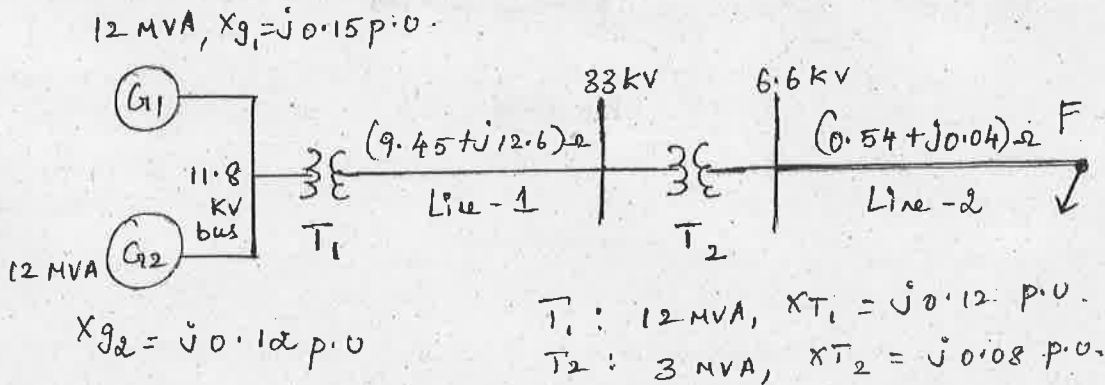


Fig. 13(a)

Or

- (b) A 3 phase, 5 MVA, 6.6 kV alternator with a reactance of 8% is connected to a feeder series impedance $(0.12 + j0.48)$ ohm/phase/km through a step up transformer. The transformer is rated at 3 MVA, 6.6 kV/33 kV and has a reactance of 5%. Determine the fault current supplied by the generator operating under no load with a voltage of 6.9 kV, when a 3 phase symmetrical fault occurs at a point 15 km along the feeder. (16)

Given: Rating of each machine 1200 kVA, 600 V with $X' = X_2 = 10\%$, $X_0 = 5\%$. Each three-phase transformer is rated 1200 kVA, 600/3300V (Delta/Star) with leakage reactance of 5%. The reactances of the transmission line are $X_1 = X_2 = 20\%$ and $X_0 = 40\%$ on a base of 1200 kVA, 3300 V. The reactances of the neutral grounding reactors are 5% on the kVA and voltage base of the machine. (13)

15. (a) Write the swing equation describing the rotor dynamics of a synchronous machine connected to infinite bus through a double circuit transmission line. (13)

Or

- (b) The per unit system reactances that are converted in a common base, are shown in this Figure. 6. Let us assume that the infinite bus voltage is $1\angle 0^\circ$. The generator is delivering 1.0 per unit real power at a lagging power factor of 0.9839 to the infinite bus. While the generator is operating in steady state, a three-phase bolted short circuit occurs in the transmission line connecting buses 2 and 4 — very near to bus 4. The fault is cleared by opening the circuit breakers at the two ends of this line, find the critical clearing time for various values of H . (13)

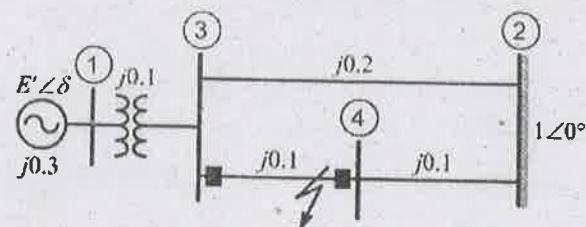


Figure. 6

PART C — (1 × 15 = 15 marks)

16. (a) Figure. 7 shows a part of a power system, where the rest of the system at two points of coupling have been represented by their Thevenin's equivalent circuit (or by a voltage source of 1 pu together its fault level which corresponds to the per unit value of the effective Thevenin's impedance). (15)

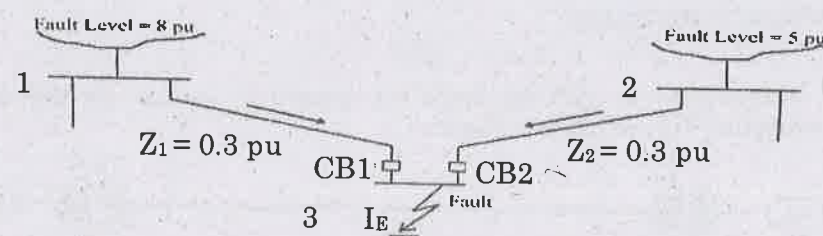


Figure. 7

With CB1 and CB2 open, short circuit capacities are
SCC at bus 1 = 8 pu. gives $Z_{g1} = 1/8 = 0.125$ pu
SCC at bus 2 = 5 pu. gives $Z_{g2} = 1/5 = 0.20$ pu
Each of the lines are given to have a per unit impedance of 0.3 pu.
 $Z_1 = Z_2 = 0.3$ p.u.

Determine the fault current at bus 3.

Or

- (b) Discuss in detail the importance of Power system stability study. Also discuss the solution of swing equation by Euler method and RK method.

Reg. No. :



Question Paper Code : 20458

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2018.

Fifth Semester

Electrical and Electronics Engineering

EE 6501 — POWER SYSTEM ANALYSIS

(Regulations 2013)

(Also Common to PTEE 6501 — Power System Analysis — For B.E. (Part – Time) — Fifth Semester — Electrical and Electronics Engineering – Regulations – 2014)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

- What is the need for base values?
- What are the approximations made in impedance diagram?
- What is the need for slack bus?
- When the generator bus is treated as load bus in NR load flow study? What will be the reactive power and bus voltage when the generator bus is treated as load bus?
- What is the need for short circuit studies or fault analysis?
- What is the significance of subtransient reactance and transient reactance in short circuit studies?
- Define negative sequence and zero sequence components.
- Define the operator 'a' and express the value of 'a' and 'a²' in both polar and rectangular form.
- What are coherent machines?
- How to improve the transient stability limit of the power system.

PART B — (5 × 13 = 65 marks)

11. (a) 300 MVA, 20 kV three-phase generator has a subtransient reactance of 20%. The generator supplies a number of synchronous motors over 64-km transmission line having transformers at both ends, as shown in Figure.1 All motors are rated as 13.2 kV and represented by just two equivalent motors. Rated inputs to the motors are 200 MVA and 100 MVA for M1 and M2, respectively. For both motors $X'' = 20\%$. The three phase transformer T1 is rated 350 MVA, 230/20 kV with leakage reactance of 10%. Transformer T2 is composed of three single-phase transformers each rated 127/13.2 kV, 100 MVA with leakage reactance of 10%. Series reactance of the transmission line is $0.5\Omega/\text{km}$. Draw the impedance diagram, with all impedances marked in per-unit. Select the generator rating as base in the generator circuit. (13)

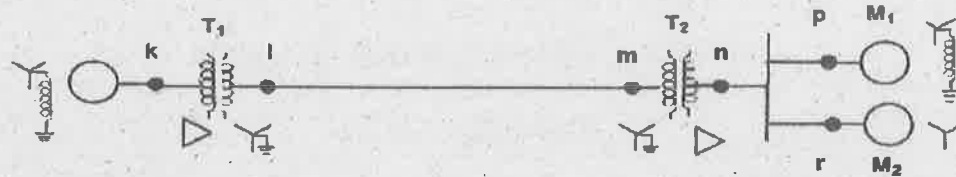


Figure. 1
Or

- (b) Draw the impedance diagram of the power system shown in below Figure. 2.

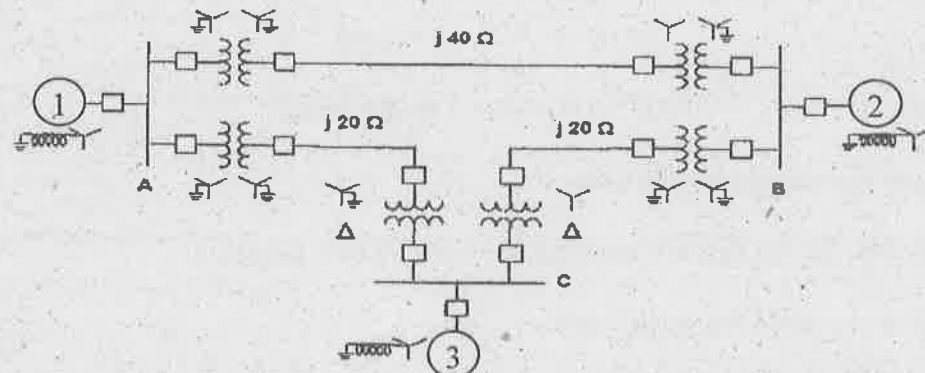


Figure. 2

Mark impedances in per unit. Neglect resistance and use a base of 50 MVA, 138 kV in the 40-Ω line. The ratings of the generator, motors and transformers are:

Generator 1: 20 MVA, 18 kV, $X'' = 20\%$

Generator 2: 20 MVA, 18 kV, $X'' = 20\%$

Synchronous motor 3: 30 MVA, 13.8 kV, $X'' = 20\%$

Three phase Y-Y transformers: 20 MVA, 138Y/20Y kV, $X = 10\%$

Three phase Y-Δ transformers: 15 MVA, 138Y/13.8 Δ kV, $X = 10\%$. (13)

12. (a) With a neat flow chart explain the computational procedure for load flow solution using Gauss-Seidel method when the system contains all types of busses.

Or

- (b) (i) Develop a power flow equation at any bus in a power system. (6)
(ii) Evaluate the Jacobian elements for NR load flow. (7)

13. (a) Construct Z Bus for the given network shown in Figure. 3 (13)

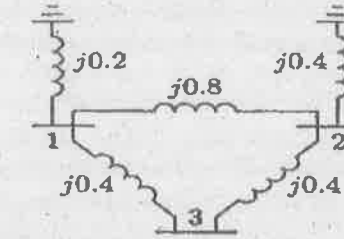


Figure. 3
Or

- (b) A 25 MVA, 11 kV generator with $X_d'' = 20\%$ is connected through a transformer, line and a transformer to a bus that supplies three identical motors as shown in Figure. 4. Each motor has $X_d'' = 25\%$ and $X_d' = 30\%$ on a base of 5 MVA, 6.6 kV. The three-phase rating of the step-up transformer is 25 MVA, 11/66 kV with a leakage reactance of 10% and that of the step-down transformer is 25 MVA, 66/6.6 kV with a leakage reactance of 10%. The bus voltage at the motors is 6.6 kV when a three-phase fault occurs at the point F.



Figure. 4

For the specified fault, calculate

- (i) the subtransient current in the fault,
(ii) the subtransient current in the breaker
(iii) the momentary current in breaker B, and
(iv) the current to be interrupted by breaker B in five cycle (13)

14. (a) Derive an expression for fault current as line-to-line fault on an unloaded generator. (13)

Or

- (b) A single line to ground fault (on phase a) occurs on the bus I of the system of Figure shown Figure. 5

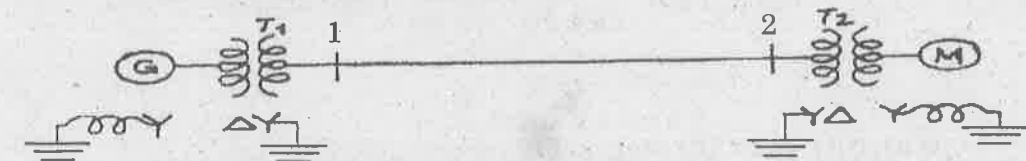


Figure. 5

Using bus impedance (Z_{BUS}) method Find

- (i) Current in the fault.
(ii) SC current on the transmission line in all the three phases.
(iii) SC current in phase 'a' of the generator.
(iv) Voltage of the healthy phases of the bus1. (13)

91491

-4-



Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 91491

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2019

Fifth Semester

Electrical and Electronics Engineering
EE 6501 – POWER SYSTEM ANALYSIS

(Regulations 2013)

(Also Common to PTEE 6501 – Power System Analysis – For B.E. (Part-Time) –
Fifth Semester – Electrical and Electronics Engineering – Regulations – 2014)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

1. What is the need for base values ?
2. What are the approximations made in impedance diagram ?
3. Compare Newton Raphson and Gauss Seidal methods of load flow solutions.
4. Write the quantities, that are associated with each bus in a system.
5. Define Short Circuit capacity.
6. The Z-bus method is very suitable for fault studies on large systems. Why ?
7. What are the symmetrical components of a three phase system ?
8. What is the sequence operator ?
9. Define Voltage Stability.
10. State few techniques to improve the stability of the power system.

15. a) Derive the expression for swing equation. (13)
(OR)
b) A synchronous motor is receiving 30% of the power that it is capable of receiving from an infinite bus. If the load on the motor is doubled, calculate the maximum value of δ during the swinging of the motor around its new equilibrium position. (13)

PART – C

(1×15=15 Marks)

16. a) Consider the three-bus system of fig. 16 (a). Assume negligible shunt admittances of the lines. Each line admittance is $-j10$ pu. 'a' is the complex turns ratio of the regulating transformer, RT, i.e.
 $a = |a| \angle \alpha$
a) Determine Y_{BUS} for $a = 1.05 \angle -2.5^\circ = 1.049 - j 0.046$.
b) Determine the changes in real and reactive power flows ΔP_{23} and ΔQ_{23} when 'a' changes from $1 \angle 0^\circ$ to $1 \angle -2.5^\circ$.
c) Repeat (b) when 'a' changes from $1 \angle 0^\circ$ to $1.05 \angle 0^\circ$. Given $|V_2| = 1.05$ pu, $|V_3| = 0.95$ pu, $\delta_2 = -3^\circ$, $\delta_3 = +2^\circ$, without the regulating transformer RT.

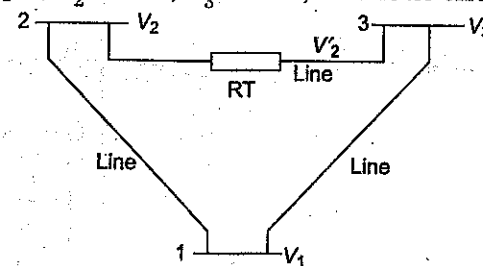


Fig. 16 (a)

(OR)

- b) A 25 MVA, 11 kV generator with $X_d'' = 20\%$ is connected through a transformer, line and a transformer to a bus that supplies three identical motors as shown in Fig. 16 (b). Each motor has $X_d'' = 25\%$ and $X_d' = 30\%$ on a base of 5 MVA, 6.6 kV. The three-phase rating of the step-up transformer is 25 MVA, 11/66 kV with a leakage reactance of 10 per cent and that of the step-down transformer is 25 MVA, 66/6.6 kV with a leakage reactance of 10 per cent. The bus voltage at the motors is 6.6 kV when a three-phase fault occurs at the point F. For the specified fault, calculate
a) the subtransient current in the fault
b) the subtransient current in the breaker B
c) the momentary current in breaker B
d) the current to be interrupted by breaker B in five cycles
Given : Reactance of the transmission line = 15% on a base of 25 MVA, 66 kV.
Assume that the system is operating on no load when the fault occurs.

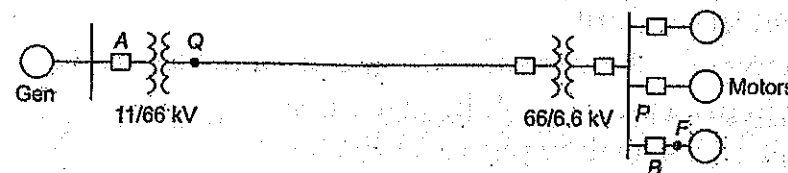


Fig. 16 (b)



PART - B

(5×13=65 Marks)

11. a) The data for the system whose single-line-diagram is shown in Fig. 11(a) is as follows :

G1 : 50 MVA, 11kV, $X'' = 1.6 \Omega$

G2 : 20 MVA, 6.6 kV, $X'' = 1.2 \Omega$

G3 : 25 MVA, 6.6 kV, $X'' = 0.56 \Omega$

T1 : 50 MVA, 33/11 kV, $X = 15.2 \Omega/\text{phase}$ on HT side

T2 : 50 MVA, 33/6.2 kV, $X = 16.0 \Omega/\text{phase}$ on HT side

Transmission Line : $X = 20.5 \Omega/\text{phase}$

Loads : A : 40 MW, 11 kV, 0.9 p.f lagging;

B : 40 MW, 6.6 kV, 0.85 p.f. lagging.

Choose the base power as 50 MVA, base kV as 33 kV. Draw the reactance diagram. Indicate pu reactances on the diagram. (13)


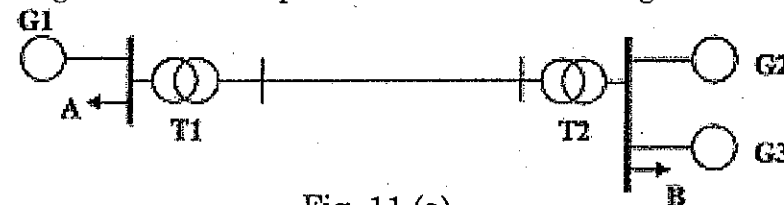


Fig. 11 (a)

(OR)

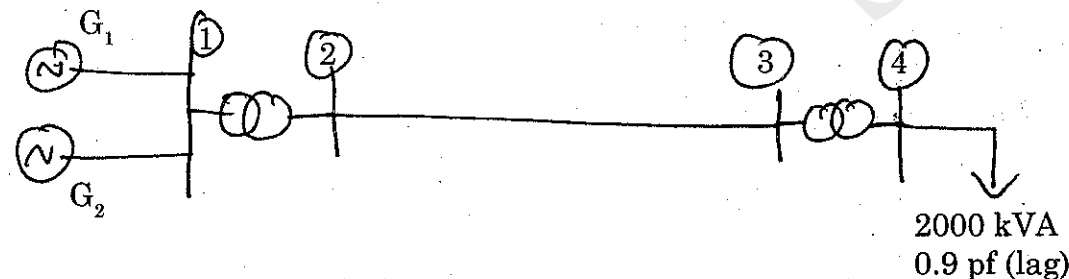- b) i) Starting from first principles show that a diagonal element of Y-bus equals the sum of admittances connected to that bus and an off diagonal element equals the negative of the sum of admittances directly connected between the buses. (6)
- ii) Prove that $[Y\text{-bus}] = [A]^T[y][A]$. (7)
12. a) With a neat flow chart, explain the computational procedure for load flow solution using Newton Raphson iterative method when the system contains all types of buses. (OR)
- b) Given: Rating of each machine 1200 kVA, 600 V with $X' = X_2 = 10\%$ $X_0 = 5\%$. Each three-phase transformer is rated 1200 kVA, 600/3300V (Delta/Star) with leakage reactance of 5%. The reactances of the transmission line are $X_1 = X_2 = 20\%$ and $X_0 = 40\%$ on a base of 1200,kVA, 3300 V. The reactances of the neutral grounding reactors are 5% on the kVA and voltage base of the machine. (13)



Perform power flow analysis employing Gauss Seidal method.

13. a) A 3 phase, 5 MVA, 6.6kV alternator with a reactance of 8% is connected to a feeder series impedance $(0.12 + j0.48) \text{ ohm/phase/km}$ through a step up transformer. The transformer is rated at 3 MVA, 6.6 kV/33 kV and has a reactance of 5%. Determine the fault current supplied by the generator operating under no load with a voltage of 6.9 kV, when a 3 phase symmetrical fault occurs at a point 15 km along the feeder. (13)

(OR)

- b) A 100 MVA, 11 kV generator with $X'' = 0.20 \text{ p.u}$ is connected through a transformer and line to a bus bar that supplies three identical motor as shown in Fig. and each motor has $X'' = 0.20 \text{ p.u}$ and $X' = 0.25 \text{ p.u}$ on a base of 20 MVA,33 kV, the bus voltage at the motors is 33 kV when three phase balanced fault occurs at the point F. Calculate (i) Sub transient current in the fault (ii) Sub transient current in the circuit breaker B (iii) Momentary current in the circuit breaker B (iv) The current to be interrupted by C.B B in 5 cycles.

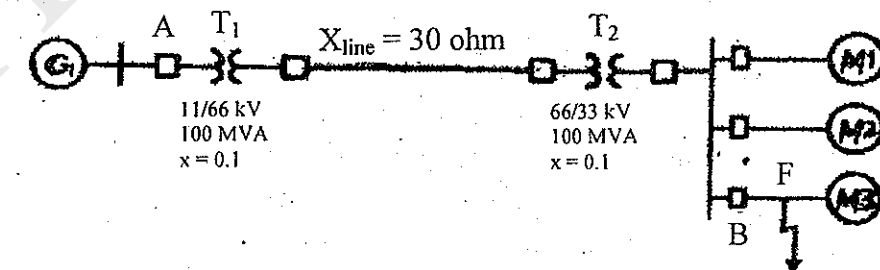


Fig. 13 (b)

14. a) Derive an expression for fault current as line-to-line fault on an unloaded generator. (13)
- (OR)
- b) A single line to ground fault (on phase a) occurs on the bus I of the system of Figure shown Figure. 5

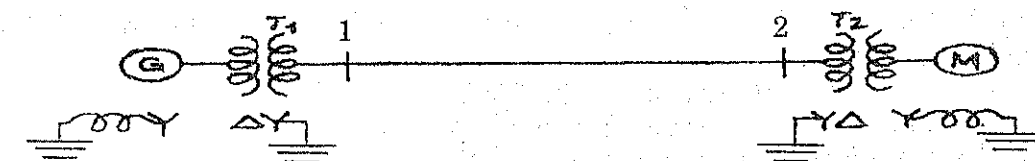


Fig. 5

Using bus impedance (Z_{BUS}) method. Find

- i) Current in the fault. (4)
- ii) SC current on the transmission line in all the three phases. (4)
- iii) SC current in phase 'a' of the generator. (2)
- iv) Voltage of the healthy phases of the bus I. (3)