

Definitions:-

Electrical Circuit:- It is a closed path of wires and electrical components which allows a current through it.

Circuit Diagram:- It is a graphical representation of an electric circuit, It shows the components and interconnections of the circuit using symbols.

Voltage (v) voltage is the difference in electric potential between two points, that pushes charged electrons (current) through a conducting loop.

Unit is volts (v)

Voltage is represented by the letter 'V' or 'E'

Current (I)

Current is the rate of flow of electric charge

Unit is amperes (A)

Current is represented by the letter 'I'.

Resistance:- (R)

Resistance is a measure of the opposition to the current flow in an electrical circuit.

It is represented by the letter 'R'

Unit of Resistance = Ω (ohms)

Resistor:-

Component that offer Resistance.

Conductance: (G)

Conductance is the reciprocal of resistance

$$G = \frac{1}{R}$$

Unit of Conductance is \mathcal{U} (mho)

Charge:-

Amount of energy or electrons that pass from one body to another.


Coulomb is the unit of electric charge.

Symbols

Resistance/Resistor:-



DC voltage Source:-

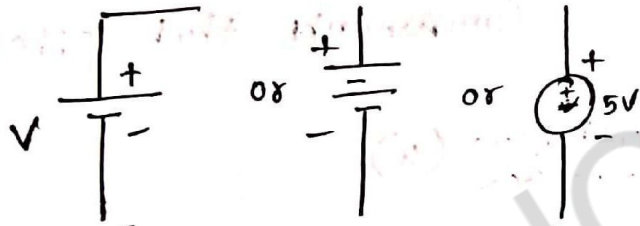

DC Current Source:-



Ammeter:-

- * Ammeter is used to measure current
- * It should be connected in series



Voltmeter:-

- * Voltmeter is used to measure voltage or potential difference between two points in a circuit.



Connection cable:-



Variable Resistor:-




value of the resistor is variable in such kind of resistors.

STUCOR APP

Downloaded from STUCOR APP

Basic Components of Electric Circuits:-

- * Branch,
- * Nodes.
- * Loops.

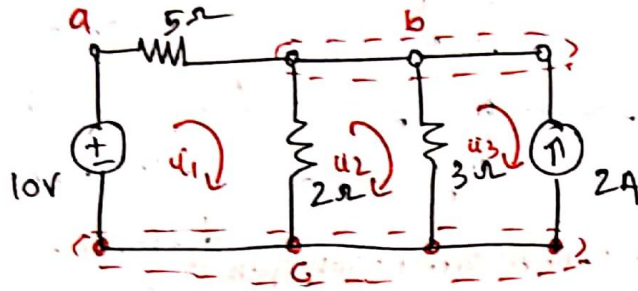

Branches:-

A branch represent a single element such as a voltage source or a resistor.

In the above circuit, 10V - voltage source, 2A - current source, 5Ω, 2Ω, & 3Ω resistors are the branches.

Node:

A Node is a point of connection between two or more branches.

Point a, b, c are nodes of the circuit.

If a short circuit (a connecting wires) connects two nodes, the two node constitutes a single node. (Even though 3 points are there near point 3 they are considered as single node)


Loop

A loop is a closed path formed by starting at a node, passing through the a set of nodes and returning to the starting node.

abca → forms first loop.

bcb → forms second loop / third loop.

eg.

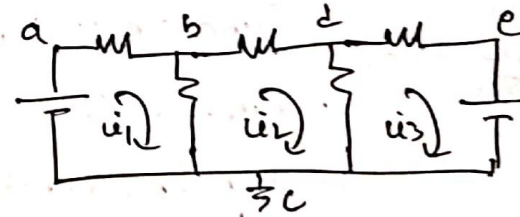

abca → 1st loop

bdcb → 2nd loop

dec d → 3rd loop

i_1, i_2, i_3 are called as loop currents.

Series & Parallel Circuits:-

Series




Resistor R_1 & R_2 are said to be in series because the same current 'I' flows in both the resistors.


$$R_{eq} = R_1 + R_2$$

Total Resistance or equivalent Resistance is the sum of the two resistors or 'n' resistors.
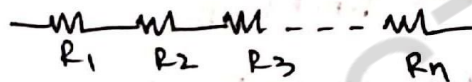
$$R_{eq} = R_1 + R_2 + \dots + R_n \text{ for 'n' resistors connected in series.}$$




eg.

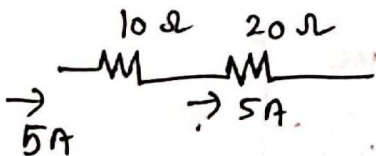

Same 5A is flowing in both 10 ohm & 20 ohm so they are connected in series.

$$R_{eq} = 10 + 20 = 30 \Omega$$

Parallel Circuit / Shunt Circuit:

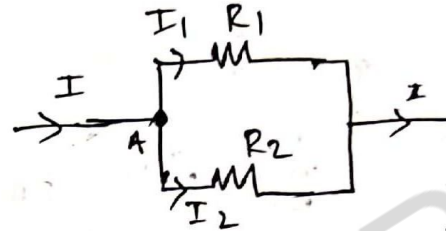


(at point A current gets split)

Resistors R_1 & R_2 are said to be connected in parallel, because different currents (I_1 in R_1 & I_2 in R_2) are flowing.

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$


or

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

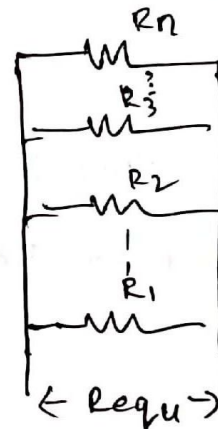

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

eg:-

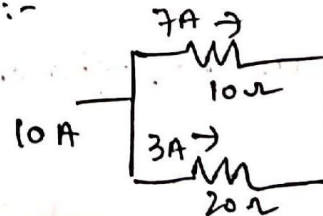

In this circuit total current enters is 10A, it is split & 7A enters 10 ohm & 3A enters 20 ohm, so, 10 ohm & 20 ohm are in parallel.

Ohm's law:-

Ohm's law states that at constant temperature the voltage across a conductor is directly proportional to the current flowing through it.

$$V \propto I$$

$$V = IR$$

V \Rightarrow voltage

$$V = IR \text{ in volts}$$

I \Rightarrow current

$$I = V/R \text{ in amp}$$

R \Rightarrow Resistance.

$$R = V/I \text{ in ohms.}$$

Problem:-


- ① An electric iron draws 2A at 10V, find its resistance

From Ohm's law

$$R = \frac{V}{I} = \frac{10}{2} = 5\Omega$$

$$R = 5\Omega$$

②

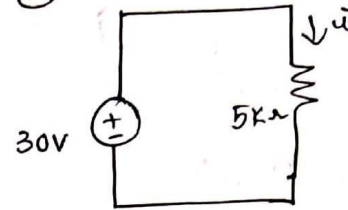

In the circuit shown, calculate the current 'i', conductance 'G' and Power 'P'.

Solution:-

Current:- $i = V/R$

$$= \frac{30}{5 \times 10^3} \rightarrow (5k = 5 \times 10^3 \Omega \text{ or } 5000 \Omega)$$

$$i = 6\text{mA} \quad (6 \text{ milliamps})$$

Conductance G

$$G = \frac{1}{R} = \frac{1}{5 \times 10^3} = 0.2 \text{ mS or } 0.2 \text{ mS}$$

(where S is Siemens)

$$G = 0.2 \text{ mS}$$

(m \rightarrow represent milli 10^{-3})

Power (P)

$$\text{Power } P = V \times I = 30 \times (6 \times 10^{-3})$$


$$P = 180 \text{ mW}$$

Kirchoff's Law:-

- * Kirchoff's Current Law (KCL)
- * Kirchoff's Voltage Law (KVL)

Kirchoff's Current Law (KCL)

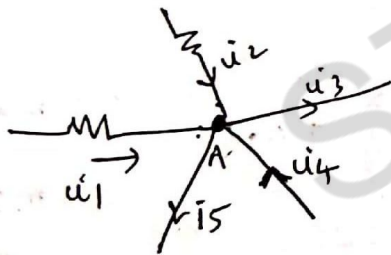Kirchoff's current law states that the sum of the currents entering a node is equal to the sum of the current leaving the node. (or) in other words algebraic sum of the currents at node is zero.



In the figure above 'A' is the node, currents entering the node are i_1, i_2, i_4 (see the arrow mark for direction) currents leaving the node are i_3 & i_5


So according to KCL

$$i_1 + i_2 + i_4 = i_3 + i_5$$

or

$$i_1 + i_2 + i_4 - i_3 - i_5 = 0.$$

Problem:-

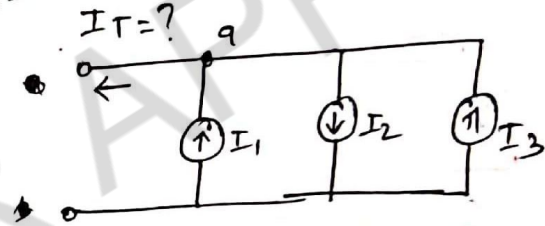

find I_T

Solution

At node 'a' I_1 & I_3 are entering. I_2 & I_T are leaving

So according to KCL $I_T + I_2 = I_1 + I_3$


$$I_T = I_1 + I_3 - I_2$$

Kirchoff's Voltage Law: (KVL)

Kirchoff's voltage law states that the algebraic sum of all voltages around a closed path or loop is zero.

or in other words. In a close circuit.

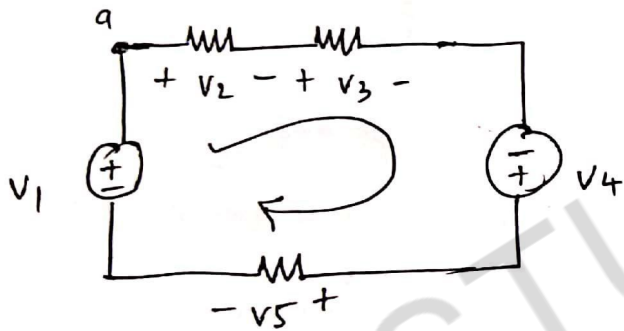Sum of the potential raise = Sum of the potential drops.



lets starts from point 'a' & traverse the loop.

$$+v_2 + v_3 - v_4 + v_5 - v_1 = 0$$

$v_1 + v_4 = v_2 + v_3 + v_5$

v_1 & v_4 = Potential raise, v_2, v_3 & v_5 - Potential drops.


Concept to remember:-

If current I_i flows in to a resistor ' R_i ' then a voltage drop v_i occurs at the resistor R_i with the polarity shown.



Polarity of the voltage depends on the direction of the current entry, ~~increased~~

Problems:-

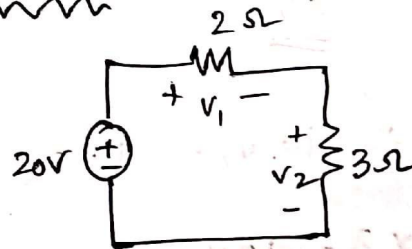

find the voltages v_1 & v_2 for the circuit shown.

Solution:-

To find v_1 & v_2 , we need to find the current flowing through the resistors.

* to find the total current we need to find the equivalent resistances of this circuit.

* Resistance 2Ω & 3Ω are connected in series (since the same current flows)

$$R_{eq} = 5\Omega \quad (2+3)$$

$$\text{Total current } i = \frac{V}{R} = \frac{20}{5} = \underline{\underline{4A}}$$

voltage drop across 2Ω i.e. $V_1 = I \times R_1$

$$4 \times 2 = \underline{\underline{8V}}$$

$$V_1 = 8V$$

voltage drop across 3Ω i.e. $V_2 = I \times R_2$

$$4 \times 3 = \underline{\underline{12V}}$$

$$V_2 = 12V$$


Verification

According to KVL voltage rise = voltage drops

$$20V = 8V + 12V$$

voltage rise \leftarrow \leftarrow voltage drops

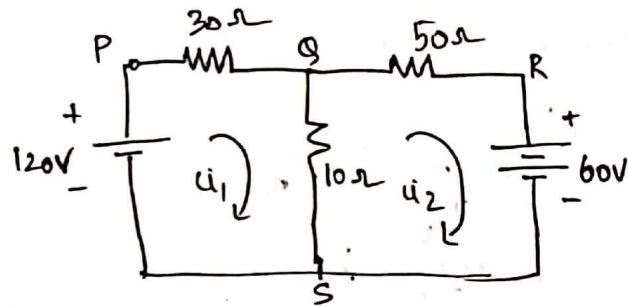1. Solve the mesh and branch currents for the circuit shown.



Solution:-

Apply KVL at loop 1 (P Q S P)

$$30u_1 + 10(u_1 - u_2) = 120$$

$$40u_1 - 10u_2 = 120 \quad \text{--- (1)}$$

Apply KVL at loop 2 (Q R S Q)

$$50u_2 + 10(u_2 - u_1) = -60$$

$$-10u_1 + 60u_2 = -60 \quad \text{--- (2)}$$

By using Cramer's rule find Δ

$$\Delta = \begin{vmatrix} 40 & -10 \\ -10 & 60 \end{vmatrix} = (60 \times 40) - (-10 \times -10)$$

$$\Delta = 2300$$

$$\Delta_1 = \begin{vmatrix} 120 & -10 \\ -60 & 60 \end{vmatrix} = (120 \times 60) - (-10 \times -60)$$

$$= 7200 - 600$$

$$\Delta_1 = 6600$$

$$\Delta_2 = \begin{vmatrix} 40 & 120 \\ -10 & -60 \end{vmatrix} = (40 \times -60) - (-10 \times 120)$$


$$= -2400 + 1200$$

$$\Delta_2 = -1200$$

$$u_1 = \frac{\Delta_1}{\Delta} = \frac{6600}{2300} = \underline{\underline{2.86 \text{ A}}}$$

$$u_2 = \frac{\Delta_2}{\Delta} = \frac{-1200}{2300} = \underline{\underline{-0.521 \text{ A}}}$$

u_1 & u_2 are loop currents.

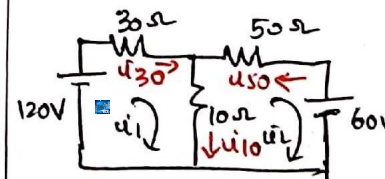

i_{30} , i_{50} & i_{10} are called branch currents.
(Simply the current at the branches).

$$i_{30} = i_1 = 2.86 \text{ A}$$

$$i_{50} = i_1 - i_2 = 0.52 \text{ A}$$

$$i_{10} = i_{30} + i_{50} = 3.38 \text{ A}$$


Note:-

i_{50} is opposite to i_2 so $i_{50} = -i_2$.

Current i_{30} & i_{50} combined & flow in
 1Ω resistor so $i_{10} = i_{30} + i_{50}$.

i_1 & i_{30} are same so $i_1 = i_{30}$.
(Refer the circuit).

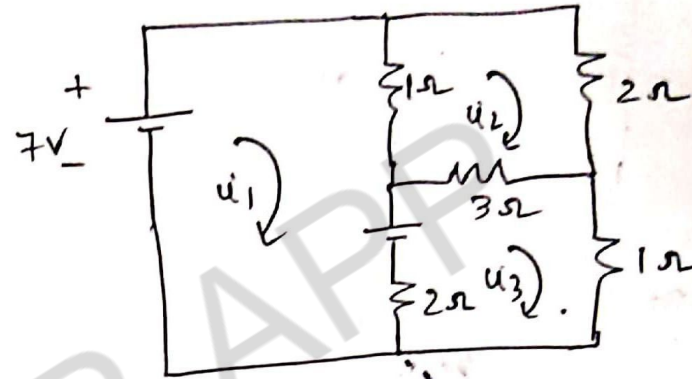2) Use the mesh analysis to determine the three mesh currents in the circuit shown.



Three loops are there in this circuit. loop 1, 2, 3.

apply KVL in loop 1:-

$$1(i_1 - i_2) + 2(i_1 - i_3) = 7 - 6$$

$$3i_1 - i_2 - 2i_3 = 1 \quad \text{--- (1)}$$

Loop 2

$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

$$-i_1 + 6i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Loop 3

$$3(i_3 - i_2) + 1i_3 + 2(i_3 - i_1) = 6$$

$$-2i_1 - 3i_2 + 6i_3 = 6 \quad \text{--- (3)}$$

Matrix representation:-

$$\begin{bmatrix} 3 & -1 & 2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix}$$

$$A = \begin{vmatrix} 3 & -1 & 2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{vmatrix}$$

$$= 3(36-9) + 1(-6-6) - 2(3+12)$$

$$= 81 - 12 - 30$$

$$\Delta = 39$$

$$\Delta_1 = \begin{vmatrix} 1 & -1 & -2 \\ 0 & 6 & -3 \\ 6 & -3 & 6 \end{vmatrix}$$

$$\Delta_2 = \begin{vmatrix} 3 & 1 & -2 \\ -1 & 0 & -3 \\ -2 & 6 & 6 \end{vmatrix}$$

$$\Delta_3 = \begin{vmatrix} 3 & -1 & 1 \\ -1 & 6 & 0 \\ -2 & -3 & 6 \end{vmatrix}$$

$$\Delta_1 = 117$$

$$\Delta_2 = 78$$

$$\Delta_3 = 117$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{117}{39} = 3A$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{78}{39} = 2A$$


$$i_3 = \frac{\Delta_3}{\Delta} = \frac{117}{39} = 3A$$

$$i_1 = 3A$$

$$i_2 = 2A$$

$$i_3 = 3A$$

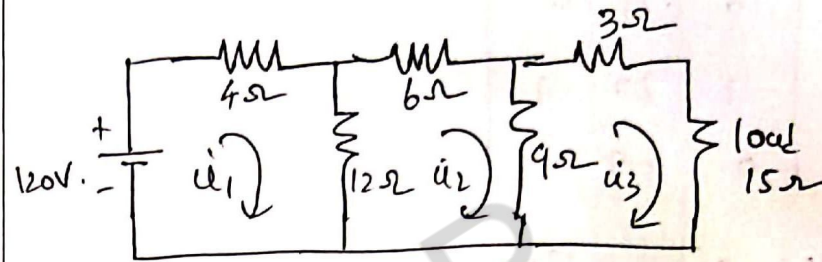3. In the circuit given in figure, obtain the load current and power delivered to the load.



Solution:-
Apply KVL at
Loop 1

$$4i_1 + 12(i_1 - i_2) = 120$$

$$16i_1 - 12i_2 = 120 \quad \text{--- (1)}$$

Loop 2

$$12(i_2 - i_1) + 6i_2 + 9(i_2 - i_3) = 0$$

$$-12i_1 + 27i_2 - 9i_3 = 0 \quad \text{--- (2)}$$

Loop 3

$$9(i_3 - i_2) + 3i_3 + 15i_3 = 0$$

$$-9i_2 + 27i_3 = 0 \quad \text{--- (3)}$$

Matrix representation:-

$$\begin{bmatrix} 16 & -12 & 0 \\ -12 & 27 & -9 \\ 0 & -9 & 27 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 16 & -12 & 0 \\ -12 & 27 & -9 \\ 0 & -9 & 27 \end{vmatrix}$$

$$= 16[729 - 81] + 12[-324 - 0] + 0$$

$$\Delta = 6480$$

$$\Delta_3 = \begin{vmatrix} 16 & -12 & 120 \\ -12 & 27 & 0 \\ 0 & -9 & 0 \end{vmatrix}$$

$$\Delta_3 = 12960$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{12960}{6480} = 2A$$

$$i_3 = 2A$$


Current through load resistor 15Ω is $2A$.

So power delivered to the load is $P = i^2 R$

$$P_{15} = 60W$$

$$= 2^2 \times 15 = 60W$$

Mesh Equation by Inspection Method:-

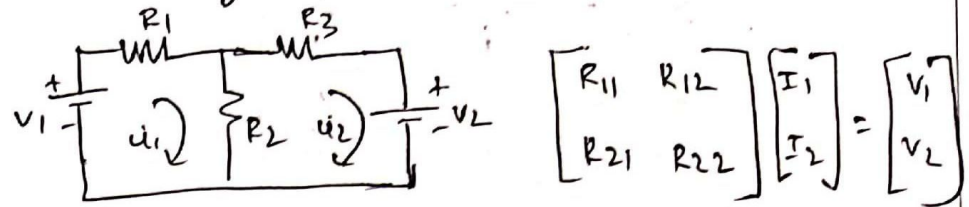


$R_{11} = R_1 + R_2$ (Sum of all resistance in the 1st loop)

$R_{21} = R_{12} = -R_2$ (Total resistance shared by loop

one and two, Negative sign indicates the current i_1 & i_2 are in opposite direction)

$R_{22} = R_2 + R_3$ (Sum of all the resistances in the 2nd loop)
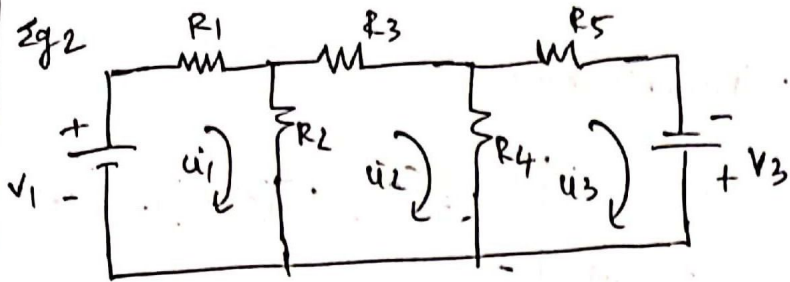
$$\begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$




$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} R_1+R_2 & -R_2 & 0 \\ -R_2 & R_2+R_3+R_4 & -R_4 \\ 0 & -R_4 & R_4+R_5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ 0 \\ V_3 \end{bmatrix}$$

Problem:

1. Find the current through 8Ω resistor

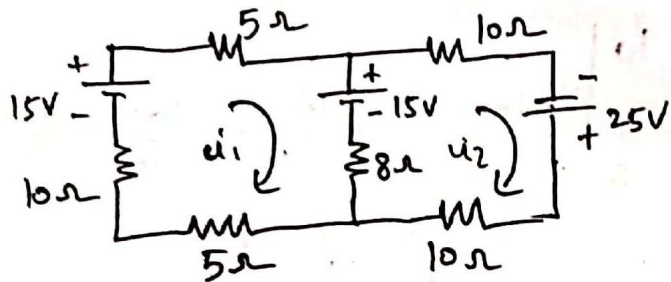

Solution by using mesh inspection method.

$$\begin{bmatrix} R_{11} & -R_{12} \\ -R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 5+8+5+10 & -8 \\ -8 & 10+10+8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 15 & -15 \\ 15 & 25 \end{bmatrix}$$

$$\begin{bmatrix} 28 & -8 \\ -8 & 28 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 40 \end{bmatrix}$$

Apply cramer's rule.

$$\Delta = \begin{vmatrix} 28 & -8 \\ -8 & 28 \end{vmatrix} = 784 - 64 = 720$$

$$\Delta_1 = \begin{vmatrix} 0 & -8 \\ 40 & 28 \end{vmatrix} = 320 \quad I_1 = \frac{\Delta_1}{\Delta} = \frac{320}{720} = 0.44A$$

$$\Delta_2 = \begin{vmatrix} 28 & 0 \\ -8 & 40 \end{vmatrix} = 1120 \quad I_2 = \frac{\Delta_2}{\Delta} = \frac{1120}{720} = 1.55A$$


Current through 8Ω resistor $i_2 - i_1 = 1.55 - 0.44$

$I_1 = 0.44A$

$i_8 = 1.11A$

$I_2 = 1.55A$

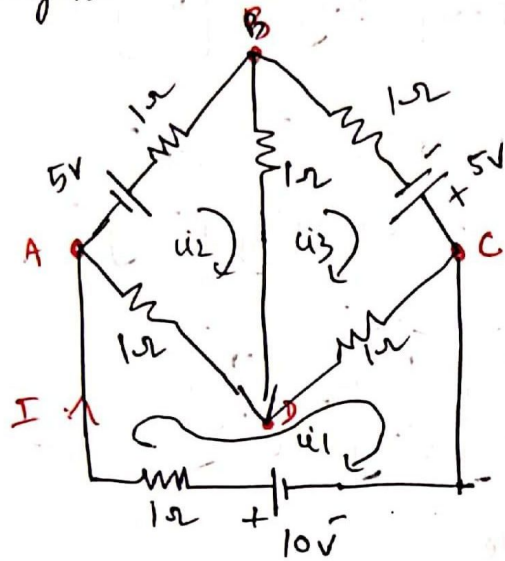2. Determine the currents in bridge circuit by using mesh analysis.



Solution:- By using inspection method.

$$\begin{bmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} 1+1+1 & -1 & -1 \\ -1 & 1+1+1 & -1 \\ -1 & -1 & 1+1+1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 5 \\ 5 \end{bmatrix}$$

By applying Cramer's rule.

$$\Delta = \begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix} = 3[9-1] + 1[-3-1] - 1[1+3] = 24 - 4 - 4 = 16$$

$$\Delta_1 = \begin{vmatrix} 10 & -1 & -1 \\ 5 & 3 & -1 \\ 5 & -1 & 3 \end{vmatrix} = 120 \quad i_1 = \frac{\Delta_1}{\Delta} = \frac{120}{16} = 7.5A$$

$$\Delta_2 = \begin{vmatrix} 3 & 10 & -1 \\ -1 & 5 & -1 \\ -1 & 5 & 3 \end{vmatrix} = 100 \quad i_2 = \frac{\Delta_2}{\Delta} = \frac{100}{16} = 6.25A$$

$$\Delta_3 = \begin{vmatrix} 3 & -1 & 10 \\ -1 & 3 & 5 \\ -1 & -1 & 5 \end{vmatrix} = 100 \quad i_3 = \frac{\Delta_3}{\Delta} = \frac{100}{16} = 6.25A$$

Current through AD is $i_1 - i_2 = 7.5 - 6.25 = 1.25A$

Current through AB is $i_2 = 6.25A$


Current through BD is $i_2 - i_3 = 6.25 - 6.25 = 0A$

Current through BC is $i_3 = 6.25A$

Current through CD is $i_1 - i_3 = 7.5 - 6.25 = 1.25A$.

Nodal Method:

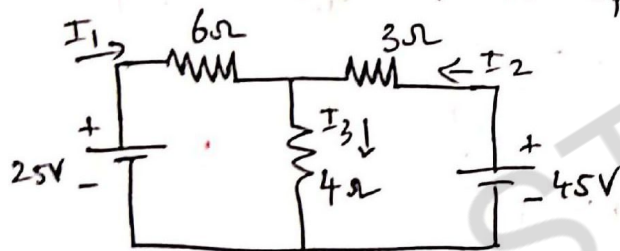
1. Using Nodal Analysis, obtain the currents flowing in all the resistors of the circuit.



Solution:- Convert all the voltage sources into equivalent sources.

$$I_1 = \frac{25}{6} = 4.166A$$

$$I_2 = \frac{45}{3} = 15A$$

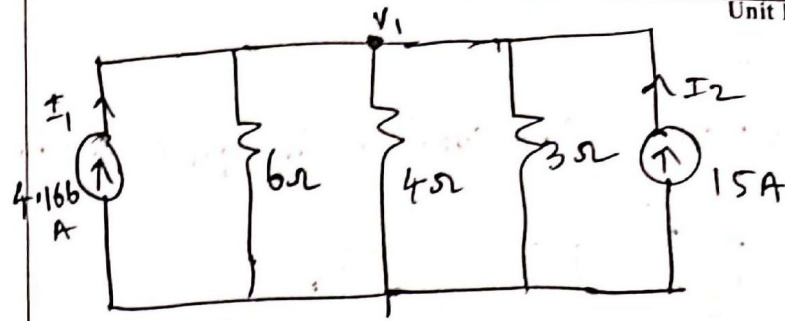

Apply KCL at node V_1

$$4.166 + 15 = \frac{V_1}{6} + \frac{V_1}{4} + \frac{V_1}{3}$$

$$19.166 = V_1 \left[\frac{1}{6} + \frac{1}{4} + \frac{1}{3} \right]$$

$$19.166 = V_1 [0.75]$$

$$V_1 = \frac{19.166}{0.75} = 25.55V$$


$$V_1 = 25.55V$$

Current through 6Ω resistor = $\frac{V_1}{6} = \frac{25.55}{6} = 4.25A$

Current through 4Ω resistor = $\frac{V_1}{4} = \frac{25.55}{4} = 6.38A$

Current through 3Ω resistor = $\frac{V_1}{3} = \frac{25.55}{3} = 8.51A$

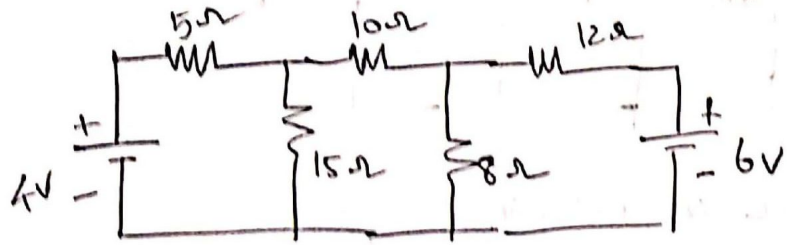2. Using Nodal Method find Current through 8Ω resistor




Convert all the voltage sources in to equivalent current sources.

$$I_1 = 4/5 = 0.8A$$

$$I_2 = 6/12 = 0.5A$$

Circuit becomes

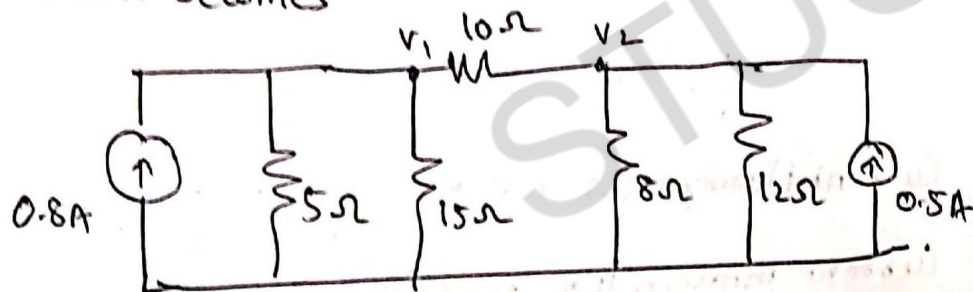

matrix form by inspection method.

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{15} + \frac{1}{10} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{1}{10} + \frac{1}{8} + \frac{1}{12} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0.8 \\ 0.5 \end{bmatrix}$$

$$\begin{bmatrix} 0.366 & -0.1 \\ -0.1 & 0.308 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0.8 \\ 0.5 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 0.366 & -0.1 \\ -0.1 & 0.308 \end{vmatrix} = 0.112 - 0.01$$

$$\Delta = 0.102$$

$$\Delta v_1 = \begin{vmatrix} 0.8 & -0.1 \\ 0.5 & 0.308 \end{vmatrix} = 0.2964$$

$$\Delta v_2 = \begin{vmatrix} 0.366 & 0.8 \\ -0.1 & 0.5 \end{vmatrix} = 0.263$$

$$v_1 = \frac{\Delta v_1}{\Delta} = \frac{0.2964}{0.102} = 2.905V$$


$$v_1 = 2.905V$$

$$V_2 = \frac{\Delta v_2}{\Delta} = \frac{0.263}{0.102} = 2.578V$$

$$V_L = 2.578V$$

Current through 8Ω resistor = $\frac{V_2}{8} = \frac{2.578}{8} = 0.322A$

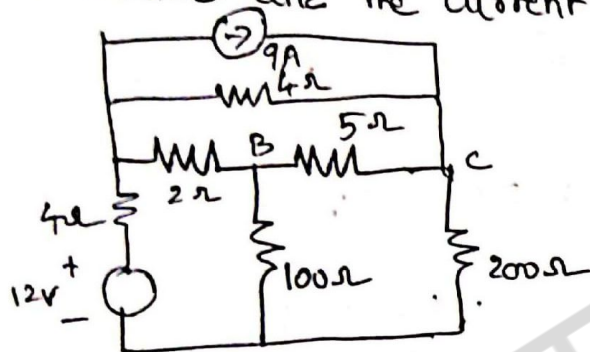
3. Use Nodal Analysis to determine the voltage across 5Ω resistance and the current in the $12V$ sources.



Solution:- Convert voltage source into current source.

$$I = V/R = 12/4 = 3A$$

Circuit becomes.

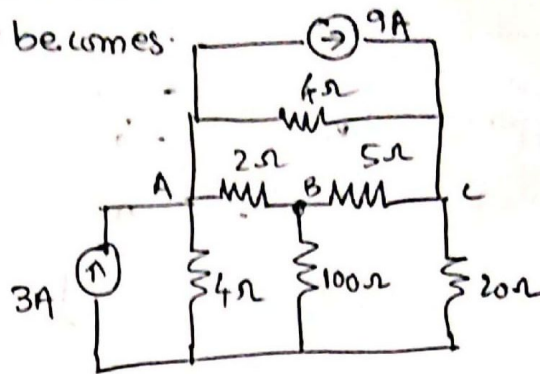

At node A, the current is $3 - 9 = -6A$

At node B, the current is zero.

At node C, the current is $9A$

Node Equation in matrix form

$$\begin{bmatrix} \frac{1}{4} + \frac{1}{2} + \frac{1}{4} & -\frac{1}{2} & -\frac{1}{4} \\ -\frac{1}{2} & \frac{1}{2} + \frac{1}{100} + \frac{1}{5} & -\frac{1}{5} \\ -\frac{1}{4} & -\frac{1}{5} & \frac{1}{5} + \frac{1}{20} + \frac{1}{4} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 9 \end{bmatrix}$$

STUCOR APP

Downloaded from STUCOR APP

$$\begin{bmatrix} 1 & -0.5 & -0.25 \\ -0.5 & -0.71 & -0.2 \\ -0.25 & -0.2 & 0.5 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 9 \end{bmatrix}$$

Solve V_B & V_C

$$\Delta = \begin{vmatrix} 1 & -0.5 & -0.25 \\ -0.5 & 0.71 & -0.2 \\ -0.25 & -0.2 & 0.5 \end{vmatrix}$$

$$= \boxed{\Delta = 0.0956} \quad \begin{aligned} & 1(0.355 - 0.04) + 0.5(-0.254 - 0.05) \\ & -0.25(0.1 + 0.1775) \end{aligned}$$

$$\Delta V_B = \begin{vmatrix} 1 & -6 & -0.25 \\ -0.5 & 0 & -0.2 \\ -0.25 & 9 & 0.5 \end{vmatrix}$$

$$= 1.125$$

$$\Delta V_B = 1.125 \quad V_B = \frac{\Delta V_B}{\Delta} = \frac{1.125}{0.0956} = \underline{\underline{11.76V}}$$

$$\boxed{V_B = 11.76V}$$

$$\Delta V_C = \begin{vmatrix} 1 & -0.5 & -6 \\ -0.5 & 0.71 & 0 \\ -0.25 & -0.2 & 9 \end{vmatrix}$$

$$= 2.475$$


$$\Delta V_C = 2.475$$

$$V_C = \frac{\Delta V_C}{\Delta} = \frac{2.475}{0.0956} = \boxed{V_C = 25.88V}$$

Voltage across 5Ω is $V_B - V_C$

$$= 11.76 - 25.88$$

$$\boxed{V_{5\Omega} = \underline{\underline{-14.12V}}}$$

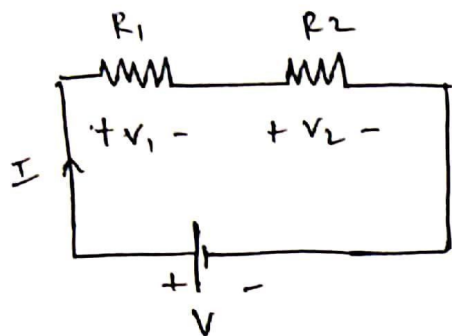
Voltage Division rule:-

If two resistors are connected in series and if the total voltage applied is \$V\$, then the voltage across any one resistance can be found by using the formula

$$= \frac{\text{total voltage} \times \text{same Resistance in which voltage need to be found}}{\text{Sum of the Resistance.}}$$

$$V_1 = \frac{V \times R_1}{R_1 + R_2}$$

$$V_2 = \frac{V \times R_2}{R_1 + R_2}$$

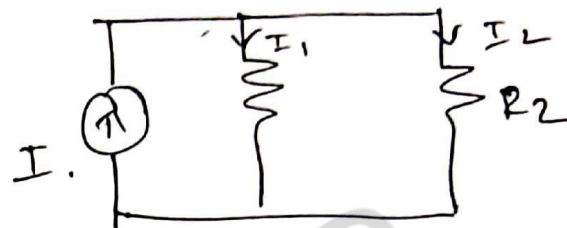Current Division Rule:-

If two resistors are connected in parallel and the total current entering the parallel combination is known. then the current flowing through the resistors can be calculated using


$$\frac{\text{total current} \times \text{opposite Resistance}}{\text{Sum of the Resistance.}}$$

$$I_1 = \frac{I R_2}{R_1 + R_2}$$

$$I_2 = \frac{I R_1}{R_1 + R_2}$$


Super Position Theorem:-

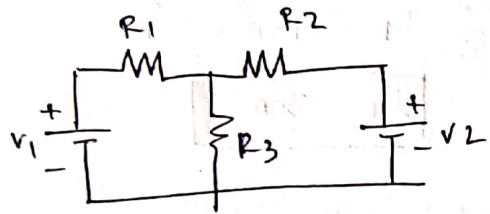Super position Theorem states that the response in a circuit with multiple sources is given by the algebraic sum of responses due to individual sources acting alone.




Procedure/Steps:

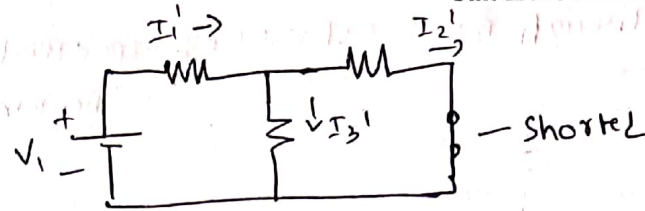
- ① In a circuit with multiple sources keep only one source active (V_1 - active, V_2 - short)
- ② Remove all the other sources (voltage sources must be short circuited, current sources must be open circuited)
- ③ Find the response of the circuit for the individual sources and label the term as I_1' , I_2' & I_3' etc.



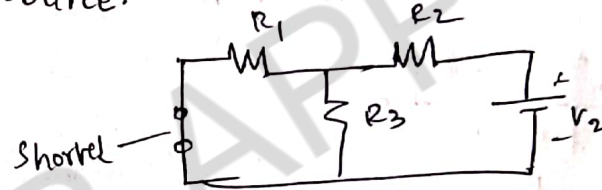- ④ Now keep the other source active and remove the first source.



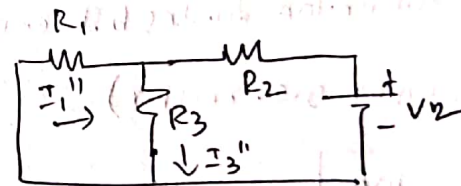- ⑤ Now take find the response due to the source V_2 and label the current as I_1'' , I_2'' & I_3'' ...



(Follow the same procedure if more than two sources present)

- ⑥ Now find the overall response of the circuit by sum up the individual responses:


$$I_1 = I_1' + I_1''$$

$$I_2 = I_2' + I_2''$$


$$I_3 = I_3' + I_3''$$

[Note: Depending upon the direction assumed sign may vary, once current is calculated other parameters like voltage, Power etc can be calculated]

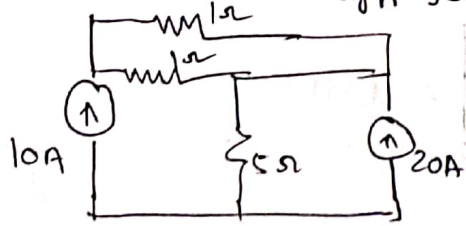① Find the current through 5Ω resistor using Super position Theorem.



Step 1: Keep 10A Active & Remove 20A

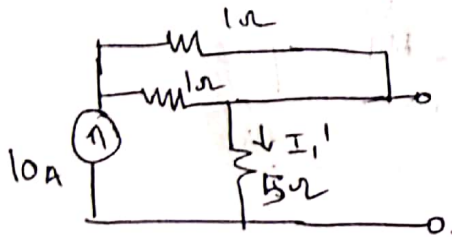


From the fig above current through 5Ω is 10A

(Even though the current 10A divides between two 1Ω it agains join & enter 5Ω resistor)

$$I_{L1} = 10A$$

Step 2 Keep 20A Active & Remove 10A

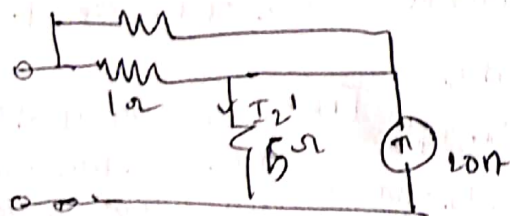

By inspecting the circuit itself we can observe, the current through 5Ω is 20A.


$$I_{L2} = 20A$$

So total current through 5Ω resistor $I = I_{L1} + I_{L2}$


$$I_L = 10A + 20A$$

$$I_L = 30A$$

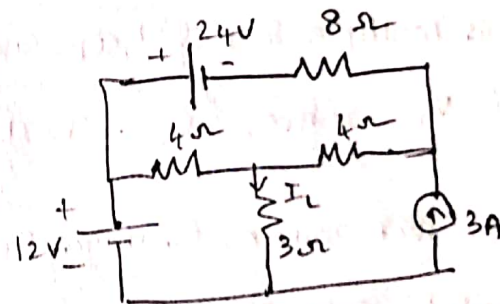② Using Super position theorem find the current through 3Ω resistor.



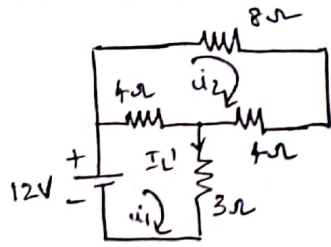Solution: - Step 1 Keep 12V source active 24V - Short, 3A - open circuit.



By KVL


$$-7i_1 + 4i_2 = -12 \quad \text{--- (1)}$$

$$4i_1 - 6i_2 = 0 \quad \text{--- (2)}$$

$$i_1 = 2A \quad i_2 = 0.5A$$

So $I_L' = 2A$ (since $i_1 = I_L'$ in this circuit)

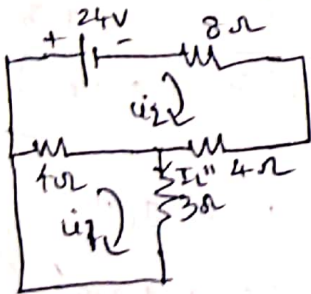Step 2 Keep 24V source active & 12V source short circuited and 3A open circuited.



let I_L'' be the current through 3Ω resistor because of the voltage source 24V

$$16i_1 - 4i_2 = -24 \quad \text{--- (1)}$$

$$7i_1 - 4i_2 = 0 \quad \text{--- (2)}$$


$$i_2 = -1.75A$$

$$i_1 = -1A$$

$$I_L'' = i_1 = -1A$$


$$I_L'' = -1A$$

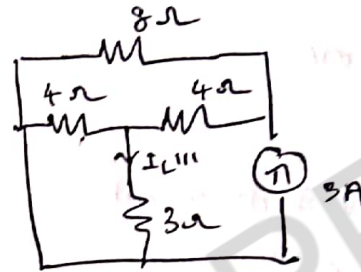Steps: Keep 12V & 24V source short circuited and 3A source - Active.




let $I_L''' = I_{3\Omega}$ due to 3A source.

$$4\Omega || 3\Omega = \frac{4 \times 3}{4+3} = 1.714\Omega$$

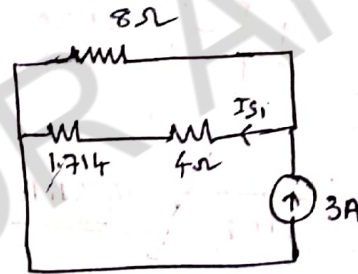

$$I_{S1} = \frac{3 \times 8}{4 + 7.14 + 8} \quad (\text{by current division rule})$$

$$I_{S1} = 1.887A$$

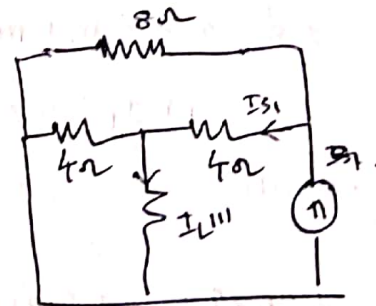

Current division rule.

$$I_{3\Omega} = I_L''' = \frac{1.887 \times 4}{4+3}$$


$$I_L''' = 1.078A$$

So $I_L = I_L' + I_L'' + I_L'''$
 $= 2 - 1 + 1.07 = 3.07A$


$$I_L = 3.07A$$

EC 3251 Circuit Analysis

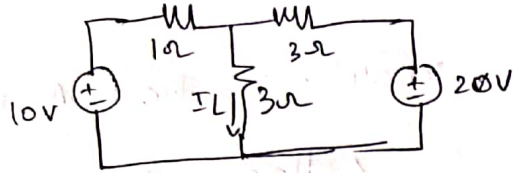
3. Find the current I_L in the circuit using Super position Theorem



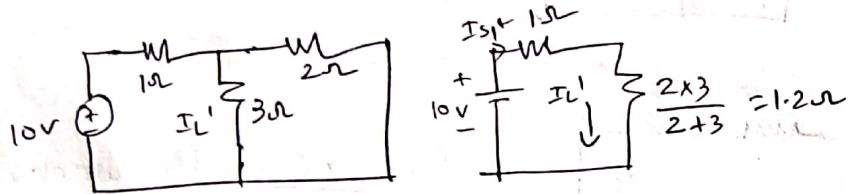Step 1: Keep 10V source active & 20V short circuit.



$$I_{S1} = \frac{10}{1+1.2} = 4.54A$$


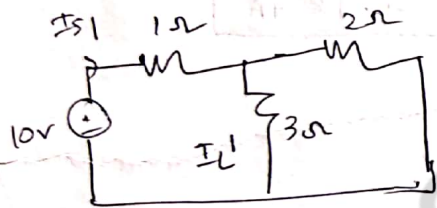


2 & 3 Ω are in parallel
So current $I_{L'}$ can be


calculated using current division rule.

$$I_{L'} = \frac{I_{S1} \times 2}{2+3} = \frac{4.54 \times 2}{2+3} = 1.8182A$$

$$I_{L'} = 1.8182A$$

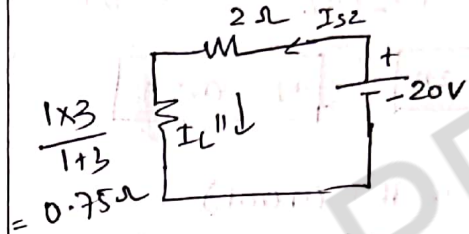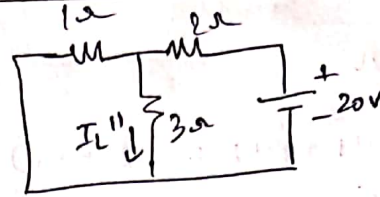

$$I_{S2} = \frac{20}{2+0.75} = 7.27A$$

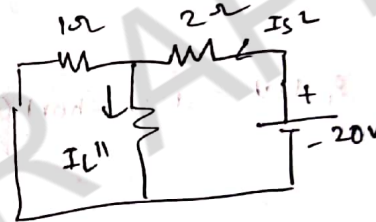

$$I_{S2} = \frac{20}{2+0.75} = 7.27A$$

$$I_{L''} = I_{S2} \times \dots$$

$$I_{L''} = I_{S2} \times \frac{1}{1+3}$$

$$I_{L''} = 1.818A$$

$$I_L = I_{L'} + I_{L''} = 1.8182 + 1.8182$$

$$I_L = 3.6364A$$

Thevenin's Theorem:-

Thevenin's Theorem states that a circuit with two terminals can be replaced with an equivalent circuit consisting of a voltage source in series with a resistance or impedance.

Steps:

Steps:- Calculate R_{th} (Thevenin's Equivalent resistance)

Step 1: Remove the load resistor

Step 2: Remove all the voltage sources (short circuit)

Step 3: Remove all the current sources (open circuit)


Step 4: Measure the Resistance across the load terminals, which is the thevenin's resistance. (R_{th})

Steps to calculate V_{th} (Thevenin's Equivalent Voltage)

Step 1:- Remove the load resistor and then measure the voltage drop across the load terminal, which gives the open circuit voltage also called Thevenin's voltage


Step 3: To calculate the current through load resistance use the formula.

$$I_L = V_{th} / R_{th} + R_L$$

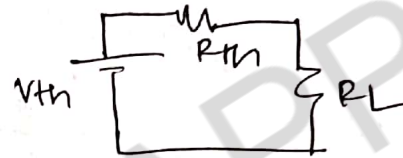


Redraw the circuit as shown above & find I_L .

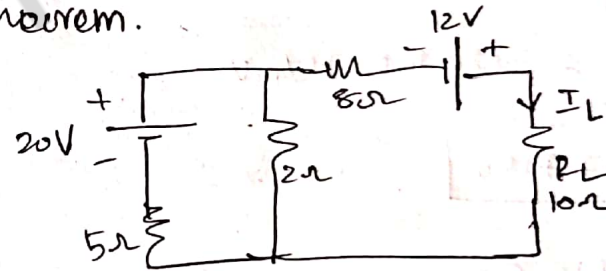Problems: Determine the current I_L using Thevenin's theorem.



Step 1:

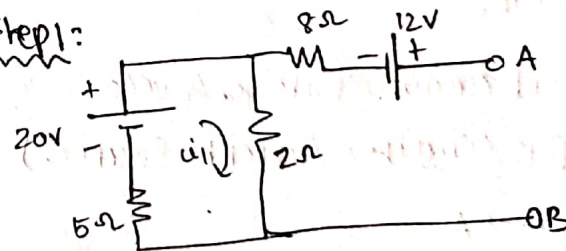

$$2i_1 + 5i_2 = 20$$

$$i_1 = 20/7 = 2.857A$$


Voltage across 2Ω resistor

$$V_{2\Omega} = I_{2\Omega} \times R$$

$$= 2.857 \times 2$$

$$V_{2\Omega} = 5.714V$$

12 v voltage source is added

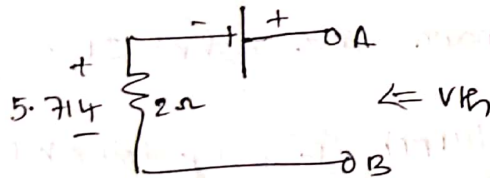


$$V_{th} = 12V + V_{2\Omega} = 12V + 5.714V$$

$$V_{th} = 17.714V$$

Step 2 To calculate R_{th}

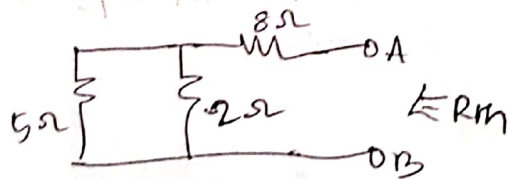Remove load, short circuit - voltage source
Open circuit - current source



$$R_{th} = 8 + \frac{5 \times 2}{5 + 2} = 8 + 1.428 = 9.428\Omega$$

$$R_{th} = 9.428\Omega$$


Step 3 To calculate load current I_L

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$


$$I_L = \frac{17.714}{9.428 + 10} = 0.9118A$$


$$I_L = 0.9118A$$

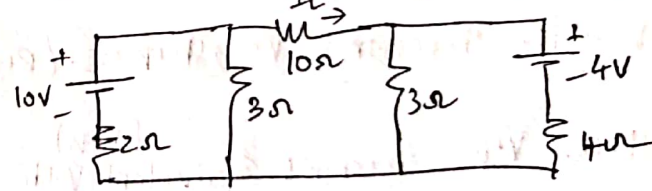2) Using Thevenin's theorem find the current I_L in the circuit.



To find V_{th} .

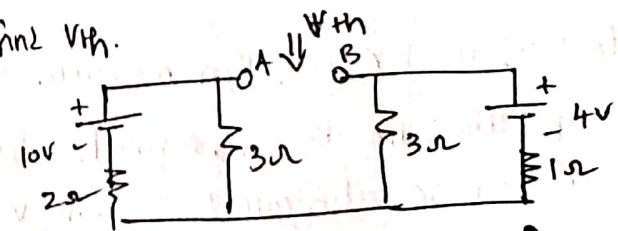

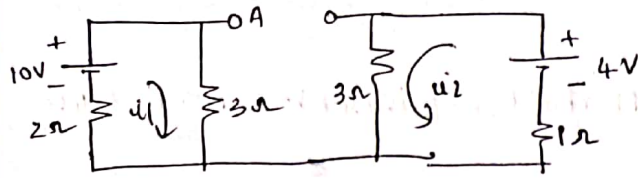

loop 1
 $3i_1 + 2i_1 = 10$

$5i_1 = 10$


$i_1 = 2A$

loop 2
 $3i_2 + 1i_2 = 4$

$4i_2 = 4$

$i_2 = 1A$

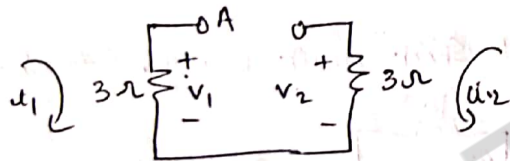
To find voltage drop across A & B, we need to find voltage drop across both the 3Ω resistors.



Voltage $v_1 = i_1 \times 3 = 2 \times 3 = 6V$

$v_2 = i_2 \times 3 = 1 \times 3 = 3V$

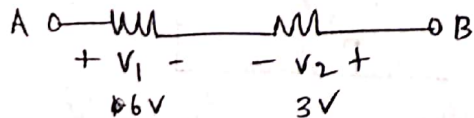
Redraw the circuit for better understanding




So $V_{AB} = V_{th} = 6V - 3V = 3V$

$V_{th} = 3V$

To find Thevenin's Resistance R_{th}

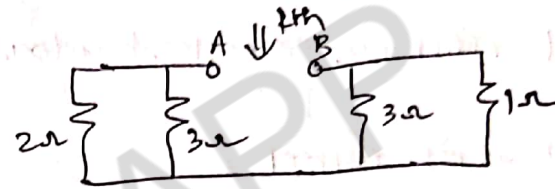


Redraw the circuit.

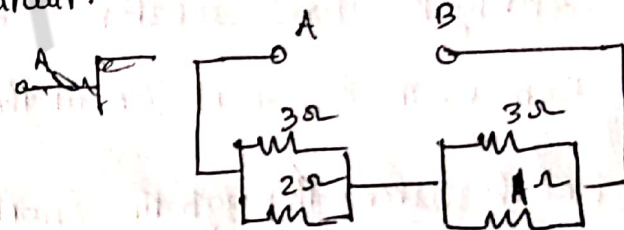

$R_{th} = \left(\frac{3 \times 2}{3 + 2} \right) + \left(\frac{3 \times 1}{3 + 1} \right)$

$R_{th} = 1.95\Omega$

Thevenin's circuit:

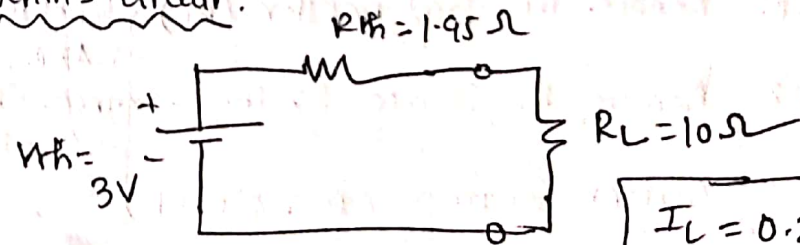

$I_L = 0.251A$

$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{3}{1.95 + 10} = 0.251A$

EC 3251 Circuit Analysis

Norton's Theorem:

States that It is possible to simplify any linear circuit to an equivalent circuit with just a single current source and parallel resistance connected to a load.

Steps: To calculate Norton's current:-

- Step 1: Identify the load resistor.
- Step 2: Remove it & short circuit the terminal.
- Step 3: find the current through the short circuit terminal which is the Norton's current (I_N).


Steps: To calculate R_{th} or R_N (Norton's Resistance)

- Step 1: Remove the load resistor (R_L) & label the terminal as A & B
- Step 2: Remove the source (voltage source - short circuit current source - open circuit)
- Step 3: measure the resistance across the terminals A & B, which gives the Norton's resistance R_N


Steps: Draw the Norton's equivalent circuit & use the formula

$$I_{RL} = \frac{I_N \cdot R_N}{R_N + R_L}$$

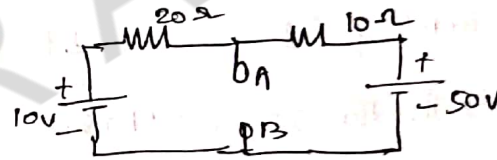Problem:- Find the thevenin's & Norton's equivalents of the circuit with respect to terminal A & B.




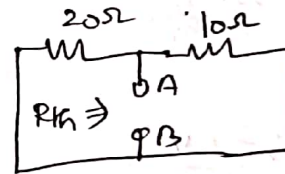Solution:- To find R_{th} short circuit voltage sources.



$$R_{th} = \frac{20 \times 10}{20 + 10} = \underline{\underline{6.667 \Omega}}$$

Step 2 To find V_{th}

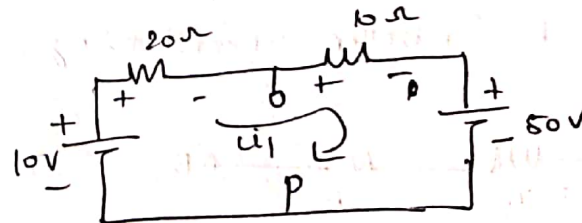



$$20i_1 + 10i_1 + 50 - 10 = 0$$

$$30i_1 = -40$$

$$i_1 = -40/30 = -1.33A$$

$$i_1 = -1.33A$$

Voltage across A & B is either

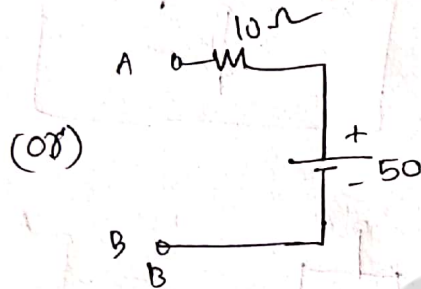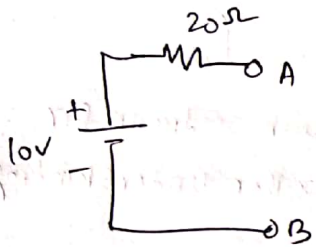

We select LHS


$$V_{AB} = 10V - \text{voltage across } 20\Omega$$

$$V_{20\Omega} = i_1 \times 20 = -26.66V$$


$$V_{Th} = V_{AB} = 10 - (-26.66V)$$

$$V_{Th} = 36.66V$$

Thevenin's Circuit:-

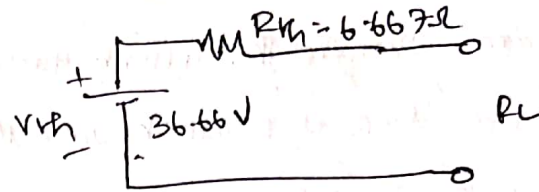

for Norton's Theorem:

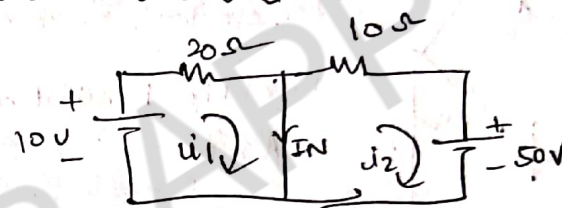

loop 1

$$20i_1 = 10$$

$$i_1 = 0.5A$$

loop 2


$$10i_2 + 50 = 0$$

$$i_2 = -5A$$


$$I_N = i_1 - i_2$$

$$= 0.5 - (-5) = I_N = 5.5A$$

Norton's equivalent ckt:

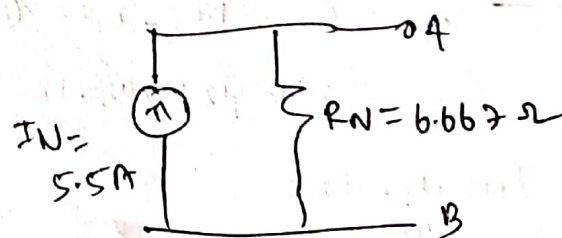


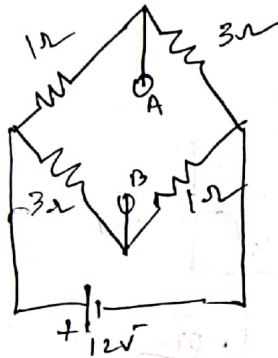② Using Norton's theorem, determine the current through an ammeter connected across A & B of the circuit, take the resistance of the ammeter as 0.5Ω



1. Remove load resistor & label the terminals as A & B.

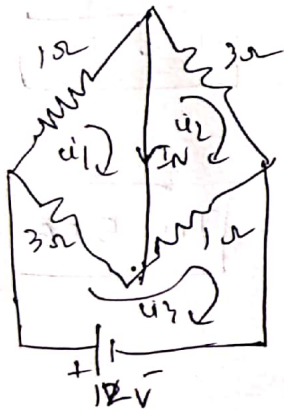2. Short circuit the terminal A & B and find the current through it



$$i_1 + 3i_2 - 3i_3 = 0 \text{ --- (1)}$$

$$4i_1 - 3i_3 = 0 \text{ --- (2)}$$

$$4i_2 - i_3 = 0 \text{ --- (3)}$$

$$-3i_1 - i_2 + 4i_3 = 12 \text{ --- (4)}$$

$$i_1 = 6A$$

$$i_2 = 2A$$


$$i_3 = 8A$$

$$I_N = i_1 - i_2$$


$$= 6 - 2 = 4A$$

$$I_N = 4A$$

To find R_{th} or R_N

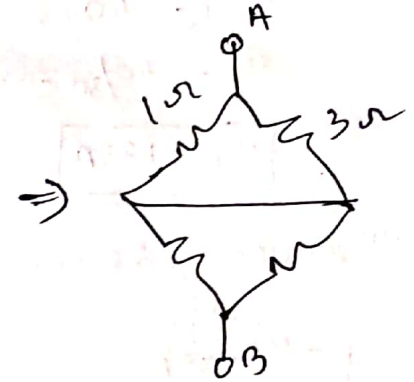


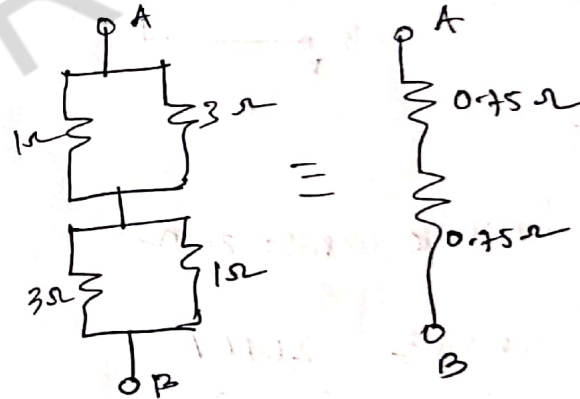Circuit is drawn for better understanding



$$R_N = 1.5 \Omega$$

Norton's Equivalent Circuit:

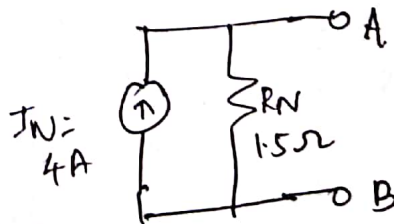

Maximum Power Transfer Theorem (MPTT)

MPTT states that maximum power will be delivered to the load when the load impedance and source impedance are equal.


Steps:

- 1) Find R_{th} (Remove voltage source; current source & load resistance) & label the terminal as A & B)
- 2) find the V_{th} (Thevenin's equivalent voltage) i.e. the voltage across the terminal A & B.
- 3) find maximum power using the formula.

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$


Problems:

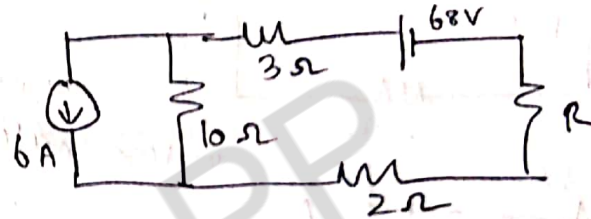1) find the value of 'R' for maximum power transfer and calculate the maximum power.




Soln

Step:- find R_{th} (Remove R_L)

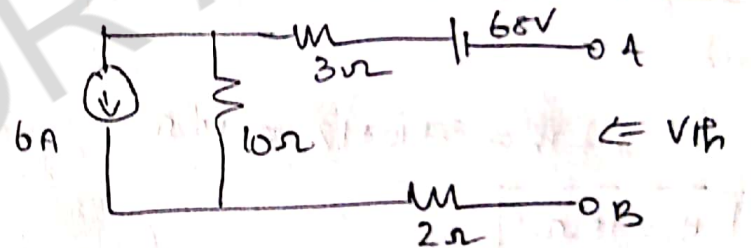

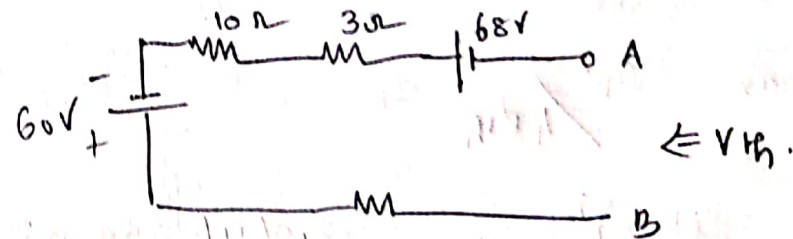$V = IR$ (By source transformation formula)





68V & 60V are in series

So $V_{th} = 128V$

EC 3251 Circuit Analysis

Step 2 To find R_{Th}

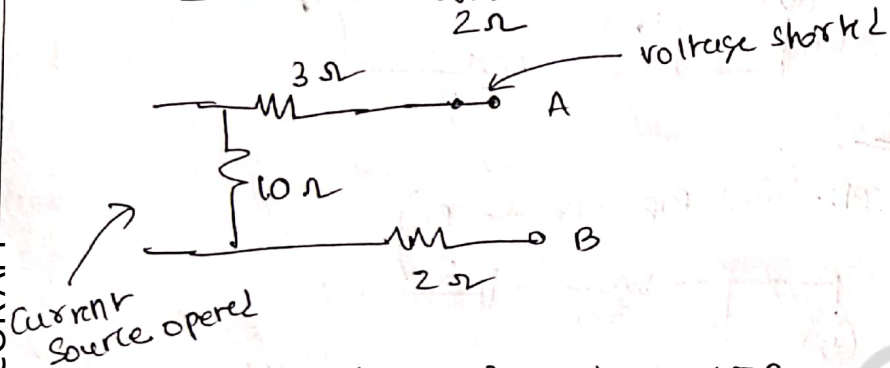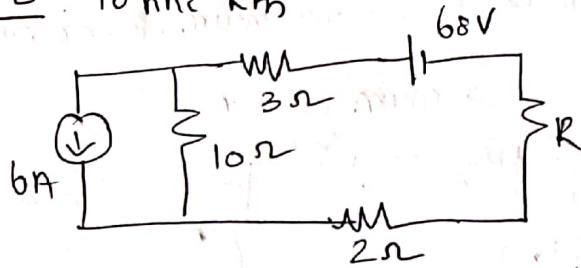

$$R_{Th} = 3 + 10 + 2 = 15\Omega$$

$$R_{Th} = 15\Omega$$

Maximum power P_{max}

$$P_{max} = \frac{V_{th}^2}{4R_{Th}}$$

$$= \frac{(128)^2}{4 \times 15} = 273.06W$$

$$P_{max} = 273.06W \quad R_{Th} = R_L = 15\Omega$$



Reciprocity Theorem:

The Reciprocity theorem states that in a linear bilateral, single source circuit, the ratio of excitation to response is constant, when the position of the excitation and response are interchanged.

Steps:-


1. Interchange the position of source & response.

[voltage - short]
[current - open]


2. Find the response at the particular branch.

3. Compare it with the response ^{that you got} before interchanging.

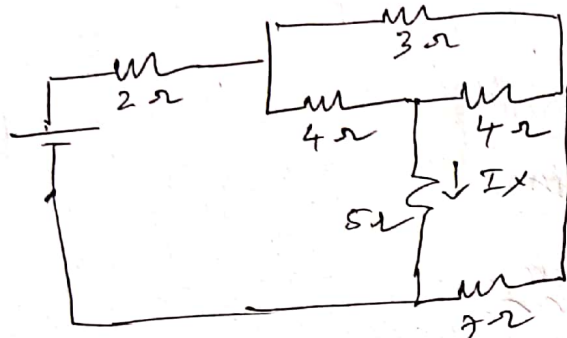1. Calculate I_x from the reciprocity theorem by Interchanging the position of $10V$ source & I_x .



Soln: Interchanging source & response.

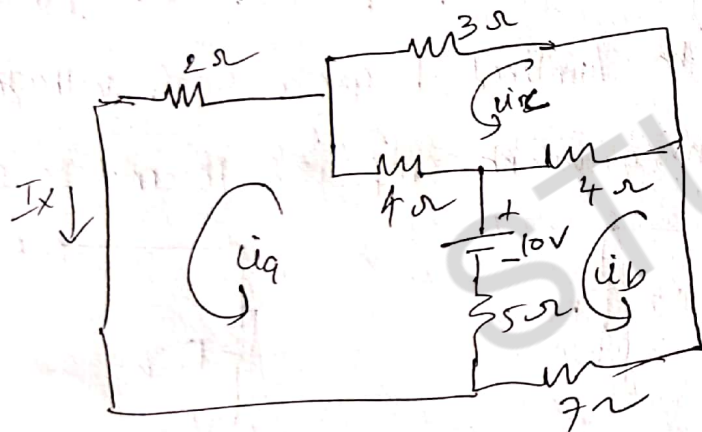

$$\begin{bmatrix} 2+4+5 & -5 & -4 \\ -5 & 5+4+7 & -4 \\ -4 & -4 & 3+4+4 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 10 \\ -11 \\ 0 \end{bmatrix}$$

$$\Delta = 1069$$


$$\Delta a = \begin{bmatrix} 10 & -5 & -4 \\ -10 & 16 & -4 \\ 0 & -4 & 11 \end{bmatrix} = 890$$

$$I_x = I_a = \frac{\Delta a}{\Delta} = \frac{890}{1069}$$

$$I_x = I_a = \frac{\Delta a}{\Delta} = \frac{890}{1069} = 0.8326A$$

$$I_x = I_a = 0.8326A$$

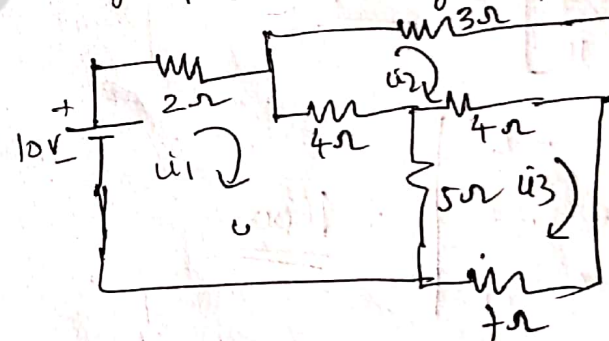for original circuit (original position of the voltage source)



$$I_x = I_1 - I_2$$


STUCORAPP

Downloaded from STUCORAPP


$$Z_{eq} = \frac{1}{\frac{1}{z_1} + \frac{1}{z_2} + \dots + \frac{1}{z_n}}$$

$$E_{eq} = \left[\frac{E_1}{z_1} + \frac{E_2}{z_2} + \frac{E_3}{z_3} + \dots + \frac{E_n}{z_n} \right] z_{eq}$$

Problem:-

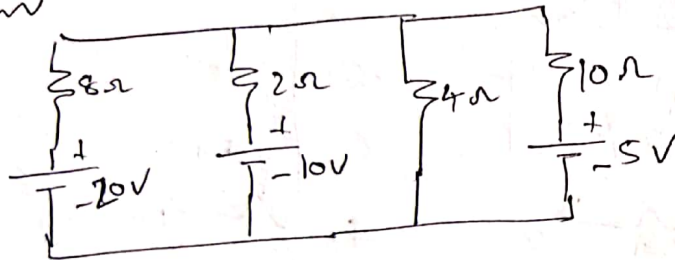

Soln Re-arranging the circuit.

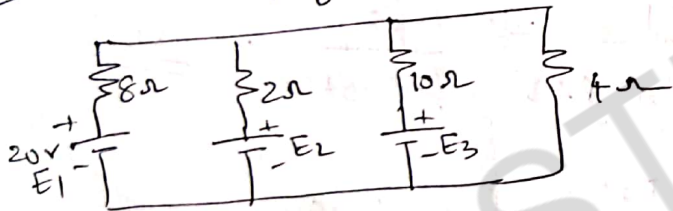


$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{8} + \frac{1}{2} + \frac{1}{10}}$$

$$R_{eq} = 1.3793 \Omega$$

$$E_{eq} = \left[E_1/R_1 + E_2/R_2 + E_3/R_3 \right] \cdot R_{eq}$$

$$= \left[\frac{20}{8} + \frac{10}{2} + \frac{5}{10} \right] \times 1.3793$$

$$E_{eq} = 11.0344 \text{ V}$$

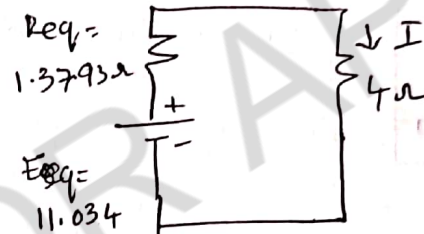


$$V = IR$$

$$I = V/R$$

$$= \frac{11.0344}{(1.3793 + 4)}$$

$$I = 2.0513 \text{ A}$$

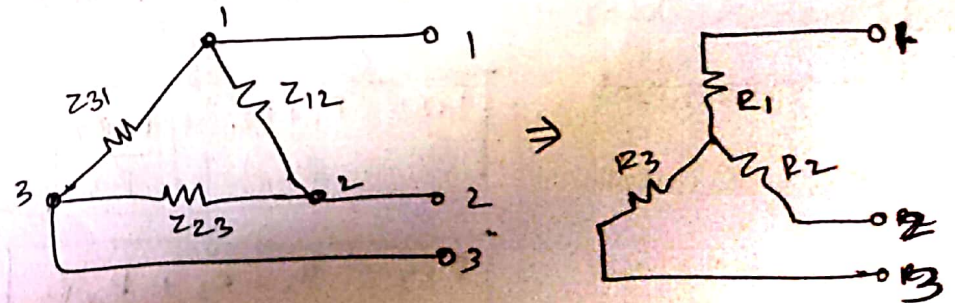Impedance in star to delta ($\lambda \rightarrow \Delta$) & Delta to star





$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

Star to Delta:

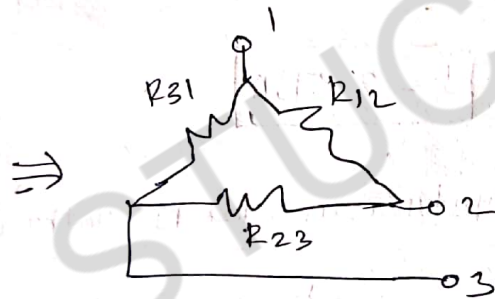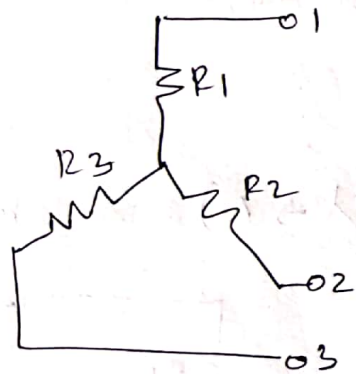


$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$


$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$

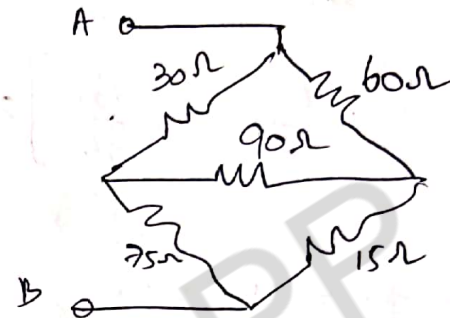Problem: Find the equivalent resistance of the network.




Soln

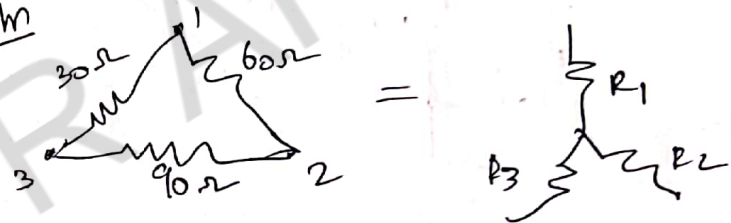

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{31} + R_{23}} = \frac{60 \times 30}{30 + 90 + 60} = \underline{\underline{10\Omega}}$$


$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{60 \times 90}{30 + 90 + 60} = \underline{\underline{30\Omega}}$$
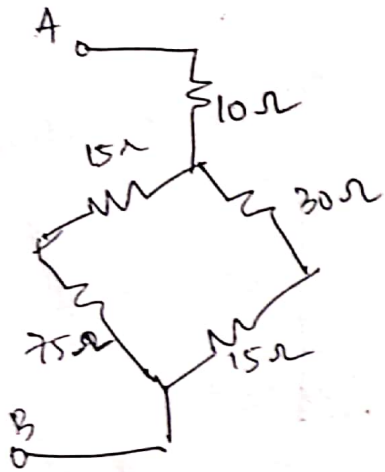
$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{30 \times 90}{30 + 90 + 60} = \underline{\underline{15\Omega}}$$




15Ω & 75Ω are in series

30Ω & 15Ω are in series

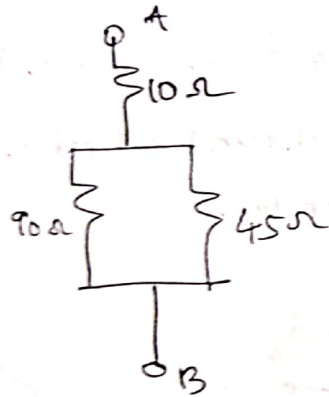


90 & 45 are in parallel.
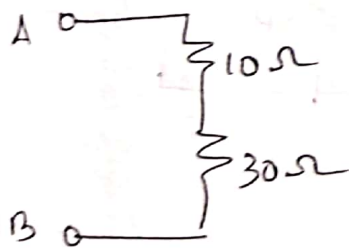
$$90 \parallel 45 = \underline{\underline{30\Omega}}$$




$$R_{AB} = 40\Omega$$

Duality:

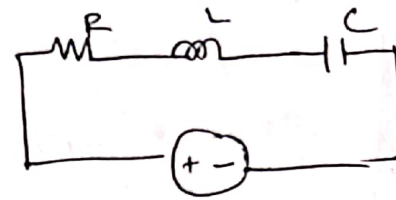

Original network

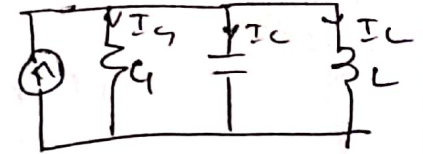

Dual Network

* In an electrical network, electrical terms are associated in to pairs called as duals.

* A dual of a expression is formed by interchanging

voltage & current in the expressions

Dual Elements.

| original | Dual. |
|----------------|-----------------|
| Resistance | Conductance |
| Capacitance | Inductance |
| Inductance | Capacitance. |
| Voltage source | Current source. |

Original

Dual

Current Source

Voltage Source

Series Branch

Parallel Branch

Mesh equation

Node equation

KCL

KVL

Switch closed at $t=0$

Switch opened at $t=0$

Open circuit

Short circuit

Short circuit

Open circuit


Impedance

Admittance


Reactance

Susceptance

Draw the dual of the network shown.

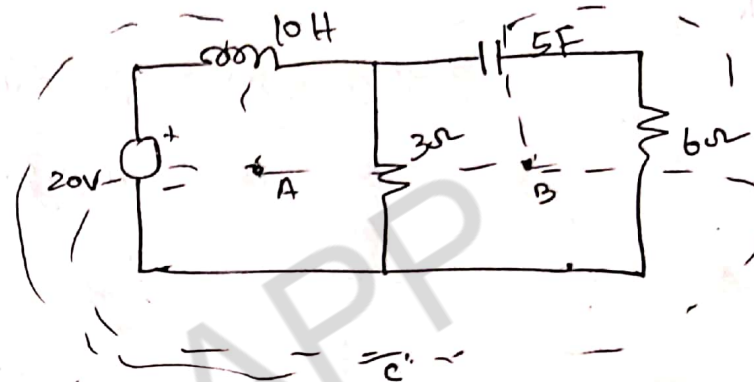

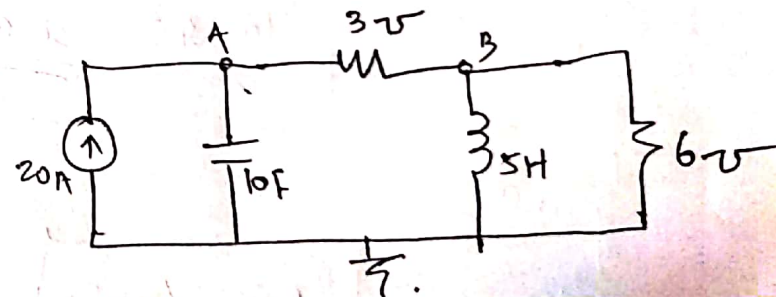- ① Label A & B inside loops & place reference node outside
- ② Draw a dotted line from each node to reference node through all the available branches.
- ③ Draw its Dual.




Sinusoid \rightarrow is a signal that has the form of the cosine or sine function.

$$v(t) = V_m \sin \omega t$$

V_m = amplitude of the sinusoid.

ω = angular frequency in radian/s

ωt = the argument of the sinusoid.

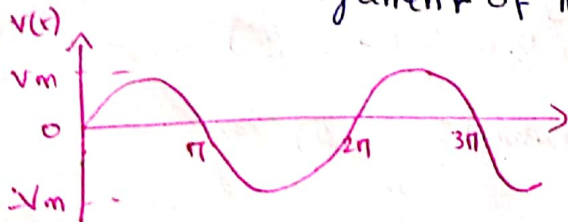

$$\omega T = 2\pi$$

$$T = \frac{2\pi}{\omega}$$

T = Period of sinusoid.

$$f = 1/T$$

$$\omega = 2\pi f$$


f = frequency in hertz \Rightarrow or
' f ' is also called cycle frequency.

ω = angular frequency.

More general expression for the sinusoid.

$$v(t) = V_m \sin(\omega t + \phi)$$

ϕ = phase.

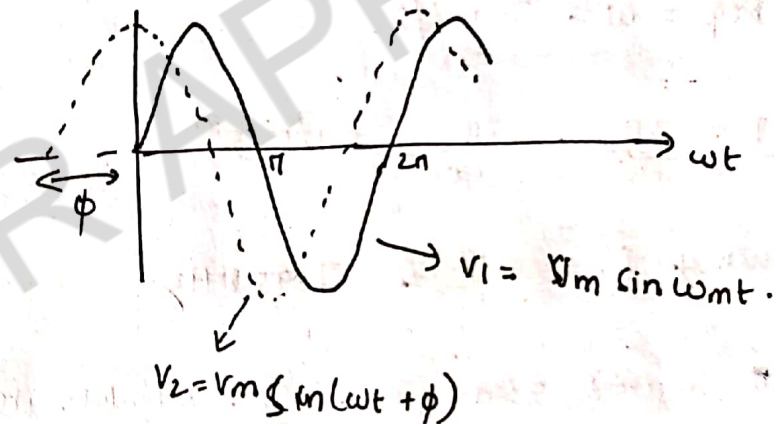

The starting point of v_2 occurs first in time, therefore

we say that v_2 leads v_1 by ϕ (or) v_1 lags v_2 by ϕ

if $\frac{\phi}{\omega} = 0 \Rightarrow v_1$ & v_2 are in-phase.

$\phi \neq 0 \Rightarrow v_1$ & v_2 are out-of phase.

① Find the amplitude, phase & frequency of the sinusoid.

$$v(t) = 12 \cos(50t + 10^\circ)$$

$$\text{Amplitude} = V_m = 12 \text{ V}$$

$$\text{Phase} = \phi = 10^\circ$$

$$\text{Angular freq} = \omega = 50 \text{ rad/s}$$

$$\text{Period } T = \frac{2\pi}{\omega} = \frac{2\pi}{50} = 0.1257 \text{ s}$$

$$\text{Frequency } f = \frac{1}{T} = 7.958 \text{ Hz}$$

② Given the sinusoid $5 \sin(4\pi t - 60^\circ)$, calculate its amplitude, phase, angular frequency, period and frequency.

$$\text{Amplitude} = 5 \text{ V}$$

$$\text{Phase} = -60^\circ$$

$$\text{Angular frequency } \omega = 4\pi = 4 \times 3.14 = 12.56 \text{ rad/sec}$$

$$\text{Frequency } f = \frac{\omega}{2\pi} = \frac{12.56}{2 \times \pi} = \underline{\underline{2 \text{ Hz}}}$$

① Calculate the phase angle between $v_1 = -10 \cos(\omega t + 50^\circ)$ and $v_2 = 12 \sin(\omega t - 10^\circ)$ state which sinusoid is leading.

$$v_1 = -10 \cos(\omega t + 50^\circ)$$

$$= 10 \cos(\omega t + 50^\circ - 180^\circ)$$

$$= 10 \cos(\omega t - 130^\circ) \quad (\text{or}) \quad 10 \cos(\omega t + 230^\circ)$$

1 --- ①

$$v_2 = 12 \sin(\omega t - 10^\circ) = 12 \cos(\omega t - 10^\circ - 90^\circ)$$

$$v_2 = 12 \cos(\omega t - 100^\circ) \quad \text{--- ②}$$

From ① & ② Phase difference between v_1 & v_2 is 30° .

v_2 leads v_1 by 30° .

Phasors:

A Phasor is a complex number that represents the amplitude and phase of a sinusoid.

Rectangular form.

$Z = x + jy$ ← Complex no in rectangular form.

$j = \sqrt{-1}$

x ⇒ real part

y ⇒ imaginary part

Complex no. can also be written in polar form:-

Polar form:

$Z = r \angle \phi = r e^{j\phi}$

Complex no. 'z' can also be written in polar or exponential form.

r = magnitude of 'z'

ϕ = phase of z

$Z = x + jy$ ⇒ Rectangular form

$Z = r \angle \phi$ ⇒ Polar form

$Z = r e^{j\phi}$ ⇒ Exponential form.

Addition & Subtraction are better performed in Rectangular form.

Multiplication & Division are better performed in Polar form

Addition:

$Z_1 + Z_2 = (x_1 + x_2) + j(y_1 + y_2)$

Subtraction:

$Z_1 - Z_2 = (x_1 - x_2) + j(y_1 - y_2)$

Multiplication:

$Z_1 Z_2 = r_1 r_2 \angle \phi_1 + \phi_2$

Division:

$\frac{Z_1}{Z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$

Reciprocal:

$$1/z = 1/z \angle -\phi$$

Squareroot

$$\sqrt{z} = \sqrt{r} \angle \phi/2$$


Complex Conjugate:

$$z^* = x - jy = r \angle -\phi = r e^{-j\phi}$$

$$v(t) = V_m \cos(\omega t + \phi) = \text{Time Domain Representation}$$

$$V = V_m \angle \phi = \text{Phasor domain representation}$$

Phasor-Diagram:

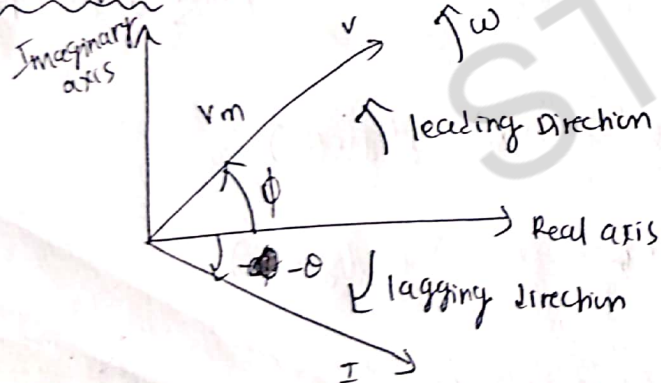

Phasor Diagram showing.

$$V = V_m \angle \phi \quad \& \quad I = I_m \angle -\theta$$

Problems:

Transform the sinusoids to phasors.

① $i = 6 \cos(50t - 40^\circ) \text{ A}$

$$I = 6 \angle -40^\circ \text{ A}$$

② $v = -4 \sin(30t + 150^\circ) \text{ V}$

$$= 4 \cos(30t + 150^\circ + 90^\circ)$$

(Since $-\sin A = \cos(A + 90^\circ)$)

$$= 4 \cos(30t + 140^\circ) \text{ V}$$

$$V = 4 \angle 140^\circ \text{ V}$$

③ $v = -7 \cos(2t + 40^\circ) \text{ V}$

$$= 7 \cos(2t + 40 + 180)$$


$$= 7 \cos(2t + 220) \text{ V}$$

$$V = 7 \angle 220^\circ \text{ V}$$

④ $i = 4 \sin(10t + 10^\circ) A$
 $= 4 \cos(10t + 10^\circ - 90^\circ) A$
 $= 4 \cos(10t - 80^\circ) A$

$i = 4 \angle -80^\circ A$

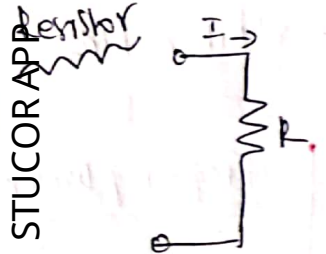Phasor relationships for circuit elements:-



$i = I_m \cos(\omega t + \phi) = \text{Current}$
 $V = iR$
 $V = R I_m \cos(\omega t + \phi)$


Phasor form:-

$V = R I_m \angle \phi$
 $I = I_m \angle \phi$


$V = IR$

Voltage and current are in-phase.

Phasor Diagram for Resistor

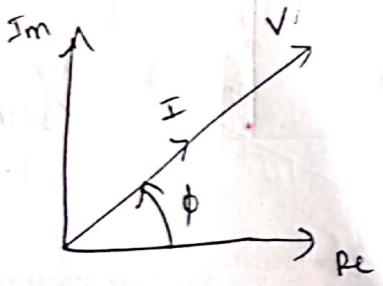


For Inductor:-

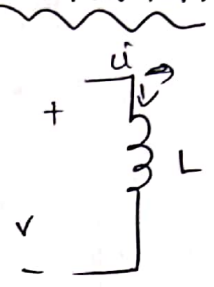

Time Domain

$V = L \frac{di}{dt}$

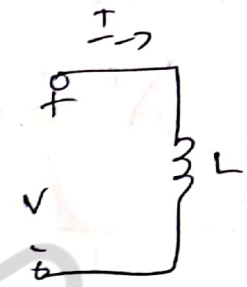


freq-domain

$V = j\omega L I$

Assume current through inductor is $i = I_m \cos(\omega t + \phi)$

$V = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \phi)$

~~sin A~~

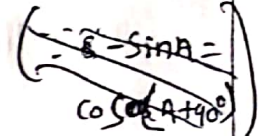


$V = \omega L I_m \cos(\omega t + \phi + 90^\circ)$

$\therefore -\sin A = \cos(A + 90^\circ)$

$V = \omega L I_m \angle \phi + 90^\circ$

$I_m \angle \phi = I$


Phasor diagram for Inductor:-

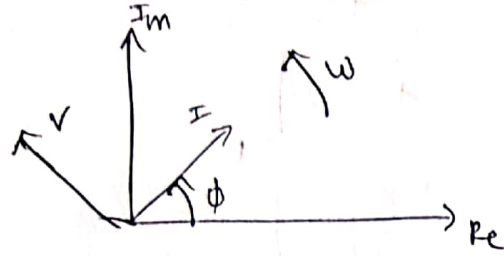

Voltage & current are 90° out of phase.

Current lags voltage by 90°.

For Capacitor:-

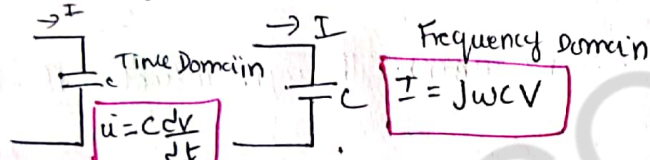


assume the voltage across it is $v = V_m \cos(\omega t + \phi)$

Current through the capacitor is

$$i = C \frac{dv}{dt}$$
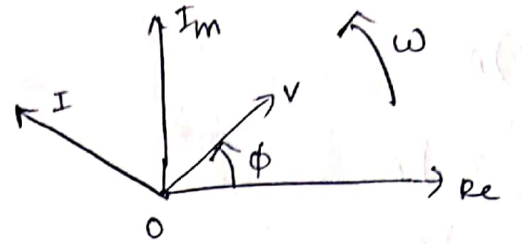
$$I = jwCV \Rightarrow V = \frac{I}{jwC}$$



Current & voltage are 90° out of phase.

Current leads the voltage by 90°.

Summary of voltage current relationships.

| Element | Time Domain | Frequency Domain |
|---------|---------------|---------------------|
| R | $V = Ri$ | $V = RI$ |
| L | $V = L di/dt$ | $V = jwLI$ |
| C | $i = C dv/dt$ | $V = \frac{I}{jwC}$ |

EC 3251 Circuit Analysis

Problem:-

The voltage $V = 12 \cos(60t + 45^\circ)$ is applied to a 0.1H Inductor, Find the steady state current through the inductor.

Soln

$$V = j\omega L I \quad \omega = 60 \text{ rad/s}$$

$$V = 12 \angle 45^\circ \text{ V}$$

$$I = \frac{V}{j\omega L} = \frac{12 \angle 45^\circ}{j60 \times 0.1} = \frac{12 \angle 45^\circ}{6 \angle 90^\circ}$$

$$I = 2 \angle -45^\circ \text{ A}$$

$$I = 2 \cos(60t - 45^\circ) \text{ A}$$

(Time Domain)

If voltage $v = 6 \cos(100t - 30^\circ)$ is applied to a 50mF capacitor, calculate the current through it.

$$V = I / j\omega C$$

$$I = V j\omega C$$


$$= 6 \angle -30^\circ \times j100 \times 50 \times 10^{-6}$$

$$I = 30 \cos(100t + 60^\circ) \text{ mA}$$

Impedance & Admittance of Passive Elements:-

| Element | Impedance | Admittance |
|---------|-------------------|-------------------|
| R | $Z = R$ | $Y = 1/R$ |
| L | $Z = j\omega L$ | $Y = 1/j\omega L$ |
| C | $Z = 1/j\omega C$ | $Y = j\omega C$ |

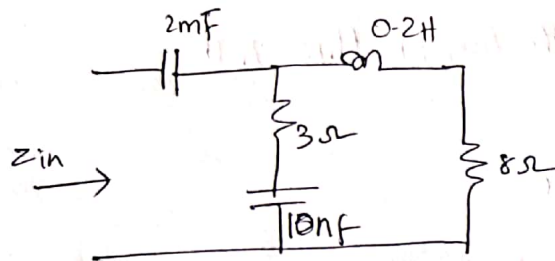Find the input impedance of the circuit; operate at $\omega = 500 \text{ rad/s}$



$$Z_1 = \frac{1}{j\omega C} = \frac{1}{j500 \times 2 \times 10^{-3}} = -j10 \Omega$$

$$Z_2 = 3 + \frac{1}{j\omega C} = 3 + \frac{1}{j500 \times 10 \times 10^{-3}} = (3 - j2) \Omega$$

$$Z_3 = 8 + j\omega L = 8 + j500 \times 0.2 = (8 + j10) \Omega$$


Input Impedance

$$Z = Z_1 + Z_2 \parallel Z_3$$

$$= -j10 + \frac{(3 - j2)(8 + j10)}{11 + j8}$$

$$Z_{in} = 3.22 - j11.07 \Omega$$

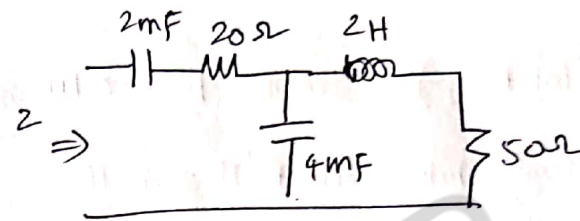Determine the input impedance of the circuit at $\omega = 100 \text{ rad/s}$



$$Z = 32.38 - j73.76 \Omega$$

$$Z_1 = 20 + \frac{1}{j\omega C} = 20 + \frac{1}{j100 \times 2 \times 10^{-3}} = 20 - 50j$$

$$Z_2 = \frac{1}{j\omega C} = \frac{1}{j100 \times 4 \times 10^{-3}} = -25j$$

$$Z_3 = 50 + j\omega L = 50 + j100 \times 2 = 50 + 20j$$


$$Z_1 + (Z_2 \parallel Z_3)$$

$$\frac{(20 - 50j) + \frac{(-25j)(50 + 20j)}{(-25j + 50 + 20j)}}{50.24 \angle -5.71}$$

$$= 53.85 \angle -68.1 + 26.79 \angle -63.02$$

$$Z = 32.23 - j73.83 \Omega$$


Determine $V_o(t)$ in the circuit.

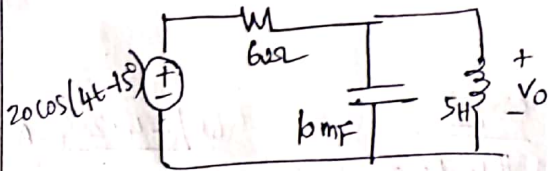

$$V_s = 20 \cos(4t - 15^\circ) = 20 \angle -15^\circ \text{ V}, \quad \omega = 4$$

$$10 \text{ mF} = \frac{1}{j\omega C} = \frac{1}{j4 \times 10 \times 10^{-3}} = -j25 \Omega$$
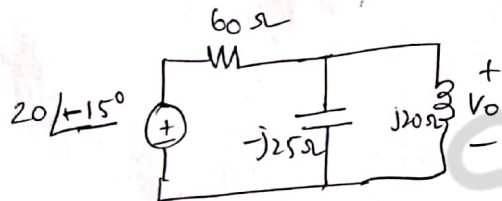
$$5 \text{ H} = j\omega L = j4 \times 5 = j20 \Omega$$




$$Z_1 = 60 \Omega, \quad Z_2 = -j25 \parallel j25 = j100 \Omega$$

$$V_o = \frac{Z_2}{Z_1 + Z_2} V_s = \frac{j100}{60 + j100} (20 \angle -15^\circ)$$

$$= (0.8575 \angle 30.96^\circ) (20 \angle -15^\circ) = 17.15 \angle 15.96^\circ \text{ V}$$

Time domain $\rightarrow V_o(t) = 17.15 \cos(4t + 15.96^\circ) \text{ V} \leftarrow$

(2) Calculate V_o

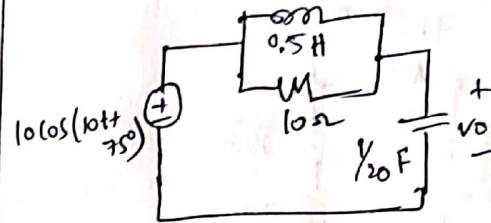

$$V_s = 10 \cos(10t - 75^\circ) \text{ V} \quad (0.5 \text{ H} \parallel 10 \Omega) + (1/20 \text{ F})$$

$$V_s = 10 \angle -75^\circ \text{ V}$$

$$\omega = 10 \text{ rad/sec}$$

$$Z_1 = 10 \Omega, \quad Z_2 =$$

$$Z_1 = (0.5 \text{ H} \parallel 10 \Omega) \quad Z_2 = (1/20 \text{ F})$$

$$0.5 \text{ H} \Rightarrow j\omega L = j10 \times 0.5 =$$

$$Z_1 = j\omega L = j10 \times 0.5 = 5j$$

$$Z_2 = 10 \Omega$$

$$Z_3 = 1/j\omega C = 1/j10 \times 1/20 = 1/0.5j = -2j$$

$$Z = (Z_1 \parallel Z_2) + Z_3$$

$$(5j \parallel 10) + (-2j)$$

$$= \frac{(10 \times j5)}{(10 + j5)} - 2j$$

$$= \frac{(j50)}{(10 + j5)} - 2j$$

$$2 + j4 - 2j$$

$$Z_{in} = 2 + j2 \Omega$$


$$I = V/R_{in} = \frac{10 \angle -75^\circ}{2 + j2} = 3.06 + j1.76j$$

$$V_o = I \times Z_3 = (3.06 + j1.76j) (-2j)$$

$$V_o(t) = 7.06 \angle -60^\circ \text{ (or)} 7.06 \cos(10t - 60^\circ)$$

$$V_o(t) = 7.06 \cos(10t - 60^\circ) \text{ V}$$

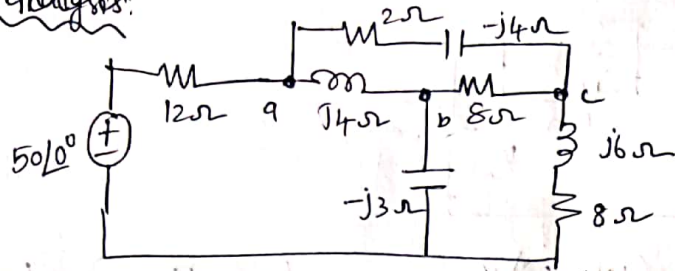Find the current I' in the circuit
Mesh Analysis:



Delta network connected to nodes a, b, & c can be converted to the Y network

$$Z_{an} = \frac{j4(2-j4)}{j4+2-j4+8} = \frac{4(4+j2)}{10} = (1.6 + j0.8) \Omega$$

$$Z_{bn} = \frac{j4(8)}{10} = j3.2 \Omega$$

$$Z_{cn} = \frac{8(2-j4)}{10} = (1.6 - j3.2) \Omega$$


The total impedance at the source terminals: Z

$$\begin{aligned} Z &= 12 + Z_{an} + (Z_{bn} - j3) \parallel (Z_{cn} + j6 + 8) \\ &= 12 + 1.6 + j0.8 + (j0.2) \parallel (9.6 + j2.8) \\ &= 13.6 + j0.8 + \frac{j0.2(9.6 + j2.8)}{9.6 + j3} \end{aligned}$$

$$= 13.6 + j1 = 13.64 \angle 4.204^\circ \Omega$$

The desired current is
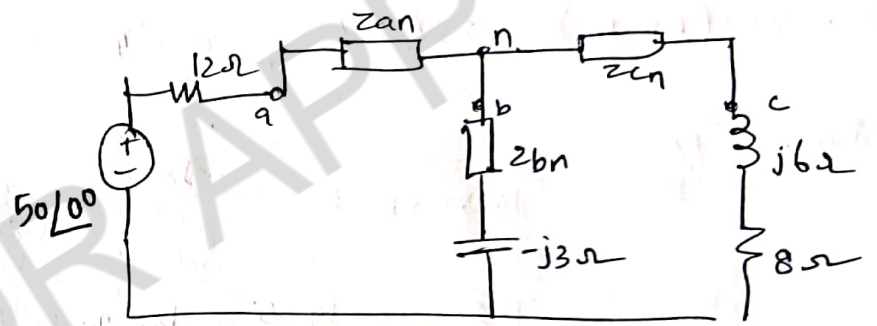
$$I = \frac{V}{Z} = \frac{50 \angle 0^\circ}{13.64 \angle 4.204^\circ} = 3.666 \angle -4.204^\circ \text{ A}$$




STUCOR APP

Downloaded from STUCOR APP

EC 3251 Circuit Analysis

Mesh Analysis:

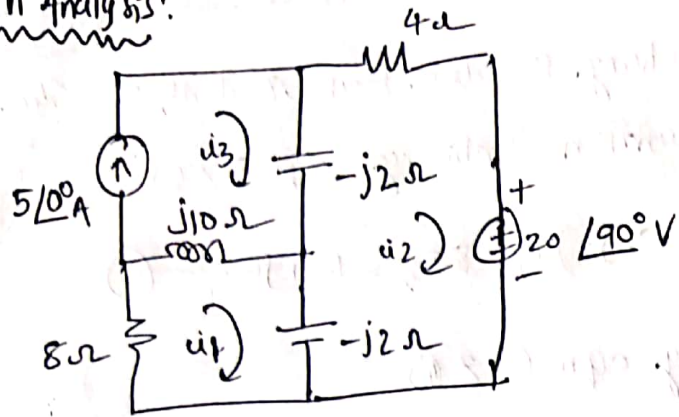

KVL @ loop 1

$$(8 + j10 - j2)I_1 - (-j2)I_2 - j10I_3 = 0 \quad \text{--- (1)}$$

KVL @ loop 2

$$(4 - j2 - j2)I_2 - (-j2)I_1 - (-j2)I_3 + 20\angle 90^\circ = 0 \quad \text{--- (2)}$$

From loop 3

$$I_3 = 5\angle 0^\circ \quad \text{--- (3) sub mis in (1) & (2)}$$

$$(8 + j8)I_1 + j2I_2 = j50 \quad \text{--- (4)}$$

$$j2I_1 + (4 - j4)I_2 = -j20 - j10 \quad \text{--- (5)}$$

$$\begin{bmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j30 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{vmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j30 \end{bmatrix}$$


$$= 32(1 + j)(1 - j) + 4 = 68$$

$$\Delta_2 = \begin{vmatrix} 8 + j8 & j50 \\ j2 & -j30 \end{vmatrix} = 340 - j240 = 416.17 \angle -35.22^\circ$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{416.17 \angle -35.22^\circ}{68} = 6.12 \angle -35.22^\circ \text{ A}$$

$$I_0 = -I_2 = 6.12 \angle 144.78^\circ \text{ A}$$

② Solve for V_0 in the fig.

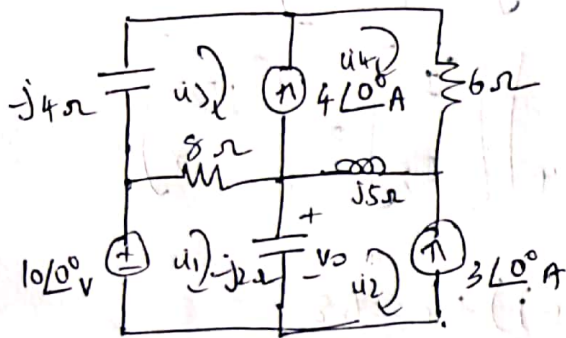

for loop 1

$$-10 + (8 - j2)I_1 - (-j2)I_2 - 8I_3 = 0$$

$$(8 - j2)I_1 + j2I_2 - 8I_3 = 10 \quad \text{--- (1)}$$

for loop 2

$$I_2 = -3 \quad \text{--- (2)}$$

for Super Mesh

$$(8 - j4)I_3 - 8I_1 + (6 + j5)I_4 - j5I_2 = 0 \quad \text{--- (3)}$$

From loop 3 & 4

$$I_4 = I_3 + 4 \quad \text{--- (4)}$$

Instead of solving the above four equations, we reduce them to two by elimination combining eqn (1) & (2)

$$(8 - j2)I_1 - 8I_3 = 10 + j6 \quad \text{--- (5)}$$

by combining eqn (3) & (4)

$$-8I_1 + (14 + j)I_3 = -24 + j35 \quad \text{--- (6)}$$

$$\begin{bmatrix} 8 - j2 & -8 \\ -8 & 14 + j \end{bmatrix} \begin{bmatrix} I_1 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 + j6 \\ -24 - j35 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 8 - j2 & -8 \\ -8 & 14 + j \end{vmatrix} = 112 + j8 - j28 + 2 - 64 = \underline{\underline{50 - j20}}$$

$$\Delta_1 = \begin{vmatrix} 10 + j6 & -8 \\ -24 - j35 & 14 + j \end{vmatrix} = 140 + j10 + j84 - 6 - 192 - j280$$


$$= -58 - j186 //$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{-58 - j186}{50 - j20} = \underline{\underline{3.618 \angle 274.5^\circ \text{ A}}}$$

$$\begin{aligned} \text{Voltage } V_0 &= -j2(I_1 - I_2) = -j2(3.618 \angle 274.5^\circ + 3) \\ &= -7.236 - j6.568 = \underline{\underline{9.756 \angle 222.32^\circ \text{ V}}} \end{aligned}$$

EC 3251 Circuit Analysis

Nodal Analysis:

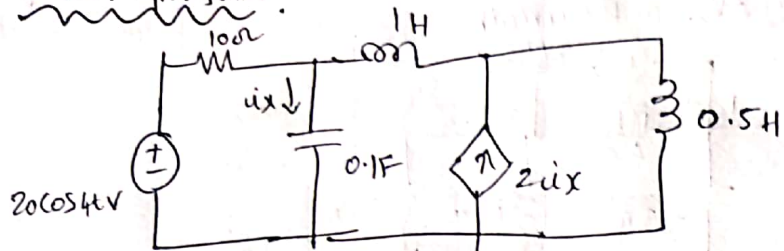

First convert to freq. domain.


$$20 \cos 4t = 20 \angle 0^\circ, \omega = 4 \text{ rad/s.}$$

$$1 \text{ H} \Rightarrow j\omega L = j4$$

$$0.5 \text{ H} \Rightarrow j\omega L = j2$$

$$0.1 \text{ F} = 1/j\omega C = -j2.5$$

freq. domain equivalent circuit.

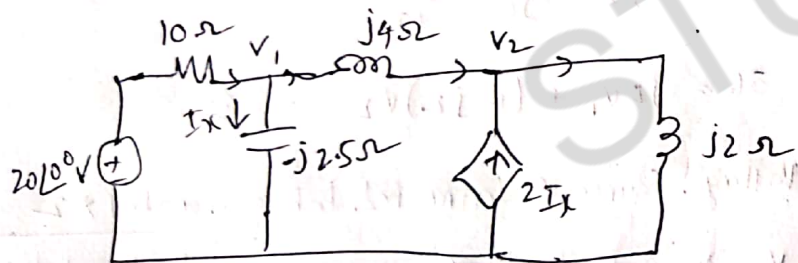

Applying KCL at node 1

$$\frac{20 - v_1}{10} = \frac{v_1}{-j2.5} + \frac{v_1 - v_2}{j4}$$

$$(1 + j1.5)v_1 + j2.5v_2 = 20 \quad \dots \textcircled{1}$$

At node 2

$$2I_x + \frac{v_1 - v_2}{j4} = \frac{v_2}{j2}$$

But $I_x = v_1 / -j2.5$

$$\frac{2v_1}{-j2.5} + \frac{v_1 - v_2}{j4} = \frac{v_2}{j2}$$

Simplifying we get

$$11v_1 + 15v_2 = 0 \quad \dots \textcircled{2}$$

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{vmatrix} = 15 - j5$$

$$\Delta_1 = \begin{vmatrix} 20 & j2.5 \\ 0 & 15 \end{vmatrix} = 300, \quad \Delta_2 = \begin{vmatrix} 1+j1.52 & 0 \\ 11 & 0 \end{vmatrix} = -220$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{300}{15-j5} = 18.97 \angle 18.43^\circ \text{ V}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-220}{15-j5} = 13.91 \angle 198.3^\circ \text{ V}$$


The current I_x is given by

$$I_x = \frac{V_1}{-j2.5} = \frac{18.97 \angle 18.43^\circ}{2.5 \angle -90^\circ} =$$


$$= 7.59 \angle 108.4^\circ \text{ A}$$

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$

2) Compute V_1 & V_2 in the circuit.

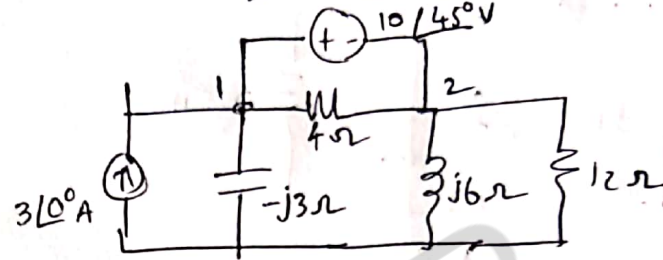

Nodes 1 & 2 form a supernode

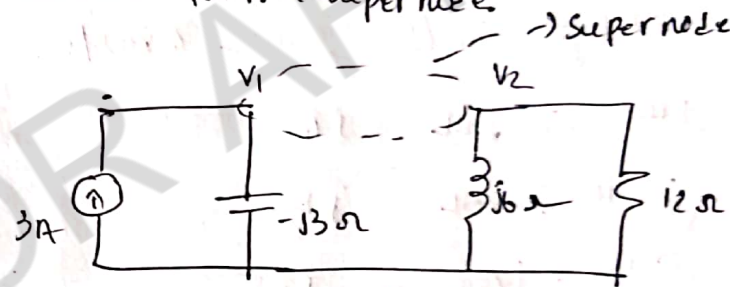

Applying KCL

$$3 = \frac{V_1}{-j3} + \frac{V_2}{j6} + \frac{V_2}{12}$$

$$36 = j4V_1 + (1-j2)V_2 \quad \dots \text{①}$$

But a voltage source is connected between nodes 1 & 2

$$\text{So } V_1 = V_2 + 10 \angle 45^\circ \quad \dots \text{②} \quad \boxed{V_1 - V_2 = 10 \angle 45^\circ}$$

Subs ② in ①

$$36 - 40 \angle 135^\circ = (1+j2)V_2 \quad | \quad V_2 = 31.41 \angle -87.18^\circ \text{ V}$$

From ②

$$V_1 = V_2 + 10 \angle 45^\circ = 25.78 \angle -70.48^\circ \text{ V} \quad \boxed{V_1 = 25.78 \angle -70.48^\circ \text{ V}}$$

Instantaneous power & Average power:-

Instantaneous power = instantaneous voltage \times instantaneous current

$$P(t) = v(t) i(t)$$

The instantaneous power (watts) is the power at any instant of time.

Let

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

V_m & $I_m \Rightarrow$ are the amplitudes

θ_v & $\theta_i \Rightarrow$ phase angles of voltage & current respectively.

$$P(t) = v(t) i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$\cos A \cos B = \frac{1}{2} [\cos(A-B) + \cos(A+B)]$$

$$P(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) \quad \text{--- (1)}$$

Constant or time dependent

Sinusoidal fn

$P(t)$ can be positive or negative

If $P(t) = \text{positive} \Rightarrow$ power is absorbed by the circuit

if $P(t) = \text{negative} \Rightarrow$ power is absorbed by the source.

Average power:

average power in watts, is the average of the instantaneous power over one period.

$$P = \frac{1}{T} \int_0^T P(t) dt \quad \text{--- (2)}$$

Subs (2) in (1)

$$P = \frac{1}{T} \int_0^T \frac{1}{2} v_m i_m \cos(\theta_v - \theta_i) dt$$

$$+ \frac{1}{T} \int_0^T \frac{1}{2} v_m i_m \cos(2\omega t + \theta_v + \theta_i) dt$$

$$= \frac{1}{2} v_m i_m \cos(\theta_v - \theta_i) \frac{1}{T} \int_0^T dt$$

$$+ \frac{1}{2} v_m i_m \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt$$

Constant

Sinusoidal

first integral is constant, second is sinusoidal.

average of a sinusoid over its period is zero.

So Average power is

$$P = \frac{1}{2} v_m i_m \cos(\theta_v - \theta_i)$$

Since $\cos(\theta_v - \theta_i) = \cos(\theta_i - \theta_v) \Rightarrow$ difference in the phases of the voltage & current.

$P(t) =$ time varying

$P =$ does not depend on time

for instantaneous power we must know $v(t)$ & $i(t)$
(time varying)

But average power can be calculated in when the voltage & current are expressed in freq. time domain. or freq. domain

eg. $V(t) = v_m \angle \theta_v$

$$I(t) = i_m \angle \theta_i$$

$$P = \frac{1}{2} VI = \frac{1}{2} v_m i_m \angle \theta_v - \theta_i$$

$$= \frac{1}{2} v_m i_m [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

Real part of this equation is average power.

$$P = \frac{1}{2} \operatorname{Re} [V I^*]$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

When $\theta_v = \theta_i$

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R = \frac{1}{2} |I|^2 R$$

(Shows the circuit is purely resistive)

When $\theta_v - \theta_i = 90^\circ$

$$P = \frac{1}{2} V_m I_m \cos 90^\circ = 0$$

Shows that the circuit is purely reactive.
Circuit absorbs no average power

A resistive load (R) absorbs power at all times,
while a reactive load (L or C) absorbs zero
average power

① Problem

Given that $v(t) = 120 \cos(377t + 45^\circ) \text{ V}$

$$i(t) = 10 \cos(377t - 10^\circ) \text{ A}$$

Find the instantaneous power & average power absorbed by the passive linear ntk.

Instantaneous power

$$P = v i = 1200 \cos(377t + 45^\circ) \cos(377t - 10^\circ)$$

$$P(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$\text{Average power} = \frac{1}{2} [V_m I_m \cos(\theta_v - \theta_i)]$$

$$= 600 [\cos(754t + 35^\circ) + \cos(754t - 55^\circ)]$$

$$P(t) = 344.2 + 600 \cos(754t + 35^\circ) \text{ W}$$

average power P_{avg}

$$P_{\text{avg}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} (1200) 10 \cos(45^\circ - (-10^\circ))$$

$$= 600 \cos 55^\circ = \underline{\underline{344.2 \text{ W}}}$$

- ② Calculate the instantaneous power & average power absorbed by the passive linear ntk.

$$v(t) = 80 \cos(10t + 20^\circ) \text{ V}$$

$$i(t) = 15 \sin(10t + 60^\circ) \text{ A}$$

$i(t)$ can be written as

$$\dot{i}(t) = 15 \cos(10t + 60^\circ - 90^\circ) \text{ V}$$

$$\dot{i}(t) = 15 \cos(10t - 30^\circ) \text{ V}$$

$$p(t) = \frac{1}{2} v_m i_m \cos(\theta_v - \theta_i) + \frac{1}{2} v_m i_m \cos(2\omega t + \theta_v + \theta_i)$$

$$= \frac{1}{2} 80 \times 15 \cos(20 - (-30)) + \frac{1}{2} 80 \times 15 \cos(2 \times 10t + 20 - 30)$$

$$= 600 \cos(50^\circ) + \frac{1}{2} 600 \cos(20t - 10^\circ)$$

$$P(t) = 385.7 + 600 \cos(20t - 10^\circ) \text{ W}$$

Average Power P_{avg}

$$P_{avg} = \frac{1}{2} v_m i_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \times 80 \times 15 \cos(20 - (-30))$$

$$= 600 \cos(50^\circ)$$

$$P_{avg} = 385.7 \text{ W}$$

- ③ Calculate the average power absorbed by an impedance $Z = 30 - j70 \Omega$ when a voltage $v = 120 \angle 0^\circ$ is applied across it.

$$I = \frac{V}{Z} = \frac{120 \angle 0^\circ}{30 - j70} = \frac{120 \angle 0^\circ}{76.16 \angle -66.8^\circ} = 1.576 \angle 66.8^\circ \text{ A}$$

$$P_{avg} = \frac{1}{2} v_m i_m \cos(\theta_v - \theta_i) = \frac{1}{2} (120)(1.576) \cos(0 - 66.8^\circ)$$

$$P_{avg} = 37.24 \text{ W}$$

- ④ A current $I = 10 \angle 30^\circ$ flows through an impedance $Z = 20 \angle -22^\circ \Omega$, Find the average power delivered to the impedance.

$$V = I \cdot Z = 10 \angle 30^\circ \times 20 \angle -22^\circ$$

$$V = 200 \angle 8^\circ \text{ V}$$

$$P_{\text{avg}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \times 200 \times 10 \cos(8^\circ - 30^\circ)$$

$$= 1000 \cos(-22^\circ)$$

$$P_{\text{avg}} = 927.2 \text{ W}$$

- ⑤ Find the avg. Power supplied by the source & the avg power absorbed by the resistor



$$I = \frac{5 \angle 30^\circ}{4 - j2} = \frac{5 \angle 30^\circ}{4.472 \angle -26.57^\circ} = 1.118 \angle 56.57^\circ \text{ A}$$

$$P_{\text{avg}} = \frac{1}{2} (5)(1.118) \cos(30^\circ - 56.57^\circ) = 2.5 \text{ W}$$

Current through resistor is

$$I_R = I = 1.118 \angle 56.57^\circ \text{ A}$$

$$V_R = 4 I_R = 4.472 \angle 56.57^\circ \text{ V}$$


Power absorbed by resistor is

$$P = \frac{1}{2} (4.472)(1.118) = 2.5 \text{ W}$$

(Since phase diff bet voltage & current is zero)

$$(\theta_v - \theta_i = 0)$$

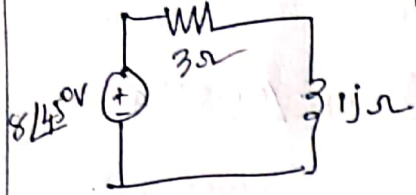which is the same as the average power delivered by the source. The zero average power is absorbed by the capacitor.



Calculate the power (avg) absorbed by the resistor & inductor. Find the avg power supplied by voltage source.

$$I = \frac{8\angle 45^\circ V}{3 + j1} = \frac{8\angle 45^\circ}{3.16\angle 18.43^\circ} = 2.53\angle 26.57^\circ A$$

Power by supply

$$P_{avg} = \frac{1}{2} \times 8 \times 2.53 \cos(45^\circ - 26.57^\circ)$$

$$P_{avg(supply)} = 9.6W$$

Current through Resistor

$$I = \frac{8\angle 45^\circ}{3} = 2.66\angle 45^\circ A$$

$$V = (2.66\angle 45^\circ) \times 3 =$$

$$P_{avg(res)} = \frac{1}{2} \times 8 \times 2.66 \cos(45^\circ - 45^\circ)$$

Current through resistor. $I = 2.53\angle 26.57^\circ A$

Voltage in resistor $(2.53\angle 26.57^\circ \times 3) = 7.59\angle 26.57^\circ$

$$P_{in resistor} = \frac{1}{2} \times 8 \times 2.53 \cos(26.57^\circ - 26.57^\circ)$$


$$= \frac{1}{2} \times 8 \times 2.53$$

$$P_{avg res.} = 9.6W$$

absorbed by

Power in Inductor is zero.

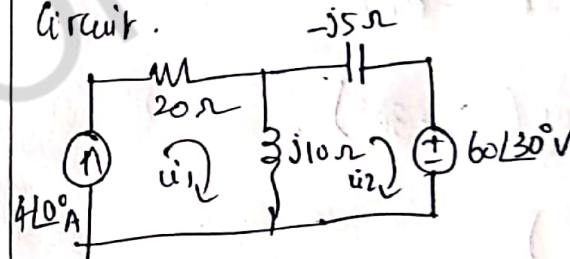③ Determine the average power generated by each source and the power absorbed by each passive elements of the circuit.



apply mesh/loop 1 $i_1 = 4A$

From mesh/loop 2

$$(j10 - j5)I_2 - j10I_1 + 60\angle 30^\circ = 0$$

$$j5I_2 = -60\angle 30^\circ + j40 \Rightarrow I_2 = -12\angle -60^\circ + 8$$

$$= 10.58\angle 79.1^\circ A$$

For the voltage source, the current flowing from it is I_2

$$I_2 = 10.58 \angle 79.1^\circ \text{ A}$$

& voltage is $60 \angle 30^\circ \text{ V}$ so avg power is

$$P_5 = \frac{1}{2} (60)(10.58) \cos(30^\circ - 79.1^\circ) = \underline{\underline{207.8 \text{ W}}}$$

This avg power is absorbed by the source, in view of the direction of I_2 & polarity of the voltage source the ckt is delivering average power to the voltage source.

for the current source: $I_1 = 4 \angle 0^\circ$

$$\begin{aligned} V_1 &= 20 I_1 + j10 (I_1 - I_2) = 80 + j10(4 - 2 - j10.39) \\ &= 183.9 + j20 \\ &= 184.984 \angle 6.21^\circ \text{ V} \end{aligned}$$

The avg power supplied by the current source is

$$P_1 = -\frac{1}{2} (184.984)(4) \cos(6.21^\circ - 0) = \underline{\underline{-367.8 \text{ W}}}$$

Negative sign indicates the current source is supplying power to the circuit.

For the resistor, the current through it is $I_1 = 4 \angle 0^\circ$

Voltage across it is $20 I_1 = 80 \angle 0^\circ$;

$$P_2 = \frac{1}{2} (80)(4) = \underline{\underline{160 \text{ W}}}$$

For the capacitor, the current through it is $I_2 = 10.58 \angle 79.1^\circ$

& the voltage across it is $-j5 I_2 = (5 \angle -90^\circ)(10.58 \angle 79.1^\circ) = 52.9 \angle 79.1^\circ - 90^\circ$

avg power absorbed by capacitor is

$$P_4 = \frac{1}{2} (52.9)(10.58) \cos(-90^\circ) = 0$$

Inductor, current is $(I_1 - I_2) = 2 - j10.39 = 10.58 \angle -79.1^\circ$

EC 3251 Circuit Analysis

Voltage across it is $10(I_1 - I_2) = 10.58 \angle -91.1 + 90^\circ$

Hence the average power absorbed by the inductor is

$$P_3 = \frac{1}{2} (10.58)(10.58) \cos 90^\circ = 0$$

Notice that the inductor & the capacitor absorb zero average power and that the total power supplied by the current source equals the power absorbed by the resistor & the voltage source, or

$$P_1 + P_2 + P_3 + P_4 + P_5 = -36 \angle -8 + 160 + 0 + 0 + 20 \angle 8 = 0$$

indicating that power is conserved.

Effective or Rms value:

The effective value of a periodic current is the dc current that delivers the same average power to a resistor as the periodic current.

$$I_{eff} = I_{rms}$$

$$V_{eff} = V_{rms}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

average power can be written in terms of rms values

$$P = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

Apparent Power & Power Factor:-

Apparent power (in VA) is the product of the rms values of voltage and current.

$$\text{units (volt-Amp)}$$

Power factor:- Ratio of average power to apparent power

$$P_f = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

$\theta_v - \theta_i =$ Power factor angle.

Power factor is the cosine of the phase difference between voltage & current. It is also the cosine of the angle ϕ of load.

- ① A Series-connected load draws a current $i(t) = 4 \cos(100\pi t + 10^\circ) \text{ A}$ when the applied voltage is $v(t) = 120 \cos(100\pi t - 20^\circ) \text{ V}$, find the apparent power & the power factor of the load, determine the element values that form the series-connected load.

$$\text{Apparent power } S = V_{\text{rms}} I_{\text{rms}} = \frac{120}{\sqrt{2}} \frac{4}{\sqrt{2}} = \underline{\underline{240 \text{ VA}}}$$

$$\text{Power factor } PF = \cos(\theta_v - \theta_i) = \cos(-20 - 10) = 0.866 \text{ (leading)}$$

(Because current leads voltage)

$$Z = \frac{V}{I} = \frac{120 \angle -20^\circ}{4 \angle 10^\circ} = 25.98 - j15 \Omega$$

$$PF = \cos(-30^\circ) = 0.866 \text{ (leading)}$$

load impedance 'Z' can be modeled by a

25.98 Ω resistor in series with a capacitor

$$X_C = -15 = -1/\omega C$$

$$C = 1/15\omega = 1/15 \times 100\pi = 2122 \mu\text{F}$$

- ② Obtain power factor & the apparent power of a load whose impedance is $Z = 60 + j40 \Omega$ $V(t) = 150 \cos(377t + 10^\circ) \text{ V}$

Apparent power $S = V_{\text{rms}} I_{\text{rms}}$:

$$I(t) = \frac{V(t)}{Z} = \frac{150 \angle 10^\circ}{60 + j40} = \frac{150 \angle 10^\circ}{72.11 \angle 33.69^\circ}$$

$$I(t) = 2.08 \angle -23.69^\circ$$

$$S = V_{\text{rms}} I_{\text{rms}} = \frac{150}{\sqrt{2}} \times \frac{2.08}{\sqrt{2}} = \underline{\underline{156 \text{ VA}}}$$

$$PF = \cos(\theta_v - \theta_i) =$$

$$= \cos(10 + 23.69) = 0.832 \text{ (lagging)}$$

(Because current lags voltage)

Complex power: in (VA)

is the product of the rms voltage phasor and the complex conjugate of the rms current phasor. As a complex quantity its real part is real power (P) & its imaginary part is reactive power Q.

$$\text{Complex power} = S = P + jQ = \frac{1}{2} V I^*$$

$$= V_{\text{rms}} I_{\text{rms}} \angle \theta_v - \theta_i$$

$$\text{Apparent power } S = |S| = V_{\text{rms}} I_{\text{rms}} = \sqrt{P^2 + Q^2}$$

$$\text{Real power} = P = \text{Re}(S) = S \cos(\theta_v - \theta_i)$$

$$\text{Reactive power} = Q = \text{Im}(S) = S \sin(\theta_v - \theta_i)$$

$$\text{Power factor} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

Problem:

(1) The voltage across a load is $v(t) = 60 \cos(\omega t - 10^\circ)$ V and the current through the element in the direction of the voltage drop is $i(t) = 1.5 \cos(\omega t + 50^\circ)$ A.

- Find (a) complex & apparent powers
(b) real & reactive power
(c) power factor & the load impedance.

(a)

$$V_{\text{rms}} = \frac{60}{\sqrt{2}} \angle -10^\circ \quad I_{\text{rms}} = \frac{1.5}{\sqrt{2}} \angle 50^\circ$$

$$\text{Complex power} = V_{\text{rms}} I_{\text{rms}}^* \left(\frac{60}{\sqrt{2}} \angle -10^\circ \right) \left(\frac{1.5}{\sqrt{2}} \angle -50^\circ \right)^*$$

$$\text{Complex power} = 45 \angle -60^\circ \text{ VA}$$

Apparent power

$$S = |S| = 45 \text{ VA}$$

b) we can express the complex power in rectangular form

$$S = 45 \angle -60^\circ = 45 [\cos(-60) + j \sin(-60^\circ)] \\ = 22.5 - j38.97$$

Since $S = P + jQ$, the real power is

$$\text{Real power } P = 22.5 \text{ W}$$

while reactive power is

$$Q = -38.97 \text{ VAR}$$

c) The power factor

$$\text{Pf} = \cos(-60^\circ) = 0.5 \text{ (leading)}$$

$$Z = \frac{V}{I} = \frac{60 \angle -10^\circ}{1.5 \angle +50^\circ} = 40 \angle -60^\circ \Omega$$

② for a load $V_{\text{rms}} = 110 \angle 85^\circ \text{ V}$, $I_{\text{rms}} = 0.4 \angle 15^\circ \text{ A}$

Determine complex power, apparent power, Real Power, reactive power, Power factor & load Impedance.

Complex power

$$S = V_{\text{rms}} I_{\text{rms}}^*$$

$$S = \frac{110}{\cancel{100}} \angle 85^\circ \times \frac{0.4}{\cancel{100}} \angle -15^\circ$$

$$S = 44 \angle 70^\circ \text{ VA}$$

Apparent power:

$$|S| = 44 \text{ VA}$$

Real power

Complex power in rectangular form

$$15.04 + j41.3 \text{ W}$$

$$S = P + jQ$$

Real power $P = 15.04 \text{ W}$

Reactive power $Q = 41.3 \text{ VAR}$

Power factor

$$\begin{aligned} \text{PF} &= \cos(\theta_v - \theta_i) \quad \text{or} \quad \text{PF} = \cos(\theta) \\ &= \cos(85 - 15) \quad \text{From complex power} \\ &= \cos(70^\circ) \quad \text{power} \end{aligned}$$

$$\text{PF} = 0.342 \text{ lagging!}$$

Impedance

$$\begin{aligned} Z &= \frac{V}{I} = \frac{V_{\text{rms}} \angle \theta_v}{I_{\text{rms}} \angle \theta_i} = \frac{110 \angle 85^\circ}{0.4 \angle 15^\circ} \\ &= 275 \angle 70^\circ \Omega \end{aligned}$$

$$Z = 94.05 + j258.4 \Omega$$

② for a load, $V_{\text{rms}} = 110 \angle 85^\circ \text{ V}$, $I_{\text{rms}} = 0.4$

③ A load Z draws 12 kVA at a P.F. of 0.856 lagging from a 120 V rms sinusoidal source. Calculate the average & reactive power delivered to the load,

(b) Peak current and the (c) load impedance.

Given that $\text{PF} = \cos \theta = 0.856$, we obtain the power angle as $\theta = \cos^{-1} 0.856 = 31.13^\circ$

If apparent power is $S = 12000 \text{ VA}$ the average or real power is

$$P = S \cos \theta = 12000 \times 0.856 = 10.272 \text{ kW}$$

while the reactive power is

$$Q = S \sin \theta = 12000 \times 0.517 = 6.204 \text{ kVAR}$$

(b) Since the PF is lagging, the complex power is

$$S = P + jQ = 10.272 + j6.204 \text{ kVA}$$

From $S = V_{rms} I_{rms}^*$

$$I_{rms}^* = \frac{S}{V_{rms}} = \frac{100 \angle 10.272 + j6204}{120 \angle 0^\circ}$$

$$= 85.6 + j51.7 A$$

$$= \underline{\underline{100 \angle 31.13^\circ A}}$$

Thus $I_{rms} = 100 \angle -31.13^\circ$ & the Peak current is

$$I_m = \sqrt{2} I_{rms} = \sqrt{2} \times 100 = \underline{\underline{141.4 A}}$$

The load Impedance

$$Z = \frac{V_{rms}}{I_{rms}} = \frac{120 \angle 0^\circ}{100 \angle -31.13^\circ} = \underline{\underline{1.2 \angle 31.13^\circ \Omega}}$$

which is an inductive Impedance.

TRANSIENTS AND RESONANCE IN RLC CIRCUIT

Here we shall examine two types of

Simple Circuits:

- A Circuit comprising a resistor and capacitor
- and a circuit comprising a resistor and an


Inductor.

These are called RC and RL.

The Source-free RC Circuit:

* A source-free RC circuit occurs when its DC source is suddenly disconnected. The energy already stored in the capacitor is released to the resistors.

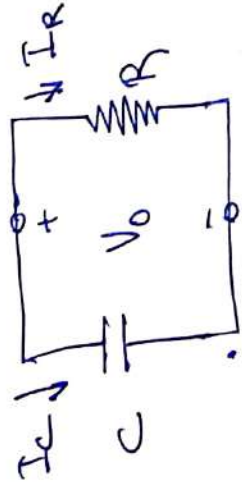- Consider a series combination of a resistor and an initially charged capacitor.



- Objective is to determine the circuit response, assume to be the voltage

$V(t)$ across the capacitor.

Since capacitor initially charged, we can assume that at time $t=0$, the initial voltage is V_0 .

Value of energy stored

$$w(t) = \frac{1}{2} C V^2$$

Applying KCL at the node of the circuit,

$$i_C + i_R = 0$$

$$\text{Where } i_C = C \frac{dv}{dt} \text{ and } i_R = \frac{v}{R}$$

$$C \frac{dv}{dt} + \frac{v}{R} = 0$$

by rearranging

$$\frac{dv}{v} = - \frac{1}{RC} dt$$

Integrating both sides,

$$\ln v = - \frac{t}{RC} + \ln A$$

A \rightarrow integration constant, thus,

$$\frac{\ln v}{\ln A} = - \frac{t}{RC}$$

Taking Powers of e produce


$$\frac{v}{A} = e^{-t/RC}$$

$$\therefore v(t) = A e^{-t/RC}$$

at initial condition $v(0) = A = V_0$

$$v(t) = V_0 e^{-t/RC}$$

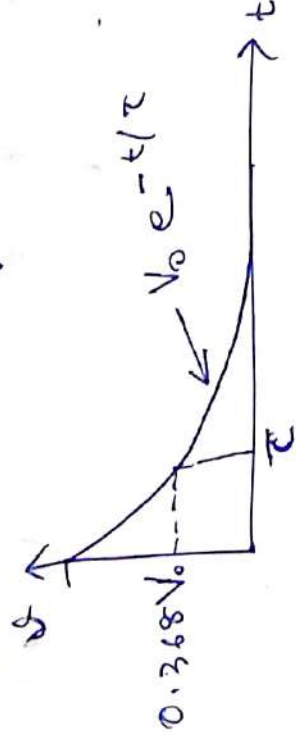This shows the Voltage Response of the RC circuit is an exponential decay of the initial voltage.



The Response is due to the initial energy stored in the physical characteristics of the circuit and not due to some external voltage or current source, it is called the natural response of the circuit.

From the graph, As t increases the voltage decreases toward zero. The rapidity with which the voltage decreases is expressed in terms of the time constant (τ).

that, $t = \tau$

$$V(t) = V_0 e^{-t/RC}$$


where $\tau = RC$

$$V(t) = V_0 e^{-t/\tau} = V_0 e^{-1}$$

$$= 0.368 V_0$$

In terms of time constant


$$V(t) = V_0 e^{-t/\tau}$$

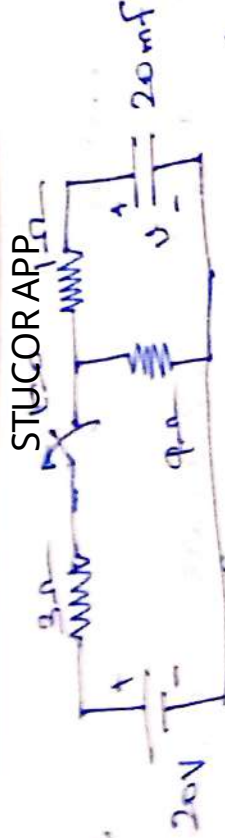

The Switch in the circuit has been closed for a long time, and it's opened at $t=0$. Find $v_C(t)$ for $t \geq 0$. Calculate the initial energy stored in the capacitor.

Solution:

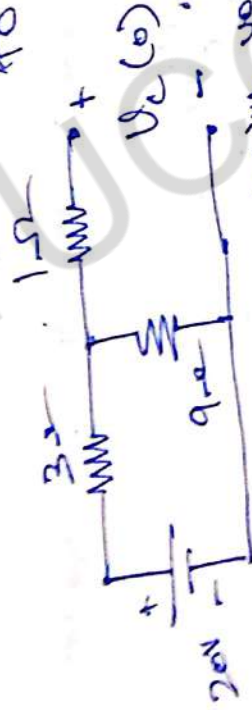for $t < 0 \rightarrow$ Switch closed, the capacitor is an open circuit, AC DC.




using voltage division Rule

$$v_C(t) = 20 \times \frac{9}{9+3} = 15 \text{ V } t < 0$$

Voltage across a capacitor cannot change instantaneously, the voltage across the capacitor at $t=0^-$ is same at $t=0$.

$$v_C(0) = V_0 = 15 \text{ V.}$$

for $t > 0$, the switch is opened,

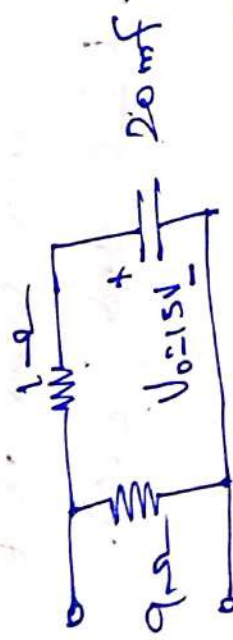

Source free RC circuit.

time constant,

$$\tau = R_{eq} C = 10 \times 20 \times 10^{-3} = 0.2 \text{ s}$$

The voltage across the capacitor

for $t \geq 0$ is


$$V(t) = V_c(0) e^{-t/\tau} \\ = 15 e^{-t/0.2} \text{ V}$$

$$V(t) = 15 e^{-5t} \text{ V}$$

Initial energy stored in the capacitor is

$$W_c(0) = \frac{1}{2} C V_c^2(0) \\ = \frac{1}{2} \times 20 \times 10^{-3} \times 15^2$$

$$W_c(0) = 2.25 \text{ J}$$

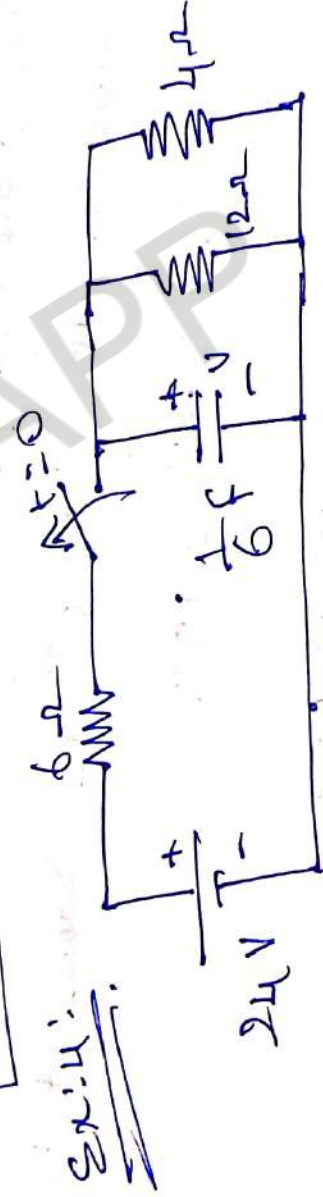


If the switch opens at $t=0$, find

$V(t)$ for $t \geq 0$ and $W_c(0)$.

Solution:

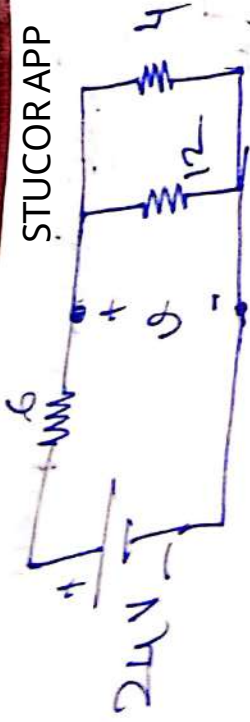for $t < 0 \rightarrow$ Switch Closed
Capacitor at Open
Circuited.




$$24V \text{ source} \Rightarrow \frac{24 \times 3}{6+3} = 8V$$

$$V_c(t) = 8V \quad t < 0$$

for $t \geq 0$ Switch Opens

$$V_c(0) = V_0 = 8V$$

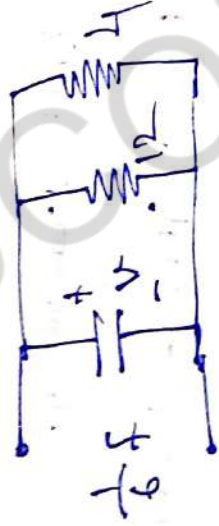

$$\tau = RC = 3 \times \frac{1}{6} = 0.5s$$

Voltage across capacitor $t \geq 0$


$$V_c(t) = V_c(0) e^{-t/0.5}$$

$$V_c(t) = 8 e^{-2t} V$$

$$V_c(0) = \frac{1}{2} e V_c^2(0) = \frac{1}{2} \times \frac{1}{6} \times 8^2$$

$$= 5.33J$$

THE SOURCE STUCCORAPP R L C CIRCUIT

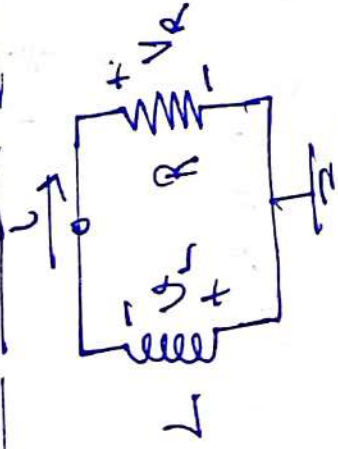

Our goal to determine the circuit

Response.

We select the inductor current as the response in order to take advantage of the idea that the inductor current cannot change instantaneously.

Assume at $t=0$ the inductor has initial current I_0 ,

$$i(0) = I_0.$$

The complementary energy stored in the inductor,

$$w(0) = \frac{1}{2} L I_0^2.$$

Apply KVL around the loop,

$$V_L + V_R = 0$$

but, $V_L = L \frac{di}{dt}$ & $V_R = iR$, thus

$$L \frac{di}{dt} + Ri = 0$$

for Simplification, divide by 'L'

$$\frac{di}{dt} + \frac{R}{L} i = 0$$

Rearranging terms and integrating gives

$$\int_{I_0}^{i(t)} \frac{di}{i} = - \int_0^t \frac{R}{L} dt$$

$$\ln i \Big|_{I_0}^{i(t)} = - \frac{Rt}{L} \Big|_0^t$$

$$\ln i(t) - \ln I_0 = - \frac{Rt}{L} + 0$$

$$\ln \frac{i(t)}{I_0} = - \frac{Rt}{L}$$

Taking e power


$$-Rt/L$$

$$i(t) = I_0 e^{-Rt/L}$$

This shows that the natural response of the RL circuit is an exponential decay of the initial current.

$i(t)$ \uparrow I_0 time constant for RL

$$0.368 I_0 \quad \tau = \frac{L}{R}$$

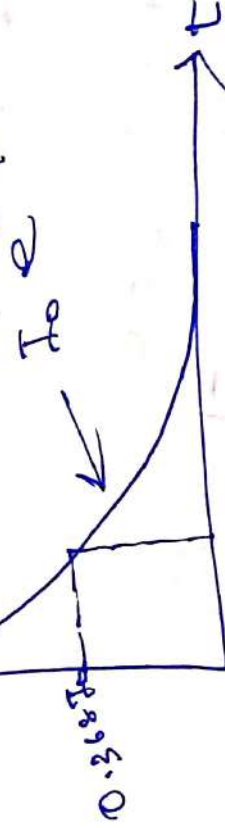

$$i(t) = I_0 e^{-t/\tau}$$

then we can find voltage across the resistors as

$$V_R(t) = iR = I_0 R e^{-t/\tau}$$


Power dissipate in the resistor

$$P = V_R i = I_0^2 R e^{-2t/\tau}$$

$$\begin{aligned} &= I_0 R e^{-t/\tau} \times I_0 e^{-t/\tau} \\ &= I_0^2 R e^{-2t/\tau} \end{aligned}$$

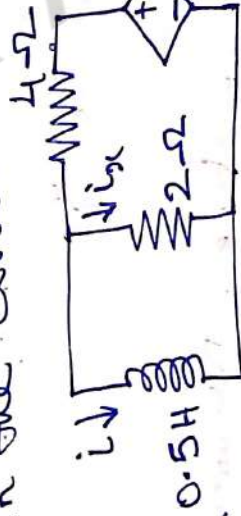
Problem:

Assuming that $i(0) = 10 \text{ A}$, calculate $i(t)$ and $i_R(t)$ in the circuit.



Solution:

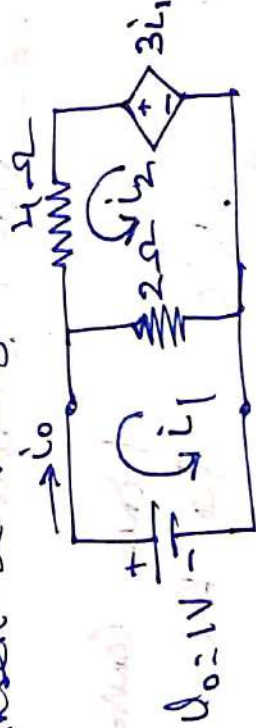Because of the dependent source, we insert a voltage source with $V_0 = 1 \text{ V}$,



Apply KVL

$$1 + 2(i_1 - i_2) = 0$$

$$4i_2 + 2(i_2 - i_1) = 0$$

$$4i_2 + 2i_2 - 2i_1 - 2i_2 = 0$$

$$6i_2 - 2i_1 = 0 \quad \text{--- (1)}$$

$$i_2 = \frac{1}{3}i_1$$

Sub i_2 in (1)

$$2i_1 - 2\left(\frac{1}{3}i_1\right) = -1$$

$$i_1 \left[2 - \frac{2}{3} \right] + 1 = 0$$

$$i_1 \left[\frac{4}{3} \right] + 1 = 0$$

$$i_1 = -\frac{3}{4} = -0.75 \text{ A}$$

$$\therefore i_0 = -i_1 = -(-0.75) = 0.75 \text{ A}$$

$$\therefore R_{eq} = R_{in} = \frac{V_0}{I_0} = \frac{1}{0.75} = 1.33 \Omega$$

then the time constant is

$$\tau = \frac{L}{R_{eq}} = \frac{0.5}{1.33} = 0.375 \text{ s}$$

the current through the inductor is

$$i(t) = i(0) e^{-t/\tau} = 10 e^{-t/0.375} \text{ A } t > 0$$

Voltage across the inductor is

$$v = L \frac{di}{dt} = 0.5 \frac{d(10 e^{-t/0.375})}{dt}$$

$$= (0.5)(10) \left(-\frac{1}{0.375}\right) e^{-t/0.375}$$

$$= -13.33 e^{-t/0.375} \text{ V}$$


Since inductor STUCORAPP Ω resistor are in

Parallel,

$$i_x(t) = \frac{V}{2} = \frac{-3.33 e^{-t/1.5}}{2} = -1.666 e^{-t/1.5} \text{ A} \quad t > 0.$$

Ex 2: find i and V_x in the circuit in

figure 1 Let $i(0) = 5 \text{ A}$

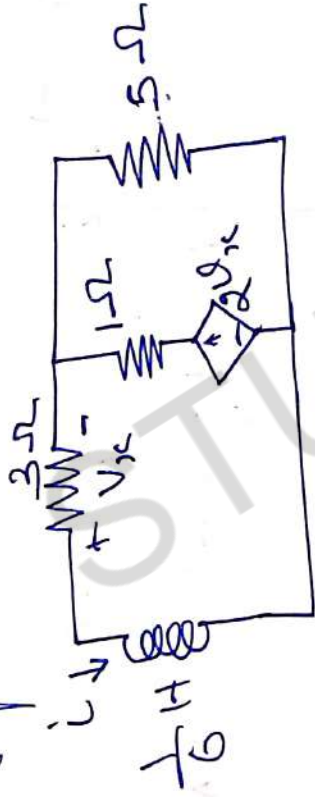


Solution:

Given: $i(0) = 5$

find: i and V_x

first find Req

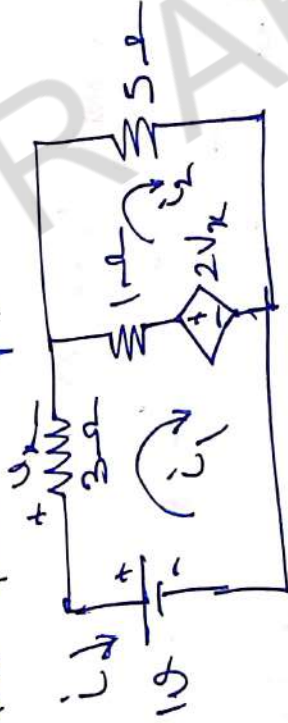

Apply KVL

$$-1 + 3i_1 + 1(i_1 + i_2) + 2V_x = 0$$

$$4i_1 - i_2 + 2(3i_1) = 0 \quad \text{--- 1}$$

$$10i_1 - i_2 = +1 \quad \text{--- 2}$$

Loop 2

$$1[i_2 - i_1] + 5i_2 - 2V_x = 0$$

$$i_2 - i_1 + 5i_2 - 2(3i_1) = 0$$

$$6i_2 - 7i_1 = 0$$

10 $\dot{i}_1 - \dot{i}_2 = 4$ STUCORAPP

$$-7\dot{i}_1 + 6\dot{i}_2 = 0$$

$$\Delta = \begin{vmatrix} 10 & -1 \\ -7 & 6 \end{vmatrix} = 60 - 7 = 53$$

$$\Delta_1 = \begin{vmatrix} 1 & -1 \\ 0 & 6 \end{vmatrix} = +6$$

$$\dot{i}_1 = \frac{+6}{53} = +0.113$$

$$R_{eq} = R_{th} = \frac{V_o}{I_o} = \frac{1}{+0.113} = 8.8 \Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{1/6}{8.8} = 0.0189 \text{ s}$$

$$i(t) = i(0) e^{-t/\tau}$$


$$i(t) = 5 e^{-t/0.0189} = 5 e^{-53t} \text{ A}$$

$$V_x = 3 \times i(t)$$

$$= 3 \times [-5 e^{-53t}]$$



$$V_x = -15 e^{-53t} \text{ V}$$

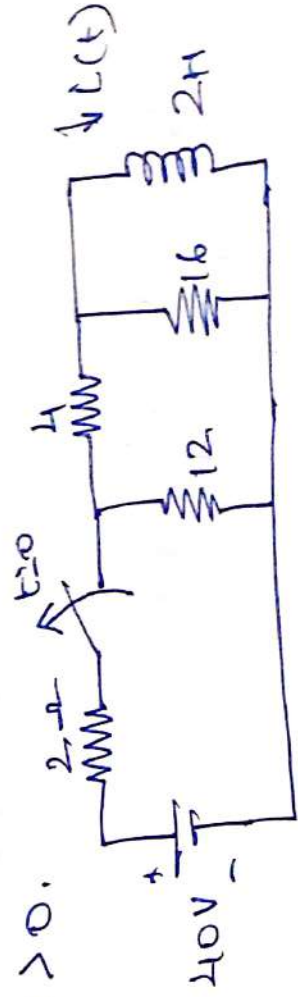Ex 3: The Switch in the circuit has been closed for a long time. At $t=0$ the switch is opened. Calculate $i(t)$ for $t > 0$.



Solution:

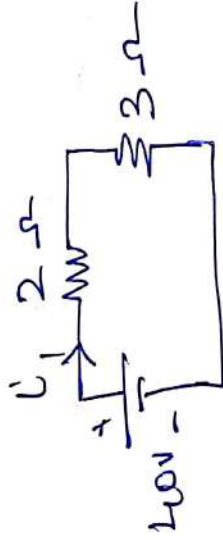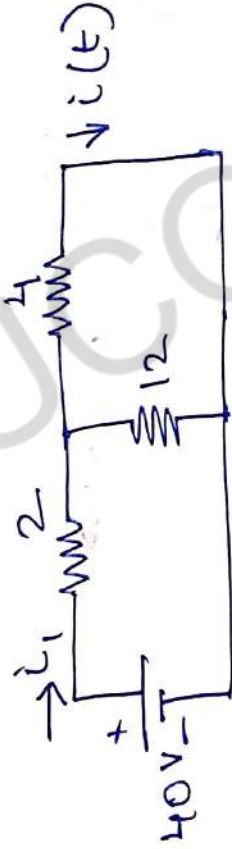at $t < 0 \rightarrow$ Switch closed, Inductor acts as Short circuit.
 \rightarrow 16 ohm Resistor is Short Circuited.



$$i_1 = \frac{40}{5} = 8 \text{ A}$$

and $i(t)$ obtain by Current Division rule

$$i(t) = 8 \times \frac{12}{12+4} = 6 \text{ A} \quad t < 0$$


Since Current through an inductor cannot change instantaneously.

$$i(0^-) = i(0^+) = 6 \text{ A} \quad \text{at } t=0$$

When $t > 0 \rightarrow$ Switch Opened,

Voltage source dis Connected.

Source free RL circuit

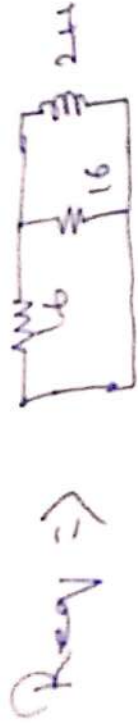

$$= \frac{16 \times 16}{16 + 16} = 8 \Omega$$

\therefore time constant


$$\tau = \frac{L}{R_{eq}} = \frac{2}{8} = \frac{1}{4} \text{ s}$$

Thus

$$i(t) = i(0) e^{-t/\tau} \quad t > 0$$


$$i(t) = 6 e^{-4t} \text{ A} \quad t > 0$$

Ex: 4

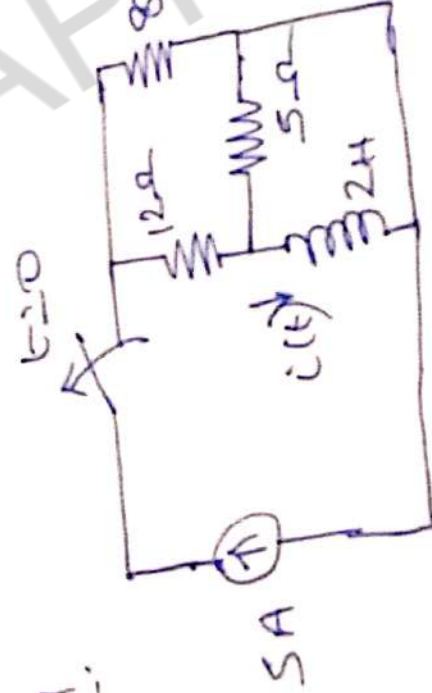


Ans: $i(t) = 2 e^{-2t} \text{ A}$

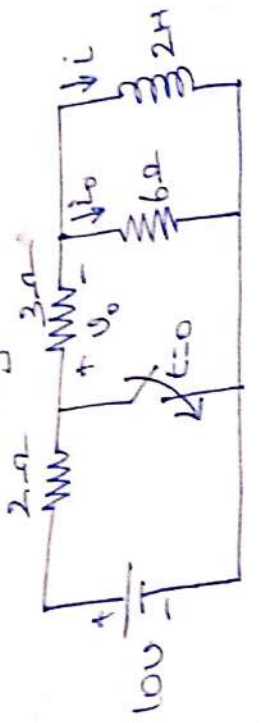Ex 7.5 In the circuit below, find i_0 , v_0 & v_0 & i_0 for all time, assuming that the switch opens for a long time.



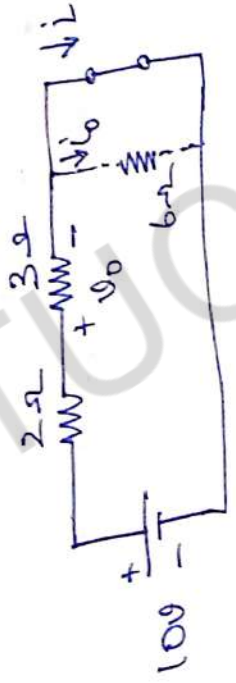Solution: \Rightarrow For $t < 0 \rightarrow$ Switch is open, then DC source connected to Inductor, so it behaves like short circuit.




$i_0 = 0; t < 0$

$i = \frac{100}{3+2} = 2 \text{ A}; t < 0$

$v_0 = i \times 3 = 2 \times 3 = 6 \text{ V}; t < 0$

then $i(0) = 2 \text{ A}$.

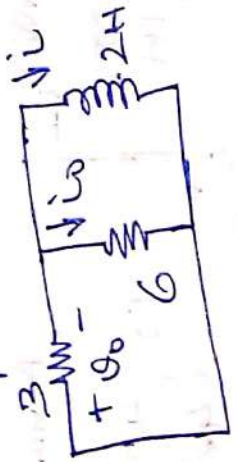\Rightarrow For $t > 0 \rightarrow$ Switch is closed, so that voltage source is short circuit.



$i(t) = i(0) e^{-t/\tau}$

$R_{eq} = \frac{3 \times 6}{3+6} = \frac{18}{9} = 2 \Omega$

$\tau = \frac{L}{R_{eq}} = \frac{2}{2} = 1 \text{ Sec}$

$$i(t) = 2e^{-t} \text{ A}$$

$$\therefore i(t) = 2e^{-t} \text{ A at } t > 0$$

Need to find i_0 i.e. current through $6\text{-}\Omega$ resistor

by Current Division Rule,

$$i_0 \text{ or } i_6 = (-2e^{-t}) \times \frac{3}{9}$$

[Note: $i(t)$ is reverse direction when current through in $6\text{-}\Omega$]

$$i_0(t) = -\frac{2}{3} e^{-t} \text{ A at } t > 0$$

$$v_0(t) = v_L = L \frac{di}{dt}$$


$$= 2 \times \frac{d(-2e^{-t})}{dt}$$

$$= 2 \times [-2(-1)e^{-t}]$$

$$= 2 \times 2e^{-t}$$

$$v_0(t) = 4e^{-t} \text{ V}$$

Ex:

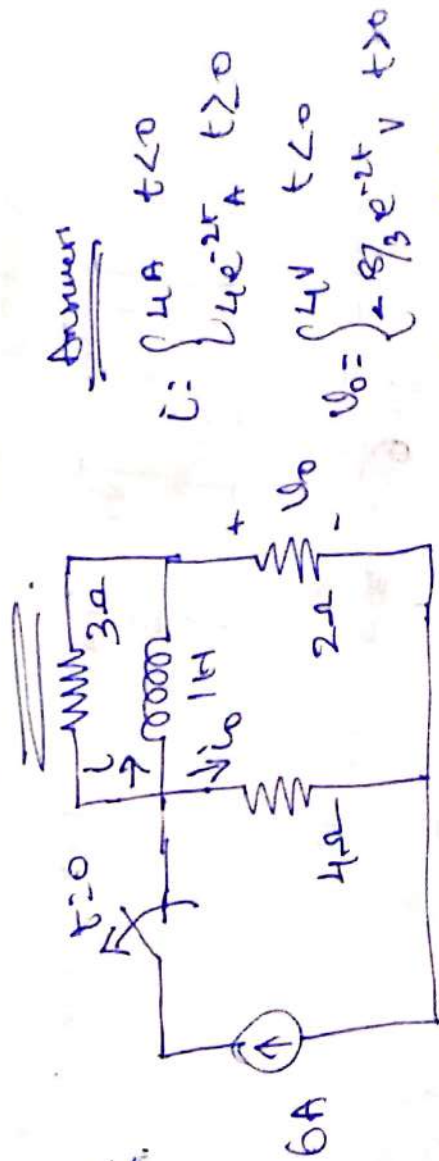

Answer

$$i = \begin{cases} 4 \text{ A} & t < 0 \\ 4e^{-2t} \text{ A} & t > 0 \end{cases}$$

$$v_0 = \begin{cases} 4 \text{ V} & t < 0 \\ \frac{8}{3} e^{-2t} \text{ V} & t > 0 \end{cases}$$

UNIT STEP FUNCTION:

The Unit Step function $u(t)$ is '0' for Negative values of 't' and '1' for positive Value of 't'.

$$\text{i.e., } u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$




The Unit Step function is Undefined at $t=0$, Where it changes abruptly from 0 to 1.

→ If the abrupt change occurs at $t = t_0$, then the Unit Step function

becomes,
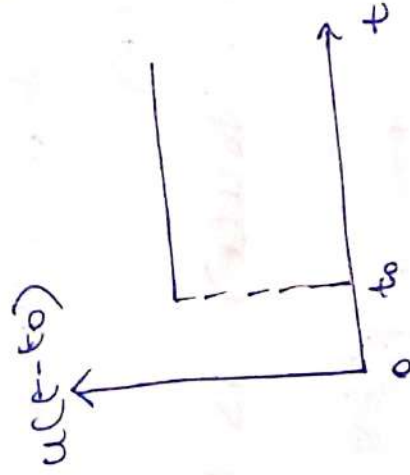
$$u(t-t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$




that $u(t)$ delayed by t_0 seconds.

→ If the change is at $t = -t_0$, then Unit Step function becomes,

STUCOR APP

$$u(t+t_0) = \begin{cases} 0, & t < -t_0 \\ 1, & t > -t_0 \end{cases}$$

i.e. $u(t)$ is advanced by t_0 seconds.

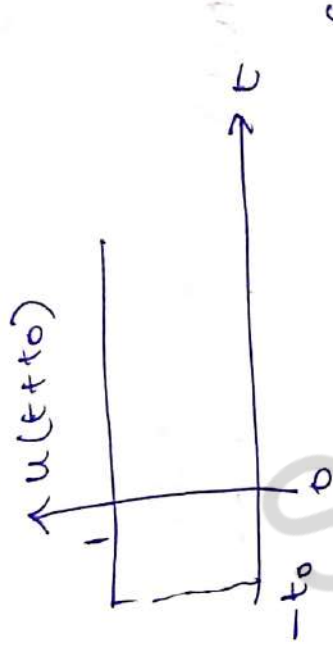

We use the step function to represent an abrupt change in voltage or current.

Example, step voltage,

$$v(t) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$


It expressed in terms of unit step function as,

$$v(t) = V_0 u(t-t_0)$$

If $t_0 = 0$, then, step voltage,


$$v(t) = V_0 u(t).$$

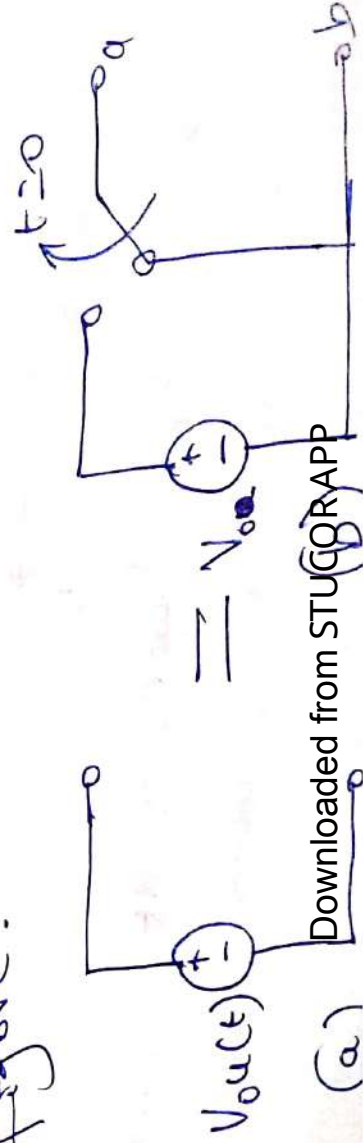A voltage source $V_0 u(t)$ is shown in figure.



from the figure (b) it is evident that terminals a-b are short circuited $v = 0$ for $t < 0$, and $v = V_0$ at terminals for $t > 0$.

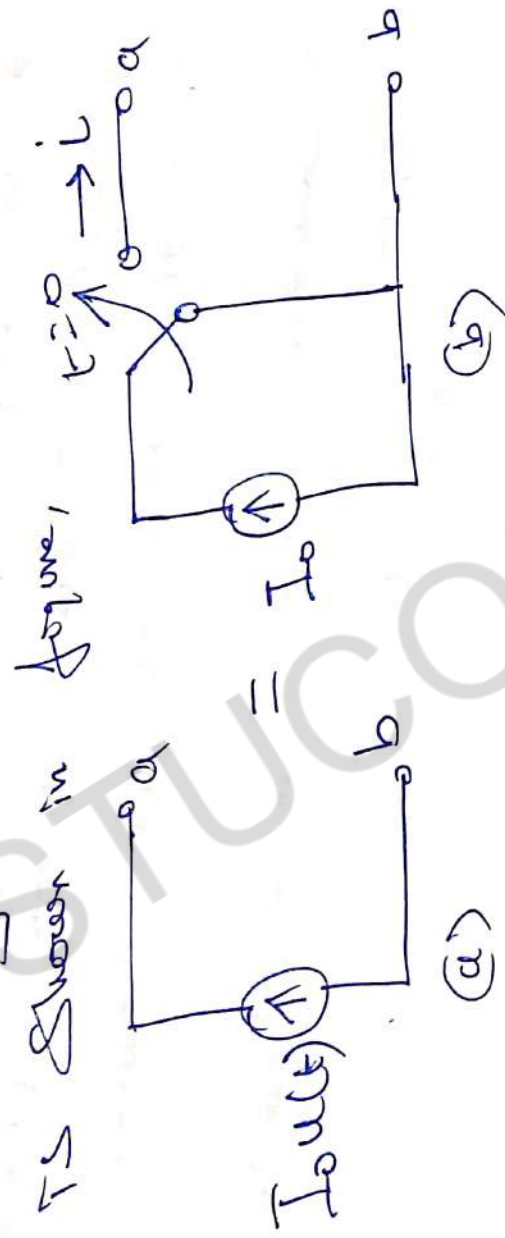Similarly, a current source of $I_0 u(t)$




from figure (b), Note that terminals a-b are open circuited $i = 0$ for $t < 0$, and $i = I_0$ flow for $t > 0$.

STEP RESPONSE OF AN RC CIRCUIT

When the dc source of an RC circuit is suddenly applied, the voltage or current source can be modeled as a step function and the response is known as a step response.


→ The step response is the response of the circuit due to sudden application of a dc voltage or current source.

→ Consider the RC circuit shown in

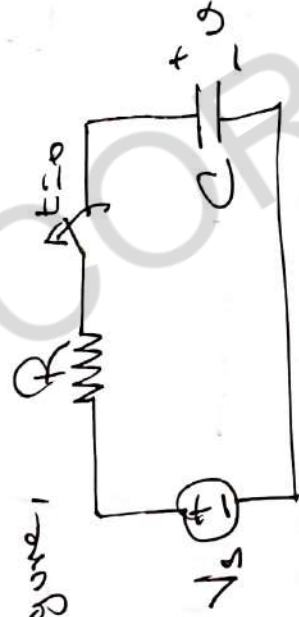

Which can be replaced by the

circuit,

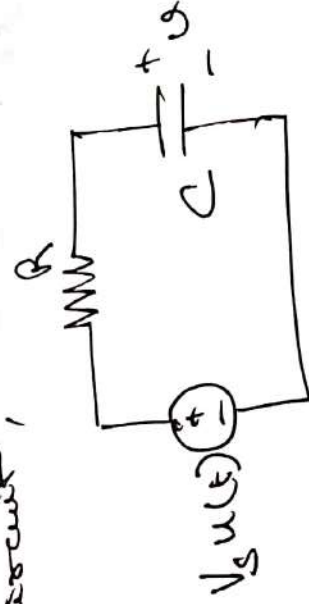

V_s → is a constant dc voltage source
Assume an initial voltage V_0 on the capacitor, the voltage on the capacitor cannot change instantaneously!

$$V(0^-) = V(0^+) = V_0$$

Apply KCL,

$$i_R + i_C = i_0$$

$$\frac{V}{R} + C \frac{dV}{dt} = \frac{V_s u(t)}{R}$$

$$\frac{V}{R} - \frac{V_s u(t)}{R} + C \frac{dV}{dt} = 0$$

$$\frac{V - V_s u(t)}{R} + C \frac{dV}{dt} = 0$$

divide by 'C'

$$\frac{V - V_s u(t)}{RC} + \frac{dV}{dt} = 0$$

$$\frac{dV}{dt} + \frac{V}{RC} = \frac{V_s u(t)}{RC}$$

where V is voltage across capacitor at $t > 0$. so $u(t) = 1$ at $t > 0$.

$$\frac{dV}{dt} + \frac{V}{RC} = \frac{V_s}{RC}$$

Rearranging terms,

$$\frac{dV}{dt} = - \frac{(V - V_s)}{RC}$$

$$\frac{dV}{V - V_s} = - \frac{dt}{RC}$$

Integrating both sides

$$\int \frac{dV}{V - V_s} = \int - \frac{dt}{RC}$$

$$\ln(V - V_s) \Big|_{V_0}^{V(t)} = -\frac{t}{RC} \Big|_0^t$$

$$\ln[V(t) - V_s] - \ln[V_0 - V_s] = -\frac{t}{RC} + 0$$

$$\ln \frac{V - V_s}{V_0 - V_s} = -\frac{t}{RC}$$

Taking exponential of both sides,

$$\frac{V - V_s}{V_0 - V_s} = e^{-t/RC}$$

$$\text{where } \tau = RC$$

$$\frac{V - V_s}{V_0 - V_s} = e^{-t/\tau}$$

$$V - V_s = (V_0 - V_s) e^{-t/\tau}$$

$$V(t) = V_s + (V_0 - V_s) e^{-t/\tau}, \quad t > 0.$$

Thus, V_0 , $t < 0$

$$V(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s) e^{-t/\tau}, & t > 0 \end{cases}$$

This is known as Complete Response of the RC circuit to a sudden application of DC voltage source. Capacitor is initially charged.

If we assume capacitor is uncharged initially $V_0 = 0$, so the equation becomes,

$$v(t) = \begin{cases} 0, & t < 0 \\ V_s (1 - e^{-t/\tau}), & t > 0 \end{cases}$$

can be written alternatively as,

$$v(t) = V_s (1 - e^{-t/\tau}) u(t)$$

This is the complete step response of the RC circuit when the capacitor is initially uncharged.

→ The current through the capacitor is obtained from above equation, by using

$$i(t) = C \frac{dv}{dt}$$

$$i(t) = C \frac{dv}{dt} = C \frac{d}{dt} V_s (1 - e^{-t/\tau}) u(t)$$

$$\tau = RC \quad t > 0, \quad u(t) = 1$$

$$i(t) = (C)(V_s) \left[-\left(-\frac{1}{\tau}\right) e^{-t/\tau} \right]$$

$$i(t) = \frac{C}{\tau} V_s e^{-t/\tau}$$

$$i(t) = \frac{V_s}{R} e^{-t/\tau} u(t)$$

Complete Response = Natural response + forced Response
 (Stored energy) (Independent Source)

Complete Response = Transient response + Steady State Response
 (Temporary part) (Permanent part)

Natural Response = Transient Response

forced Response = Steady State Response

A Complete Response may be written as,

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

$v(0) \rightarrow$ initial voltage

$v(\infty) \rightarrow$ final or Steady state value.

To find Step Response of an RC Circuit


Requires three things,

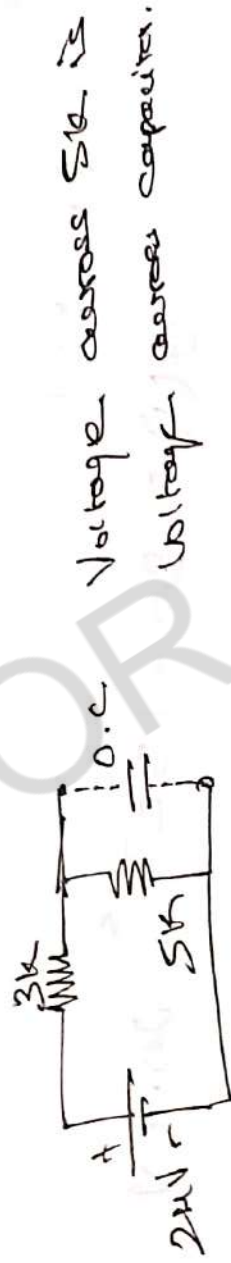1. The initial capacitor voltage $v(0) \cdot t=0$
2. The final capacitor voltage $v(\infty) \cdot t>0$
3. The time constant τ .

Ex: 1. The switch in figure has been in position A for a long time. At $t=0$, the switch moves to B. Determine $v(t)$ for $t > 0$ and calculate its value at $t=1s$ and $4s$.



Soln: For $t < 0 \rightarrow$ Switch is at position 'A', Capacitor acts like open circuit.




Using Voltage division Rule

$$v(0^-) = 24 \times \frac{5}{3+5} = 15V$$

* Actual capacitor voltage cannot change instantaneously, so

$$v(0) = v(0^-) = v(0^+) = 15V$$

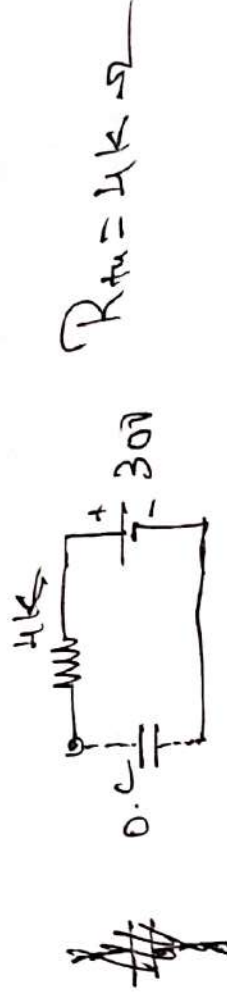* For $t > 0 \rightarrow$ Switch is in position 'B'.



$$R_{th} = 4k\Omega$$

time constant,

$$\tau = R_{th} C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2 \text{ s}$$

→ the capacitor acts like an open circuit, to DC at steady state,

$$V(\infty) = 30 \text{ V}, \quad t > 0$$

$$\begin{aligned} \text{Thus, } V(t) &= V(\infty) + [V(0) - V(\infty)] e^{-t/\tau} \\ &= 30 + [15 - 30] e^{-0.5t} \text{ V} \end{aligned}$$

$$V(t) = 30 - 15e^{-0.5t} \text{ V}$$



At $t = 1$

$$V(1) = 30 - 15e^{-0.5} = 20.9 \text{ V}$$

At $t = 4$,

$$V(4) = 30 - 15e^{-2} = 27.97 \text{ V}$$

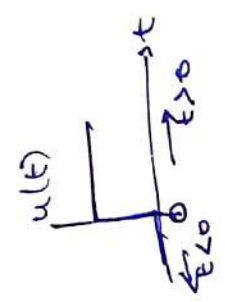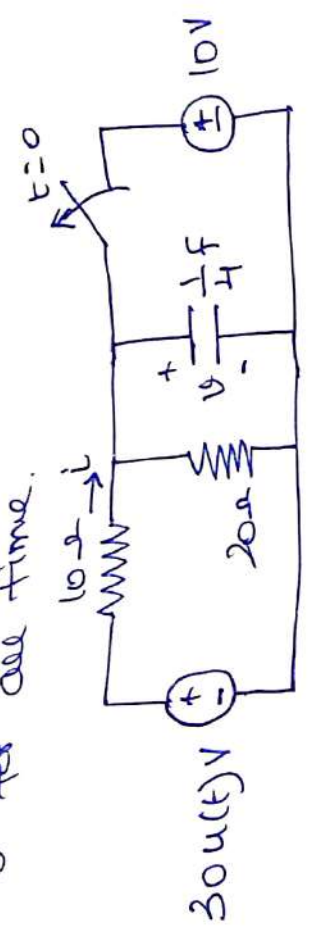Ex: 2: In figure the switch has been closed for a long time and is opened at $t=0$. Find i and v for all time.



Solution:


for $t < 0 \rightarrow$ Switch Closed

at $t < 0$ the $30\mu(t) = 0$

So 10V source connected with capacitor

It behaves Open Circuit.
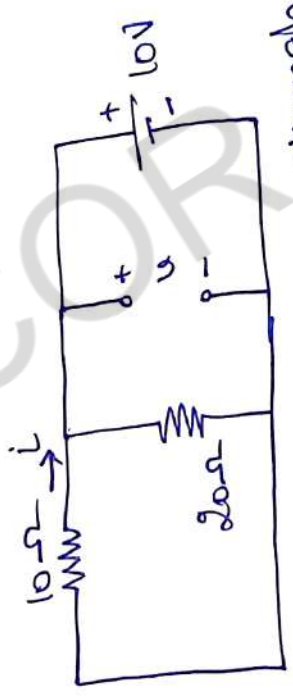
$$30\mu(t) = \begin{cases} 0 & t < 0 \\ 30 & t > 0 \end{cases}$$



No current flow through 20Ω Resistor,

$$i = -\frac{v}{10} = -\frac{10}{10} = -1A, \quad v = 10V$$


instantaneously

Capacitor voltage cannot change

$$\text{So, } v(0^-) = v(0^+) = 10V$$

Switch Opened.

for $t > 0 \rightarrow$

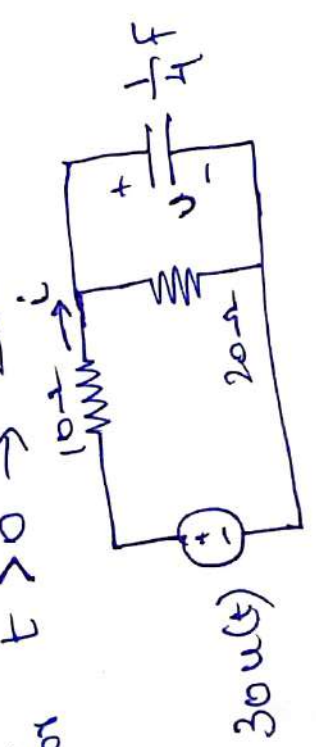

After a long time, the circuit reaches a steady state. Capacitor acts like an open circuit again.

Steady State voltage, $V(\infty)$ Obtain using Voltage division,

$$V(\infty) = 30 \times \frac{20}{20+10} = 20 \text{ V}$$

find R_{th} by,

$$R_{th} = \frac{10 \times 20}{10+20} = \frac{200}{30} = \frac{20}{3} \Omega$$

Time Constant,

$$\tau = R_{th} C = \frac{20}{3} \times \frac{1}{4} = \frac{20}{12} = \frac{5}{3} \text{ s}$$

Thus,

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau} \\ = 20 + [10 - 20] e^{-(3/5)t}$$

$$v(t) = (20 - 10 e^{-0.6t}) \text{ V}$$

To Obtain i ,

$i \rightarrow$ Sum of Current through 20Ω and Capacitor.

$$i = \frac{v}{20} + C \frac{dv}{dt}$$


$$= \frac{20 - 10 e^{-0.6t}}{20} + \frac{1}{4} \times \frac{d[20 - 10 e^{-0.6t}]}{dt}$$

$$= (1 + e^{-0.6t}) \text{ A}$$

STUCORAPP

STEP RESPONSE OF AN RL CIRCUIT

Consider the RL circuit,

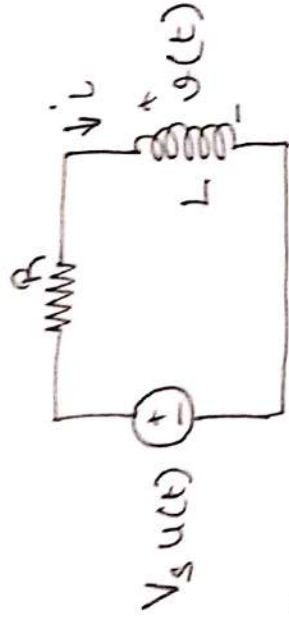

Our goal is to find the inductor current i as the circuit response.

Let the response be the sum of the natural current and the forced current.

$$i = i_n + i_f \quad \text{--- (1)}$$

↓ ↓
Natural response forced response

We know that Natural response is a decaying exponential.

$$i_n = A e^{-t/\tau} \quad \text{--- (2)}$$

A is a constant forced response is the value of the current long time after switch is closed. At the time the inductor becomes short circuit and the voltage across it is zero. The entire source voltage V_s appears across R , thus,

$$i_f = \frac{V_s}{R} \quad \text{--- (3)}$$

Sub equation (2) + (3) in (1)

$$i = A e^{-t/\tau} + \frac{V_s}{R} \quad \text{--- (4)}$$

We now determine the constant A from the value of i . Let I_0 be initial current, the current through the inductor cannot change instantaneously,

$$i(0^+) = i(0^-) = I_0 \quad (5)$$

Thus at $t=0$, then Equation (4)

$$\text{becomes, } I_0 = A + \frac{V_s}{R}$$

$$\text{then, } A = I_0 - \frac{V_s}{R}$$

'A' in equation (4)

$$i(t) = \frac{V_s}{R} + \left[I_0 - \frac{V_s}{R} \right] e^{-t/\tau} \quad (5)$$

This is the complete response of

the RL circuit.

The response in equation (5) may be

written as,

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau} \quad (6)$$

$i(0) \rightarrow$ initial value

$i(\infty) \rightarrow$ final value

To find the ^{STUCORAPP} Step response of an RL

Circuit requires three things,

1. The initial inductor current $i(0)$ at $t=0^+$
2. Final inductor current $i(\infty)$. } $t > 0$
3. The time constant τ .

If Switching takes place at time $t=t_0$

Instead of $t=0$, equation becomes,

$$i(t) = i(\infty) + [i(t_0) - i(\infty)] e^{-(t-t_0)/\tau}$$

If $I_0 = 0$, then

$$i(t) = \begin{cases} 0, & t < 0 \\ \frac{V_s}{R} (1 - e^{-t/\tau}), & t > 0 \end{cases}$$

$$\therefore i(t) = \frac{V_s}{R} (1 - e^{-t/\tau}) u(t)$$

This is the Step Response of the RL Circuit with no initial inductor current.

The voltage across the inductor is obtained

by,


$$v(t) = L \frac{di}{dt} = V_s \frac{L}{\tau R} e^{-t/\tau}$$

$$\text{where } \tau = \frac{L}{R}$$

$$\therefore v(t) = V_s e^{-t/\tau} u(t)$$

Ex 1: Find $i(t)$ in the circuit for $t > 0$.

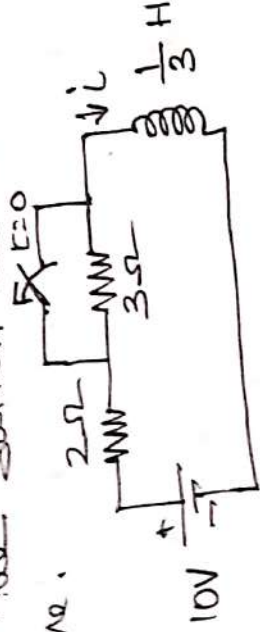Assume that the switch has been closed for a long time.



Solution:

→ For $t < 0$, → the switch is closed position,

So the 3-Ω Resistor is short-circuited, &

Inductor acts like a short circuit.

The current through the inductor at $t = 0^-$

$$i(0^-) = \frac{10}{2} = 5 \text{ A}$$

Since the inductor current cannot change instantaneously,

$$i(0) = i(0^-) = i(0^+) = 5 \text{ A.}$$

→ for $t > 0$, the switch is open,

2-Ω & 3-Ω are in series,

$$i(\infty) = \frac{10}{2+3} = 2 \text{ A at } t > 0.$$

Thevenin Resistance across inductor,

$$R_{th} = 2 + 3 = 5 \Omega.$$

for time constant,


$$\tau = \frac{L}{R_{th}} = \frac{1}{3} \times \frac{1}{5} = \frac{1}{15} \text{ s.}$$

Thus, $i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$

$$= 2 + (5-2)e^{-15t}$$

$$i(t) = 2 + 3e^{-15t} \text{ A } t > 0.$$

PRC Prob 1:

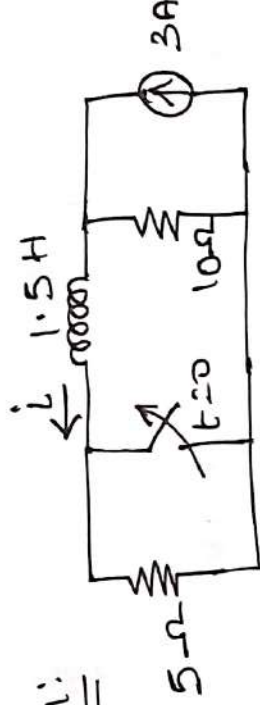

The switch in fig has been closed for a long time. It opens at $t=0$ find $i(t)$ for $t > 0$.

Solution: for $t < 0$ - Switch closed, so inductor short circuited and 5Ω & 10Ω are short circuited (no current flow through 5Ω & 10Ω).


$$i = 3 \text{ A } t < 0.$$

So initial current through inductor cannot change instantaneously!

$$i(0) = i(0^-) = 3 \text{ A } t = 0$$

for $t > 0$ Switch opened, inductor like short circuit, the current i_1 by CDR
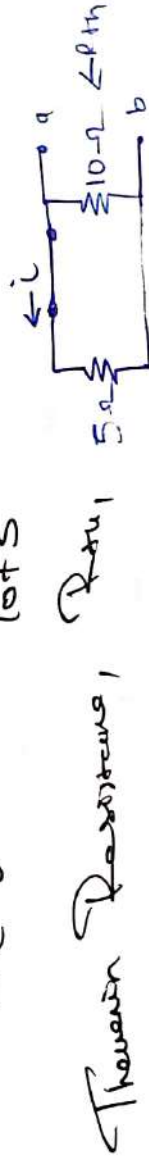
$$i(\infty) = 3 \times \frac{10}{10+5} = 2 \text{ A } t > 0$$



$$R_{th} = \frac{5 \times 10}{10+5} = \frac{50}{15} = 3 \frac{2}{3} \Omega$$

$$= 5 + 10 = 15 \Omega$$

Time Constant,

$$\tau = \frac{L}{R_{th}} = \frac{1.5}{3 \frac{2}{3}} = 0.4 \text{ s}$$


$$= \frac{1.5}{15} = 0.1$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$= 2 + [3 - 2] e^{-t/0.1}$$

$$i(t) = (2 + e^{-10t}) \text{ A}, t > 0.$$

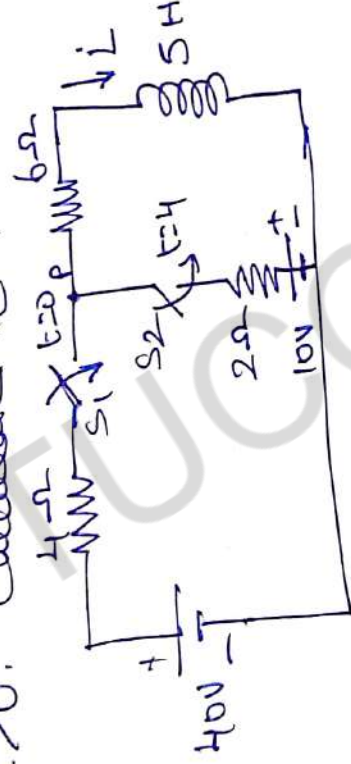Ex 2: At $t=0$, Switch 1 in fig is closed, and Switch 2 is closed 4 s later. Find $i(t)$ for $t > 0$. Calculate i for $t=2\text{ s}$ and $t=5\text{ s}$.



Solution: Need to consider two time intervals,

$t < 0$, $0 < t < 4$, $t > 4$ Separately.

→ for $t < 0$ → switches S_1 & S_2 are open, so

$$i(0^-) = i(0) = 0$$

→ for $0 < t < 4$ S_1 is closed so 4 s 6Ω are in series.

$$i(\infty) = \frac{40}{4+6} = 4 \text{ A}$$

$$R_{\text{th}} = 4+6 = 10\Omega$$

$$\tau = \frac{L}{R_{\text{th}}} = \frac{5}{10} = \frac{1}{2} = 0.5 \text{ s}$$

Then,

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$i(t) = 4 + (0 - 4)e^{-2t} = 4(1 - e^{-2t}) \text{ A}$$

$$0 < t < 4$$

→ for $t > 4$, S_2 is closed, 10 V source is connected. This sudden change does not affect the inductor current because the current cannot change abruptly. The initial current is,

$$i(4) = 4(1 - e^{-8}) \approx 4 \text{ A}$$

To find $i(\infty)$, let V be the voltage at node P in fig, using KCL,

$$\frac{40 - V}{4} + \frac{10 - V}{2} = \frac{V}{6}$$

$$\frac{40}{4} - \frac{V}{4} + \frac{10}{2} - \frac{V}{2} = \frac{V}{6}$$

$$10 + 5 - \frac{V}{4} - \frac{V}{2} - \frac{V}{6} = 0$$

$$-V \left[\frac{1}{4} + \frac{1}{2} + \frac{1}{6} \right] = -15 \Rightarrow V = 16.3636$$

$$i = \frac{V}{6} = \frac{16.3636}{6} = 2.727 \text{ A}$$

$$\therefore i(\infty) = \underline{\underline{2.727 \text{ A}}}$$

Thevenin resistance at inductor terminal,

$$R_{th} = [4 \parallel 2] + 6 = \frac{4 \times 2}{2} + 6 = \frac{22}{3} \Omega$$

$$Z = \frac{I}{R_{th}} = \frac{5}{22/3} = \frac{15}{22} \text{ A}$$

$$\therefore i(t) = i(\infty) + [i(4) - i(\infty)] e^{-(t-4)/\tau} \quad t \geq 4$$

[Note: $(t-4)$ is time delay]

$$i(t) = 2.727 + (4 - 2.727) e^{-(t-4)/\tau} - 2.727 + 1.273 e^{-0.6818(t-4)}$$

$$i(t) = 2.727 + 1.273 e^{-1.4667(t-4)}, \quad t \geq 4$$

$$\therefore i(t) = \begin{cases} 0, & t < 0 \\ 4(1 - e^{-2t}), & 0 < t < 4 \\ -2.727 + 1.273 e^{-1.4667(t-4)}, & t > 4 \end{cases}$$

At: $t = 2$


$$i(2) = 4(1 - e^{-4}) = 3.93 \text{ A}$$

$t = 4$

$$i(4) = 2.727 + 1.273 e^{-1.4667}$$

$$= 3.02 \text{ A}$$

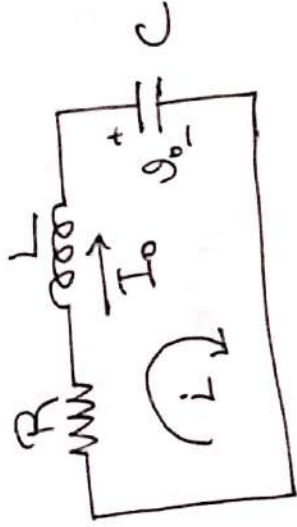STUCORAPP THE SOURCE-FREE SERIES RLC CIRCUIT



Consider Series RLC Circuit,
initial Capacitor Voltage $\rightarrow V_0$ } at $t=0$
initial Inductor Current $\rightarrow I_0$ }

\rightarrow the initial value of the derivative of

$$i, \quad \frac{di(t)}{dt} = -\frac{1}{L} [Ri_0 + V_0]$$

[This equation used to find A₂ Constant].

\rightarrow Characteristic equation of i ,
[roots of equation]

$$S_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$S_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

where $\alpha = \frac{R}{2L}$ γ $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\therefore S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Thus, Natural response of the Series RLC

circuit is,

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

A_1 find by initial value $i(0)$

A_2 find by $\frac{di(0)}{dt}$

Based on s_1 & s_2 there are three types of solutions

① If $\alpha > \omega_0 \rightarrow$ Overdamped Case

Response is,

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

② Critically Damped Response

$$\alpha = \omega_0$$

$$s_1 = s_2 = -\alpha = -\frac{R}{2L}$$

Response is,

$$i(t) = (A_2 + A_1 t) e^{-\alpha t}$$

③ $\alpha < \omega_0$ Underdamped Case

$$s_1 = -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha + j\omega_d$$

$$s_2 = -\alpha - \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha - j\omega_d$$

$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ = damped frequency

$\omega_0 \rightarrow$ Undamped frequency

Response is,


$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

time constant $\rightarrow 1/\alpha$

Period $\rightarrow T = 2\pi/\omega_d$

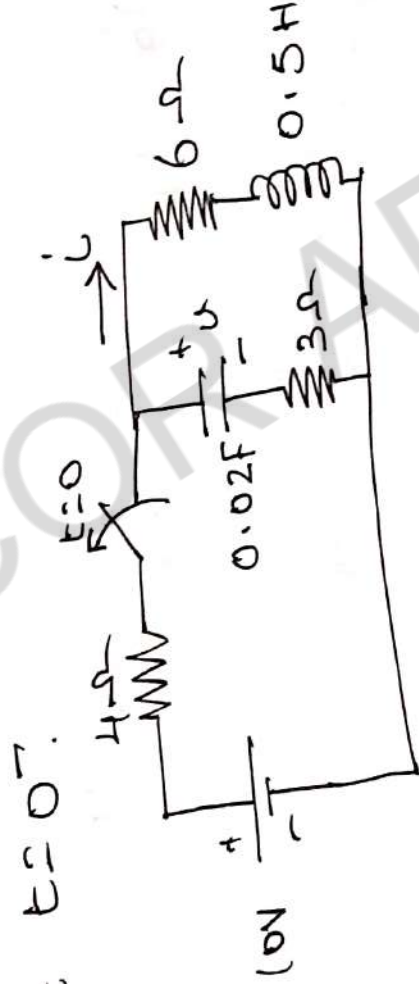Example Problem 1:

find $i(t)$ in the circuit. Assume that the circuit has reached steady state at $t=0^-$.



Solution: for $t < 0 \rightarrow$ Switch is closed.

The capacitor behaves like open circuit, & Inductor acts like short circuit, then the equivalent circuit is,




initial current through Inductor $i(0) = \frac{10}{4+6} = 1\text{ A}$ and voltage across $6\text{-}\Omega$ [voltage across $6\text{-}\Omega$]

$i(0) \rightarrow$ Current through inductor

$v(0) \rightarrow$ Voltage across capacitor.

* for $t > 0$, \rightarrow Switch opened, equivalent

Circuit is, 6Ω & 3Ω are in Series.

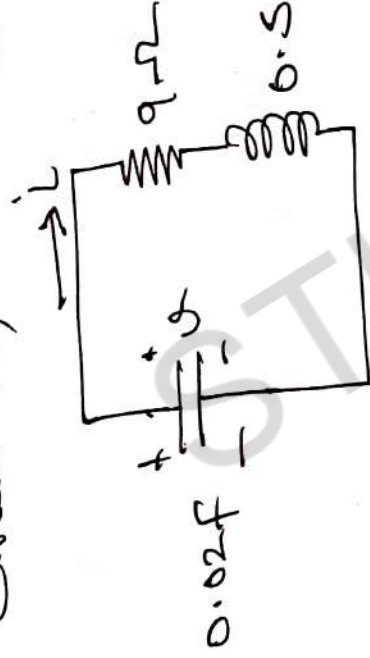

Source free
RLC circuit

Roots are calculated as,

$$\alpha = \frac{R}{2L} = \frac{9}{2 \times 0.5} = 9$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.5 \times 0.02}} = 10$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -9 \pm \sqrt{9^2 - 10^2} = -9 \pm \sqrt{81 - 100}$$

$$s_{1,2} = -9 \pm j4.359 \quad [s_{1,2} = -\alpha \pm j\omega_d]$$

$\alpha < \omega_0 \rightarrow$ Underdamped

$$i(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$

$$i(t) = e^{-9t} (A_1 \cos 4.359t + A_2 \sin 4.359t)$$

Initial conditions.

A_1 & A_2 find initial conditions.

$$\text{At } t=0, \quad i(0) = 1 = A_1$$

then A_2 find by,

$$\textcircled{1} \rightarrow \left. \frac{di}{dt} \right|_{t=0} = -\frac{1}{L} [Ri(0) + V(0)] \\ = -2 [9 - 6] = -6 \text{ A/s}$$

$V(0) = V_0 = -6 \rightarrow$ because of opposite direction of capacitor voltage \rightarrow 6Ω resistor voltage.]

Now, derivative $i(t)$

$$\textcircled{2} \rightarrow \frac{di}{dt} = -9e^{-at} (A_1 \cos 4.359t + A_2 \sin 4.359t) \\ + e^{-9t} (4.359) [-A_1 \sin 4.359t + A_2 \cos 4.359t]$$

Imposing the two equations, $\textcircled{1}$ & $\textcircled{2}$ at $t=0$

$$-6 = -9 [A_1 + 0] + 4.359 [0 + A_2] \\ -6 = -9 [1] + 4.359 [A_2] \quad [A_1 = 1]$$

$$A_2 = \frac{-6 + 9}{4.359} = \frac{3}{4.359} = 0.6882$$

Sub values A_1 & A_2 in $i(t)$

Complete response,

$$i(t) = e^{-at} (\cos 4.359t + 0.6862 \sin 4.359t) \quad A$$

///

STUCOR APP

Source free Parallel RLC ckt.

$(\alpha > \omega_0)$ Overdamped

$$V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$(\alpha = \omega_0)$ Critically Damped case

$$V(t) = (A_1 + A_2 t) e^{-\alpha t}$$

$(\alpha < \omega_0)$ Under damped case.

$$s_{1,2} = -\alpha \pm j\omega_d$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$V(t) = e^{-\alpha t} (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t))$$

$$\frac{V_0}{R} + I_0 + C \frac{dV(0)}{dt} = 0$$

$$\frac{dV(0)}{dt} = -\frac{(V_0 + RI_0)}{RC}$$

In the parallel circuit find $V(t)$ for $t > 0$,
 assuming $V(0) = 5V$, $i(0) = 0$, $L = 1H$, $C = 10mF$
 transfer these values:

$$R = 1.923 \Omega, R = 5 \Omega, R = 6.25 \Omega$$

we get

$$\text{if } R = 1.923 \Omega$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 1.923 \times 10 \times 10^{-3}} = \underline{\underline{26}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 10 \times 10^{-3}}} = \underline{\underline{10}}$$

So $\alpha > \omega_0$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -26 \pm j50$$

∴ the corresponding response is

$$V(t) = A_1 e^{-26t} + A_2 e^{-50t}$$

Initial condition to get A_1 & A_2

$$V(0) = 5 = A_1 + A_2$$

$$\frac{dV(t)}{dt} = -\frac{V(0) + R i(0)}{RC} = -\frac{5 + 0}{1.923 \times 10 \times 10^{-3}} = \underline{\underline{-260}}$$

By differentiating

$$\frac{dV}{dt} = -2A_1 e^{-26t} - 50A_2 e^{-50t}$$

At $t=0$

$$-260 = -2A_1 - 50A_2$$

$$A_1 = -0.2083$$

$$A_2 = 5.208$$

Subs A_1 & A_2

$$v(t) = -0.2083e^{-2t} + 5.208e^{-50t}$$

$$\underline{v(0) = 5}$$

$$R = 50\Omega$$

$$x = \frac{1}{2 \times 5 \times 10^{-3}} = \underline{\underline{10}}$$

while $\omega_0 = 10$ remains the same.

$\omega = \omega_0 = 10$, the response is critically damped,

$$s_1 = s_2 = -10.$$

$$v(t) = (A_1 + A_2 t) e^{-10t}$$

to get A_1 & A_2

$$v(0) = 5 = A_1$$

$$\frac{dv(t)}{dt} = -\frac{v(0) + R \cdot 0}{RC} = -\frac{5 + 0}{5 \times 10^{-3}} = \underline{\underline{-100}}$$

by diff

$$\frac{dv}{dt} = (-10A_1 - 10A_2 t + A_2) e^{-10t}$$

At $t=0$

$$-100 = -10A_1 + A_2$$

$$A_1 = 5$$

$$A_2 = -50$$

$$v(t) = \underline{\underline{(5 - 50t) e^{-10t}}}$$

Case 3When $R = 6.25 \Omega$

$$V = \frac{1}{R_{TC}} = \frac{1}{2.5 \times 10^{-3}} = \underline{\underline{8}}$$

While $\omega = 10$ remains the same, As $\omega < \omega_0$ in this case

The response is underdamped. The roots of the characteristic eqn

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -8 \pm j6$$

hence

$$v(t) = (A_1 \cos 6t + A_2 \sin 6t) e^{-8t}$$

we obtain A_1 & A_2

$$v(0) = 5 = A_1$$

$$\frac{dv(0)}{dt} = \frac{-v(0) + R i(0)}{RC} = \frac{-5 + 0}{6.25 \times 10^{-3}} = \underline{\underline{-80}}$$

But differentiating

$$\frac{dv}{dt} = (-8A_1 \cos 6t - 8A_2 \sin 6t - 6A_1 \sin 6t + 6A_2 \cos 6t) e^{-8t}$$


At $t=0$

$$-80 = -8A_1 + 6A_2$$

$$A_1 = 5, \quad A_2 = -6.667 \quad \text{Thus}$$

$$v(t) = (5 \cos 6t - 6.667 \sin 6t) e^{-8t}$$

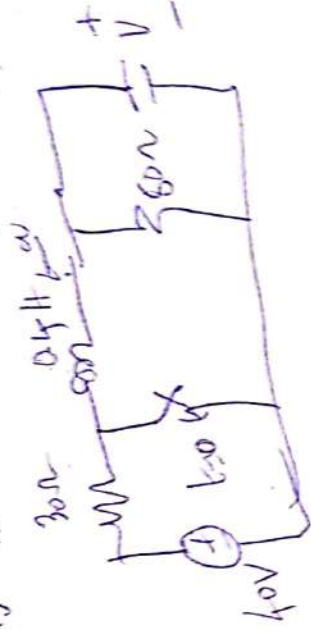Find $V(t)$ for $t > 0$ in the RC circuit.



Sim $t > 0$

$$V(0) = \frac{50 \times 40}{50 + 30} = \underline{\underline{25V}}$$

initial current through the inductor

$$i(0) = -\frac{40}{30 + 50} = \underline{\underline{-0.5A}}$$

$$\frac{dV(t)}{dt} = -\frac{V(t) + E(t)}{RC} = \frac{25 - 50 \times 10^{-6}}{50 \times 20 \times 10^{-6}} = 0$$

$t > 0$ Switch is closed, 30Ω & $10V$ are bypassed.

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 50 \times 20 \times 10^{-6}} = \underline{\underline{500}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.4 \times 20 \times 10^{-6}}} = \underline{\underline{354}}$$

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \\ = -500 \pm \sqrt{250000 - 124992} = \underline{\underline{-500 \pm 354}}$$

$$S_1 = \underline{\underline{-854}} \quad S_2 = \underline{\underline{-146}}$$

Since $\alpha > \omega$, we have overdamped region

$$V(t) = A_1 e^{-854t} + A_2 e^{-1466t}$$

At $t=0$

$$V(0) = 25 = A_1 + A_2$$

$$A_2 = 25 - A_1$$

Taking the derivative of $V(t)$

$$\frac{dV}{dt} = -854 A_1 e^{-854t} - 1466 A_2 e^{-1466t}$$


$$\frac{dV(t)}{dt} = 0 = -854 A_1 - 1466 A_2$$

$$0 = 854 A_1 + 1466 A_2$$

$$A_1 = \underline{\underline{-5.156}}$$

$$A_2 = \underline{\underline{30.16}}$$

$$V(t) = -5.156 e^{-854t} + 30.16 e^{-1466t}$$

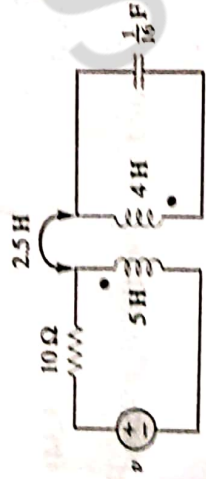Example 13.3**Figure 13.16**

For Example 13.3.

Consider the circuit in Fig. 13.16. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time $t = 1$ s if $v = 60 \cos(4t + 30^\circ)$ V.

Solution:

The coupling coefficient is

$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2.5}{\sqrt{20}} = 0.56$$

indicating that the inductors are tightly coupled. To find the energy stored, we need to calculate the current. To find the current, we need to obtain the frequency-domain equivalent of the circuit.

$$\begin{aligned} 60 \cos(4t + 30^\circ) &\Rightarrow 60 \angle 30^\circ, \quad \omega = 4 \text{ rad/s} \\ 5 \text{ H} &\Rightarrow j\omega L_1 = j20 \Omega \\ 2.5 \text{ H} &\Rightarrow j\omega M = j10 \Omega \\ 4 \text{ H} &\Rightarrow j\omega L_2 = j16 \Omega \\ \frac{1}{16} \text{ F} &\Rightarrow \frac{1}{j\omega C} = -j4 \Omega \end{aligned}$$

The frequency-domain equivalent is shown in Fig. 13.17. We now apply mesh analysis. For mesh 1,

$$(10 + j20)I_1 + j10I_2 = 60 \angle 30^\circ \quad (13.31)$$

For mesh 2,

$$j10I_1 + (j16 - j4)I_2 = 0$$

or

$$I_1 = -1.2I_2 \quad (13.32)$$

Substituting this into Eq. (13.3.1) yields

$$I_2(-12 - j14) = 60/\underline{30^\circ} \Rightarrow I_2 = 3.254/\underline{160.6^\circ} \text{ A}$$

and

$$I_1 = -1.2I_2 = 3.905/\underline{-19.4^\circ} \text{ A}$$

In the time-domain,

$$i_1 = 3.905 \cos(4t - 19.4^\circ), \quad i_2 = 3.254 \cos(4t + 160.6^\circ)$$

At time $t = 1$ s, $4t = 4$ rad = 229.2° , and

$$i_1 = 3.905 \cos(229.2^\circ - 19.4^\circ) = -3.389 \text{ A}$$

$$i_2 = 3.254 \cos(229.2^\circ + 160.6^\circ) = 2.824 \text{ A}$$

The total energy stored in the coupled inductors is

$$\begin{aligned} w &= \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 + Mi_1i_2 \\ &= \frac{1}{2}(5)(-3.389)^2 + \frac{1}{2}(4)(2.824)^2 + 2.5(-3.389)(2.824) = 20.73 \text{ J} \end{aligned}$$

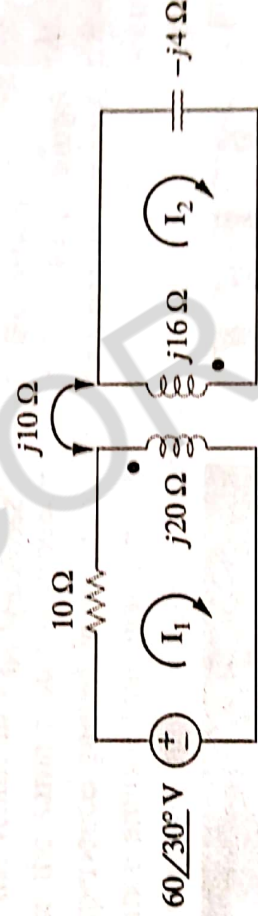


Figure 13.17

Frequency-domain equivalent of the circuit in Fig. 13.16.

Practice Problem 13.3

For the circuit in Fig. 13.18, determine the coupling coefficient and the energy stored in the coupled inductors at $t = 1.5$ s.

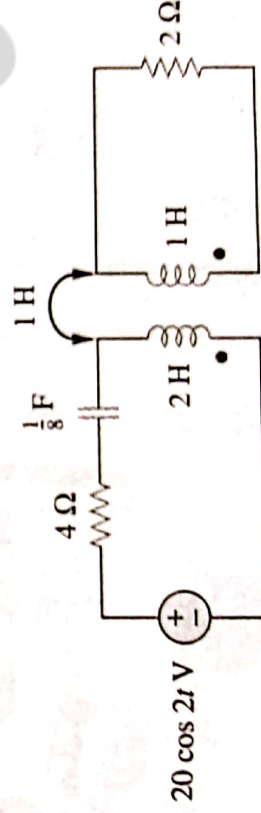


Figure 13.18

For Practice Prob. 13.3.

Answer: 0.7071, 9.85 J.

Example 13.7

An ideal transformer is rated at 2400/120 V, 9.6 kVA, and has 50 turns on the secondary side. Calculate (a) the turns ratio, (b) the number of turns on the primary side, and (c) the current ratings for the primary and secondary windings.

Solution:

(a) This is a step-down transformer, since $V_1 = 2,400 \text{ V} > V_2 = 120 \text{ V}$.

$$n = \frac{V_2}{V_1} = \frac{120}{2,400} = 0.05$$

(b)

$$n = \frac{N_2}{N_1} \Rightarrow 0.05 = \frac{50}{N_1}$$

or

$$N_1 = \frac{50}{0.05} = 1,000 \text{ turns}$$

(c) $S = V_1 I_1 = V_2 I_2 = 9.6 \text{ kVA}$. Hence,

$$I_1 = \frac{9,600}{V_1} = \frac{9,600}{2,400} = 4 \text{ A}$$

$$I_2 = \frac{9,600}{V_2} = \frac{9,600}{120} = 80 \text{ A} \quad \text{or} \quad I_2 = \frac{I_1}{n} = \frac{4}{0.05} = 80 \text{ A}$$

Practice Problem 13.7

The primary current to an ideal transformer rated at 3300/110 V is 3 A. Calculate: (a) the turns ratio, (b) the kVA rating, (c) the secondary current.

Answer: (a) 1/30, (b) 9.9 kVA, (c) 90 A.

Example 13.8

For the ideal transformer circuit of Fig. 13.37, find: (a) the source current I_1 , (b) the output voltage V_o , and (c) the complex power supplied by the source.

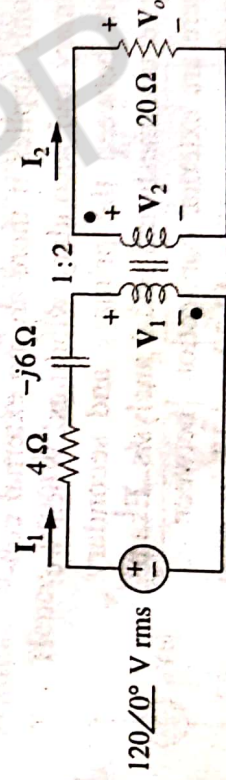


Figure 13.37
For Example 13.8.

Solution:

(a) The 20-Ω impedance can be reflected to the primary side and we get

$$Z_R = \frac{20}{n^2} = \frac{20}{4} = 5 \Omega$$

Thus,

$$\mathbf{Z}_{\text{in}} = 4 - j6 + \mathbf{Z}_R = 9 - j6 = 10.82 \angle -33.69^\circ \Omega$$

$$\mathbf{I}_1 = \frac{120 \angle 0^\circ}{\mathbf{Z}_{\text{in}}} = \frac{120 \angle 0^\circ}{10.82 \angle -33.69^\circ} = 11.09 \angle 33.69^\circ \text{ A}$$

(b) Since both \mathbf{I}_1 and \mathbf{I}_2 leave the dotted terminals,

$$\mathbf{I}_2 = -\frac{1}{n} \mathbf{I}_1 = -5.545 \angle 33.69^\circ \text{ A}$$

$$\mathbf{V}_o = 20 \mathbf{I}_2 = 110.9 \angle 213.69^\circ \text{ V}$$

(c) The complex power supplied is

$$\mathbf{S} = \mathbf{V}_s \mathbf{I}_1^* = (120 \angle 0^\circ)(11.09 \angle -33.69^\circ) = 1,330.8 \angle -33.69^\circ \text{ VA}$$

Practice Problem 13.8

In the ideal transformer circuit of Fig. 13.38, find \mathbf{V}_o and the complex power supplied by the source.

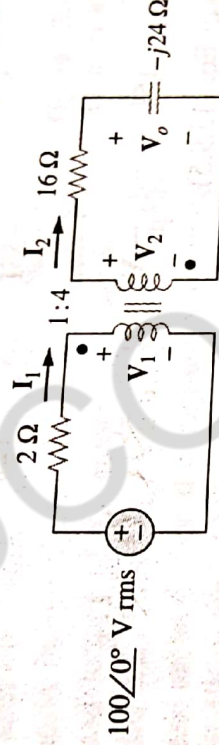


Figure 13.38

For Practice Prob. 13.8.

Answer: $178.9 \angle 116.56^\circ \text{ V}$, $2,981.5 \angle -26.56^\circ \text{ VA}$

Example 13.9

Calculate the power supplied to the $10\text{-}\Omega$ resistor in the ideal transformer circuit of Fig. 13.39.

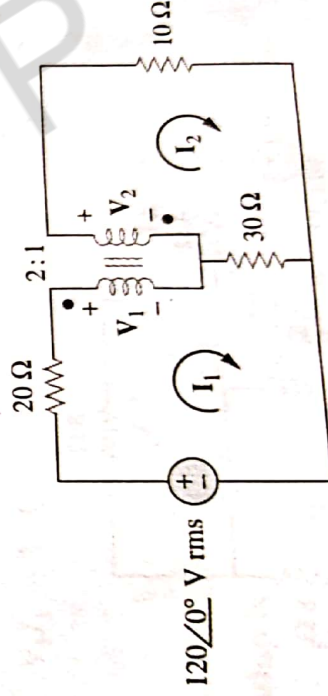


Figure 13.39

For Example 13.9.

Solution:

Reflection to the secondary or primary side cannot be done with this circuit: there is direct connection between the primary and secondary sides due to the $30\text{-}\Omega$ resistor. We apply mesh analysis. For mesh 1,

$$-120 + (20 + 30)I_1 - 30I_2 + V_1 = 0$$

or

$$50I_1 - 30I_2 + V_1 = 120$$

For mesh 2,

$$-V_2 + (10 + 30)I_2 - 30I_1 = 0$$

or

$$-30I_1 + 40I_2 - V_2 = 0$$

At the transformer terminals,

$$V_2 = -\frac{1}{2}V_1$$

$$I_2 = -2I_1$$

(Note that $n = 1/2$.) We now have four equations and four unknowns, but our goal is to get I_2 . So we substitute for V_1 and I_1 in terms of V_2 and I_2 in Eqs. (13.9.1) and (13.9.2). Equation (13.9.1) becomes

$$-55I_2 - 2V_2 = 120$$

and Eq. (13.9.2) becomes

$$15I_2 + 40I_2 - V_2 = 0 \Rightarrow V_2 = 55I_2$$

Substituting Eq. (13.9.6) in Eq. (13.9.5),

$$-165I_2 = 120 \Rightarrow I_2 = -\frac{120}{165} = -0.7272 \text{ A}$$

The power absorbed by the $10\text{-}\Omega$ resistor is

$$P = (-0.7272)^2(10) = 5.3 \text{ W}$$

Practice Problem 13.9

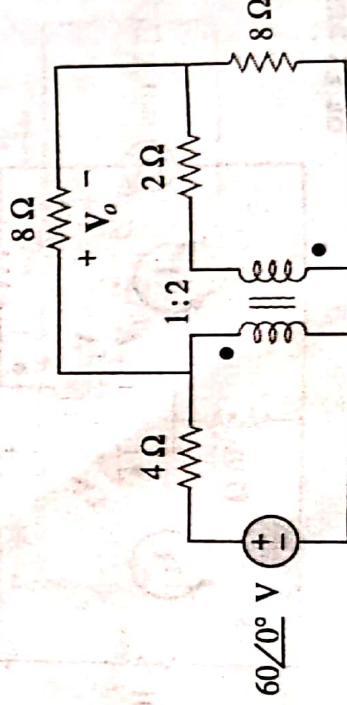
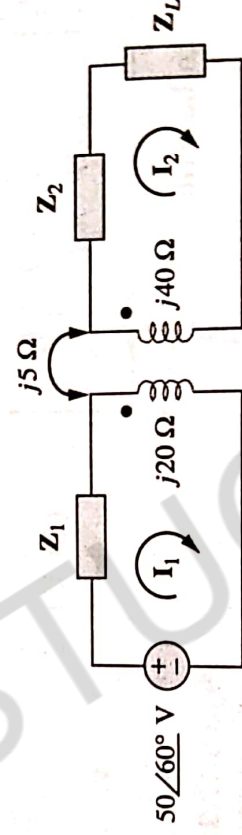
Find V_o in the circuit of Fig. 13.40.

Figure 13.40

For Practice Prob. 13.9.

Example 13.4

In the circuit of Fig. 13.24, calculate the input impedance and current \mathbf{I}_1 . Take $\mathbf{Z}_1 = 60 - j100\ \Omega$, $\mathbf{Z}_2 = 30 + j40\ \Omega$, and $\mathbf{Z}_L = 80 + j60\ \Omega$.

**Figure 13.24**

For Example 13.4.

Solution:

From Eq. (13.41),

$$\begin{aligned}
 \mathbf{Z}_{\text{in}} &= \mathbf{Z}_1 + j20 + \frac{(5)^2}{j40 + \mathbf{Z}_2 + \mathbf{Z}_L} \\
 &= 60 - j100 + j20 + \frac{25}{110 + j140} \\
 &= 60 - j80 + 0.14 \angle -51.84^\circ \\
 &= 60.09 - j80.11 = 100.14 \angle -53.1^\circ \Omega
 \end{aligned}$$

$$I_1 = \frac{V}{Z_{in}} = \frac{50 \angle 60^\circ}{100.14 \angle -53.1^\circ} = 0.5 \angle 113.1^\circ \text{ A}$$

Find the input impedance of the circuit in Fig. 13.25 and the current from the voltage source.

Practice Problem 13.4

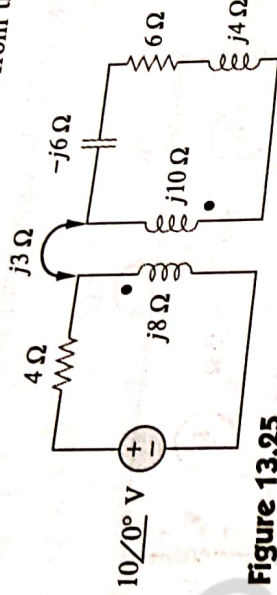


Figure 13.25
For Practice Prob. 13.4.

Answer: $8.58 \angle 58.05^\circ \Omega$, $1.165 \angle -58.05^\circ \text{ A}$.

Example 13.5

Determine the T-equivalent circuit of the linear transformer in Fig. 13.26(a).

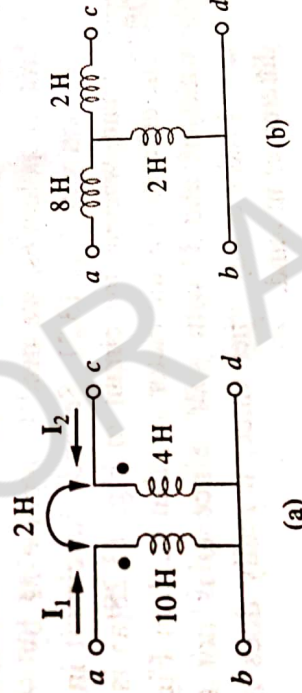


Figure 13.26
For Example 13.5: (a) a linear transformer, (b) its T-equivalent circuit.

Solution:

Given that $L_1 = 10$, $L_2 = 4$, and $M = 2$, the T-equivalent network has the following parameters:

$$L_a = L_1 - M = 10 - 2 = 8 \text{ H}$$

$$L_b = L_2 - M = 4 - 2 = 2 \text{ H}, \quad L_c = M = 2 \text{ H}$$

The T-equivalent circuit is shown in Fig. 13.26(b). We have assumed that reference directions for currents and voltage polarities in the primary and secondary windings conform to those in Fig. 13.21. Otherwise, we may need to replace M with $-M$, as Example 13.6 illustrates.

Practice Problem 13.5

For the linear transformer in Fig. 13.26(a), find the Π equivalent network.

Answer: $L_A = 18$ H, $L_B = 4.5$ H, $L_C = 18$ H.

Example 13.6

Solve for I_1 , I_2 , and V_o in Fig. 13.27 (the same circuit as for Practice Prob. 13.1) using the T-equivalent circuit for the linear transformer.

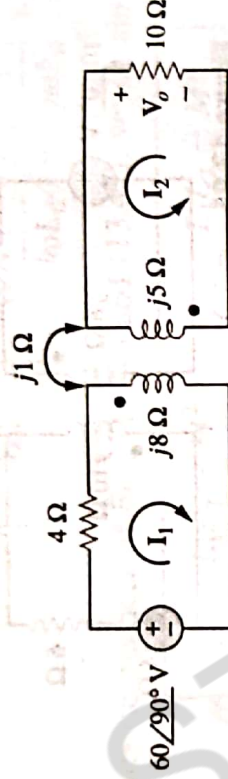


Figure 13.27
For Example 13.6.

Solution:

Notice that the circuit in Fig. 13.27 is the same as that in Fig. 13.10 except that the reference direction for current I_2 has been reversed, just to make the reference directions for the currents for the magnetically coupled coils conform with those in Fig. 13.21.

We need to replace the magnetically coupled coils with the T-equivalent circuit. The relevant portion of the circuit in Fig. 13.27 is shown in Fig. 13.28(a). Comparing Fig. 13.28(a) with Fig. 13.21 shows that there are two differences. First, due to the current reference directions and voltage polarities, we need to replace M by $-M$ to make Fig. 13.28(a) conform with Fig. 13.21. Second, the circuit in Fig. 13.21 is in the time-domain, whereas the circuit in Fig. 13.28(a) is in the frequency-domain. The difference is the factor $j\omega$; that is, L in Fig. 13.21 has been replaced with $j\omega L$ and M with $j\omega M$. Since ω is not specified, we can assume $\omega = 1$ rad/s or any other value; it really does not matter. With these two differences in mind,

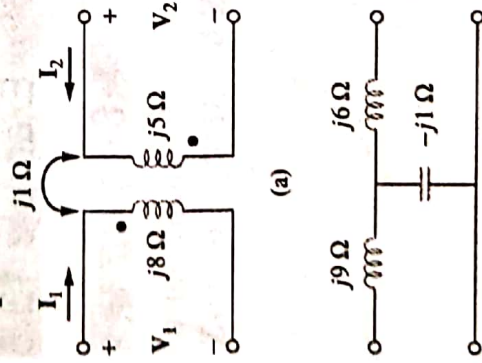


Figure 13.28
For Example 13.6: (a) circuit for coupled coils of Fig. 13.27, (b) T-equivalent circuit.

Inserting the T-equivalent circuit in Fig. 13.28(b) to replace the two coils in Fig. 13.27 gives the equivalent circuit in Fig. 13.29, which can be solved using nodal or mesh analysis. Applying mesh analysis, we obtain

$$j6 = I_1(4 + j9 - j1) + I_2(-j1) \quad (13.6.1)$$

and

$$0 = I_1(-j1) + I_2(10 + j6 - j1) \quad (13.6.2)$$

From Eq. (13.6.2),

$$I_1 = \frac{(10 + j5)}{j} I_2 = (5 - j10) I_2 \quad (13.6.3)$$

$$L_a = L_1 - (-M) = 8 + 1 = 9 \text{ H}$$

$$L_b = L_2 - (-M) = 5 + 1 = 6 \text{ H}, \quad L_c = -M = -1 \text{ H}$$

Thus, the T-equivalent circuit for the coupled coils is as shown in Fig. 13.28(b).

13.5 Ideal Transformers

573

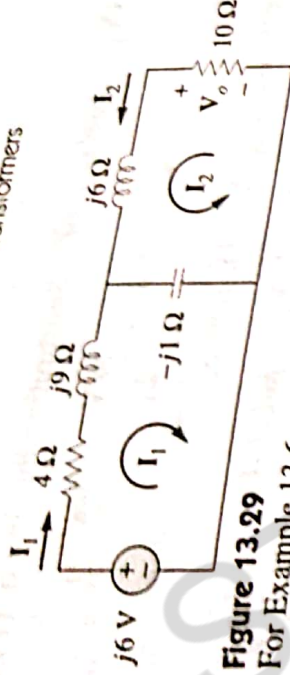


Figure 13.29
For Example 13.6.

Substituting Eq. (13.6.3) into Eq. (13.6.1) gives

$$j6 = (4 + j8)(5 - j10)I_2 - jI_2 = (100 - j)I_2 \approx 100I_2$$

Since 100 is very large compared with 1, the imaginary part of $(100 - j)$ can be ignored so that $100 - j \approx 100$. Hence,

$$I_2 = \frac{j6}{100} = j0.06 = 0.06 \angle 90^\circ \text{ A}$$

From Eq. (13.6.3),

$$I_1 = (5 - j10)j0.06 = 0.6 + j0.3 \text{ A}$$

and

$$V_o = -10I_2 = -j0.6 = 0.6 \angle -90^\circ \text{ V}$$

This agrees with the answer to Practice Prob. 13.1. Of course, the direction of I_2 in Fig. 13.10 is opposite to that in Fig. 13.27. This will not affect V_o , but the value of I_2 in this example is the negative of that of I_2 in Practice Prob. 13.1. The advantage of using the T-equivalent model for the magnetically coupled coils is that in Fig. 13.29 we do not need to bother with the dot on the coupled coils.

Practice Problem 13.6

Solve the problem in Example 13.1 (see Fig. 13.9) using the T-equivalent model for the magnetically coupled coils.

Answer: $13 \angle -49.4^\circ \text{ A}$, $2.91 \angle 14.04^\circ \text{ A}$.